



<i>Name:</i>		
<i>Student ID:</i>	<b>Section: 1</b>	<b>Quiz: 2</b>

Draw  $V_{out}$  versus  $V_{in}$  for the shown circuit assuming  $V_U$  is +5V and  $V_L$  is +3V, the opamp output is limited between +12 and -12V.

