


KING FAHD UNIVERSITY OF PETROLEUM & MINERALS
ELECTRICAL ENGINEERING DEPARTMENT

Dr. Ibrahim O. Habiballah
EE-360

Key Solution

Quiz # 4 Ser. # I.D.# Name:

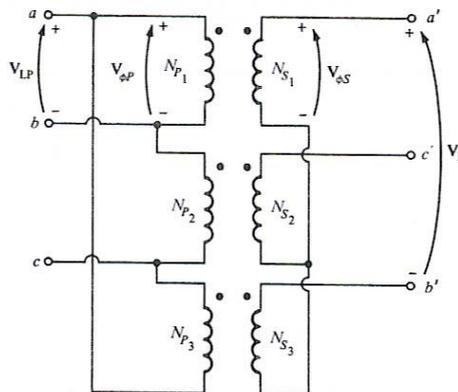A 69 kV (on primary) / 4.16 kV (on secondary), 1000 kVA three-phase transformer is shown below.



1) The rated phase voltage on the primary side is (.....) kV, and the rated phase voltage on the secondary side is (.....) kV

a- 69 ; 2.4

b- 69 ; 4.16

c- 40 ; 2.4

d- 40 ; 4.16

2) The rated phase current on the primary side is (.....) A, and the rated phase current on the secondary side is (.....) A

a- 8.33 ; 138.8

b- 8.33 ; 80.1

c- 4.83 ; 138.8

d- 4.83 ; 80.1