

**KING FAHD UNIVERSITY OF PETROLEUM & MINERALS**

**ELECTRICAL ENGINEERING DEPARTMENT**

**Dr. Ibrahim Habiballah**

**EE 463**

**MAJOR EXAM # II**

**May 7<sup>th</sup> , 2006**

**6:30 - 8:00 pm**

**Key Solution**

**Section:**

**Student Name:**

**Student I.D.#**

**Serial #:**

<b>Question # 1</b>	
<b>Question # 2</b>	
<b>Question # 3</b>	
<b>Total</b>	

Q. 1) A three-phase synchronous generator is connected to a step-up three-phase transformer  $T_1$ , which is connected to a 60-km-long transmission line. At the far end of the line, a step-down transformer bank  $T_2$  is connected. The secondary of  $T_2$  supplies two motor loads  $M_1$  and  $M_2$ . The ratings of the various types of equipment are

Generator: 10 MVA; 12 kV;  $X = 20\%$ ; wye

$T_1$ : 5 MVA; 12/69 kV;  $X = 10\%$ ; delta-wye

$T_2$ : 5 MVA; 69/4.16 kV;  $X = 10\%$ ; wye-delta

$M_1$ : 2 MVA; 4.16 kV;  $X = 20\%$ ; wye

$M_2$ : 1 MVA; 4.16 kV;  $X = 20\%$ ; wye

Transmission line:  $X = 0.5 \text{ Ohm/km}$

For a three-phase fault on the low-voltage terminals of transformer  $T_2$ , calculate the short-circuit current in amperes supplied by the generator assuming that all internal voltages are 1.0 pu. (Choose the generator ratings as bases in the generator circuit.)

(40 Marks)

$$\textcircled{a} \quad S_b = 10 \text{ MVA}$$

$$V_{bg} = 12 \text{ kV}, \quad I_{bg} = \frac{10,000}{\sqrt{3} (12)} = 481 \text{ A}$$

$$V_{bl} = 69 \text{ kV}, \quad Z_{bl} = \frac{(69)^2}{10} = 476.1 \Omega$$

$$V_{bm} = 4.16 \text{ kV}$$


$$X_{T1} = (0.10) \left( \frac{10}{5} \right) = 0.20 \text{ pu}$$

$$X_{T2} = (0.10) \left( \frac{10}{5} \right) = 0.20 \text{ pu}$$

$$X_{M1} = (0.20) \left( \frac{10}{2} \right) = 1.0 \text{ pu}$$

$$X_{M2} = (0.20) \left( \frac{10}{1} \right) = 2.0 \text{ pu}$$
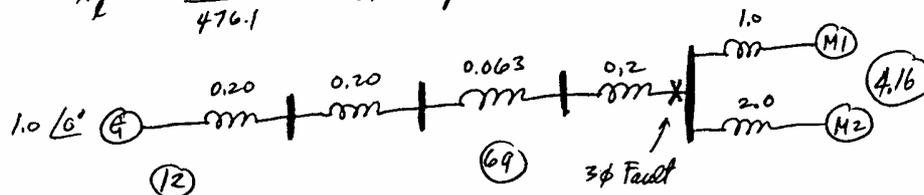
$$X_L = \frac{(0.5)(60)}{476.1} = 0.063 \text{ pu}$$



$$\textcircled{b} \quad I_{Fg} = \frac{1.0 \angle 0^\circ}{j(0.2 + 0.2 + 0.063 + 0.2)} = -j1.508 \text{ pu}$$

$$= (1.508)(481) = 725 \text{ A}$$

Q. 2-a) Obtain the three phase currents of the following sequence components of the current in a

a portion of an unbalanced power system:

$$I_{a1} = 2.5 \angle -90^\circ \text{ pu}$$

$$I_{a2} = 1.65 \angle 90^\circ \text{ pu}$$

$$I_{a0} = 0.85 \angle 90^\circ \text{ pu}$$

(15 Marks)

$$I_a = I_{a0} + I_{a1} + I_{a2} = 0.85 \angle 90^\circ + 2.5 \angle -90^\circ + 1.65 \angle 90^\circ = 0$$

$$I_b = I_{a0} + a^2 I_{a1} + a I_{a2}$$

$$= 0.85 \angle 90^\circ + 1 \angle 240^\circ 2.5 \angle -90^\circ + 1 \angle 120^\circ 1.65 \angle 90^\circ$$

$$= 3.81 \angle 160.5^\circ \text{ pu} = -3.591 + j 1.272$$



$$I_c = I_{a0} + a I_{a1} + a^2 I_{a2}$$

$$= 0.85 \angle 90^\circ + 1 \angle 120^\circ 2.5 \angle -90^\circ + 1 \angle 240^\circ 1.65 \angle 90^\circ$$

$$= 3.81 \angle 19.5^\circ \text{ pu} = 3.591 + j 1.272$$

Q. 2-b) Draw the zero sequence equivalent circuit of the system shown below,

(15 Marks)

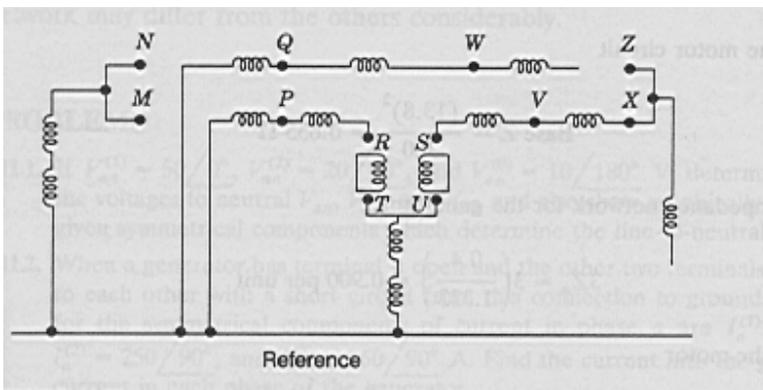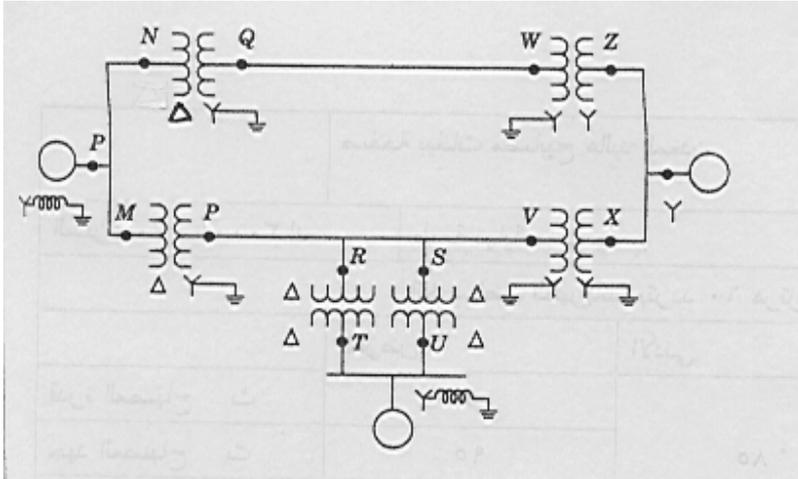

Q. 3) A generator having a solidly grounded neutral and rated 50-MVA, 30-kV has positive-, negative-, and zero-sequence reactances of 25, 15, and 5 percent, respectively. What reactance must be placed in the generator neutral to limit the fault current for a bolted (i.e., solidly grounded) line-to-ground fault to that for a bolted three-phase fault

(30 Marks)

The generator base impedance is

$$Z_B = \frac{(30)^2}{50} = 18 \ \Omega$$

The three-phase fault current is

$$I_{f3\phi} = \frac{1}{0.25} = 4.0 \text{ pu}$$

The line-to-ground fault current is

$$I_{fLG} = \frac{3}{0.25 + 0.15 + 0.05 + 3X_n} = 4.0 \text{ pu}$$

Solving for  $X_n$ , results in

$$\begin{aligned} X_n &= 0.1 \text{ pu} \\ &= (0.1)(18) = 1.8 \ \Omega \end{aligned}$$