

KING FAHD UNIVERSITY OF PETROLEUM AND MINERALS
ELECTRICAL ENGINEERING DEPARTMENT

EE 201 Major Exam I

TIME: 08:00P.M. – 09:30 P.M.

DATE: Monday October 30, 2006

Key Solution

Student's Name: _____


Student's I.D. Number: _____

Section Number: _____

Serial Number: _____

	Grade	Max. Grade
Problem 1		5
Problem 2		5
Problem 3		5
Total		15

Problem 1 (5 Points)

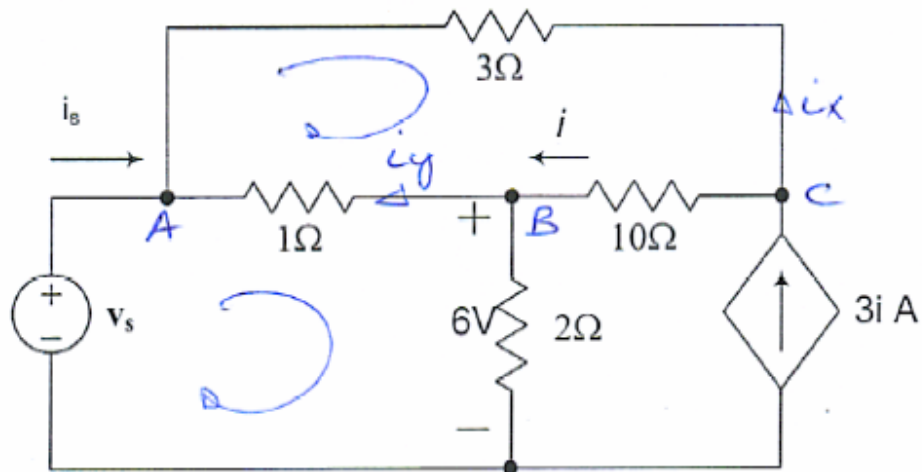

- (a) Find i_s for the circuit shown.
(b) Find v_s for the circuit shown.

Use Ohm's LAW, KCL, and KVL only.

Do not use Mesh or Nodal Analysis

Solution:

Apply KCL at C: $+i - 3i + i_x = 0 \Rightarrow \underline{i_x = 2i}$

" " " B: $i_y + \frac{6}{2} - i = 0 \Rightarrow \underline{i_y = i - 3}$

Apply KVL in the upper loop:

$$-3(2i) + 10i + (i-3) \times 1 = 0 \Rightarrow 5i = 3 \Rightarrow \underline{i = 0.6A}$$

Apply KCL at A:

$$-i_s - (i-3) - 2i = 0 \Rightarrow \underline{i_s = 1.2A}$$

Apply KVL at the bottom left loop

$$v_s = -(i-3) \times 1 + 6 \Rightarrow \underline{v_s = 8.4V}$$

ANSWERS:

$$i_s = 1.2A$$

$$v_s = 8.4V$$

Problem 2 (5 Points)

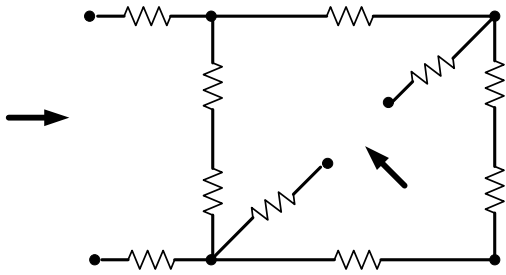


Figure (1)

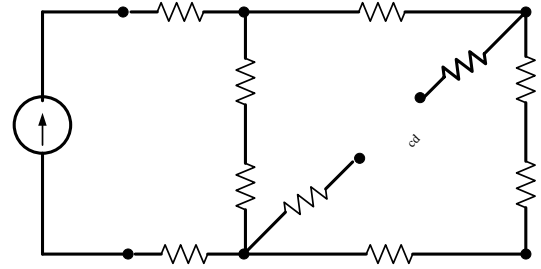


Figure (2)

- (a) For the circuit shown in Figure (1), calculate the equivalent resistance R_{ab} .
- (b) For the circuit shown in Figure (1), calculate the equivalent resistance R_{cd} .
- (c) For the circuit shown in Figure (2), calculate the voltage V_{cd} .

5 Ω

a


(a) $R_{ab} = 5 + [(2+4+6+8) \parallel (14+10)] + 12 = \mathbf{27.9 \Omega}$ **14 Ω**

(b) $R_{cd} = 3 + [(2+14+10) \parallel (4+6+8)] + 9 = \mathbf{22.63 \Omega}$

10 Ω

b

12 Ω

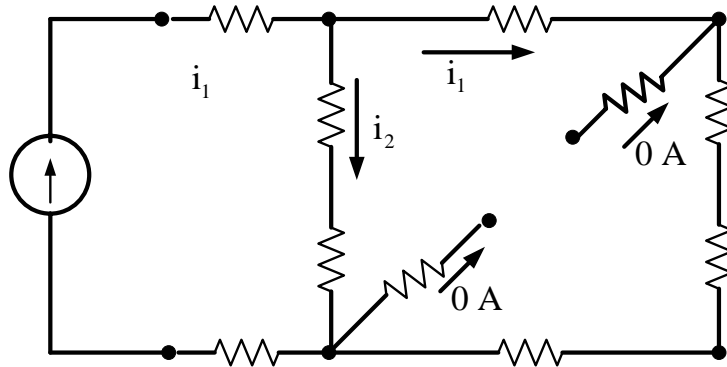

$$(c) \quad i_1 = \frac{(14+10)}{(14+10) + (2+4+6+8)} 10 = \frac{60}{11} = 5.45 \text{ A}$$

$$i_2 = \frac{(2+4+6+8)}{(2+4+6+8) + (14+10)} 10 = \frac{50}{11} = 4.45 \text{ A}$$

KVL on the upper loop

$$2i_1 + 3(0) - v_{cd} + 9(0) - 24i_2 = 0$$

$$\Rightarrow v_{cd} = 2i_1 - 24i_2 = 2\left(\frac{60}{11}\right) - 24\left(\frac{50}{11}\right) = \frac{-1080}{11} = -98.18$$

OR KVL on the lower loop


$$v_{cd} + 3(0) + 18i_1 + 9(0) = 0$$

$$\Rightarrow v_{cd} = -18i_1 = -18\left(\frac{60}{11}\right) = \frac{-1080}{11} = -98.18$$

10 A

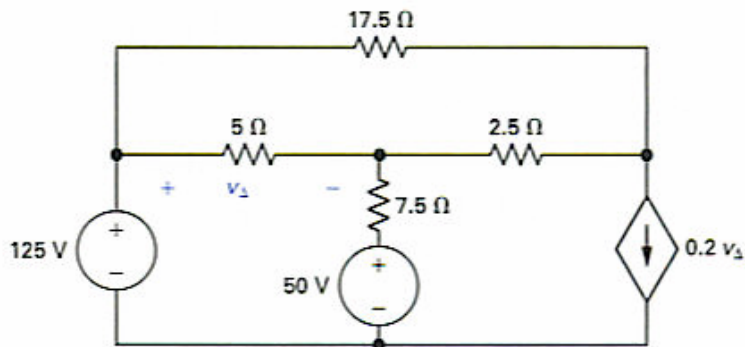
Problem 3 (5 Points)

For the circuit shown below, use **mesh analysis** to find the power (absorbed or delivered) by each of the three sources.



Solution

P 4.34

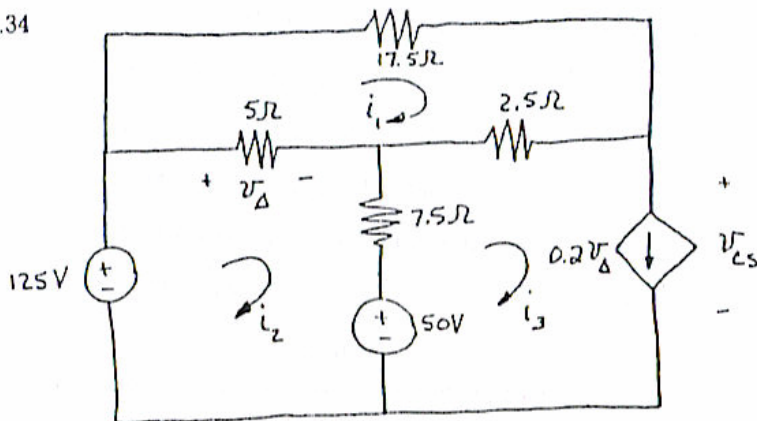

Mesh equations:

$$25i_1 - 5i_2 - 2.5i_3 = 0$$

$$75 = -5i_1 + 12.5i_2 - 7.5i_3$$

Constraint equations:

$$i_3 = 0.2v_{\Delta}$$

$$v_{\Delta} = 5(i_2 - i_1)$$

Solving, $i_1 = 3.6 \text{ A}$; $i_2 = 13.2 \text{ A}$; $i_3 = 9.6 \text{ A}$

$$v_{\Delta s} = 125 - v_{\Delta} - 2.5(i_3 - i_1) = 125 - 48 - 2.5(9.6 - 3.6) = 62 \text{ V}$$

$$p_{\Delta s} = (62)(9.6) = 595.2 \text{ W (abs)}$$