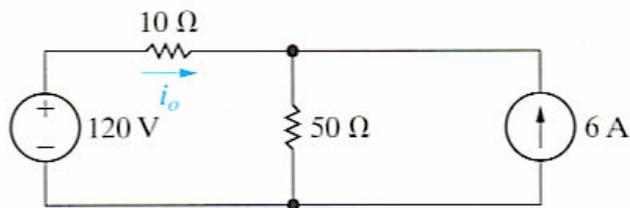


KING FAHD UNIVERSITY OF PETROLEUM & MINERALS
ELECTRICAL ENGINEERING DEPARTMENT
EE-201 ELECTRIC CIRCUITS
Dr. Ibrahim O. Habiballah

Sec: 8 Quiz # 1 Ser. # Name:

I.D.#

For the circuit shown below, find the value of the current " i_o ".



Solution:

By KCL

$$i_{50} = i_o + 6$$

By KVL

$$120 = 10(i_o) + 50(i_{50})$$

Solve for i_o

$$i_o = -3 \text{ A}$$