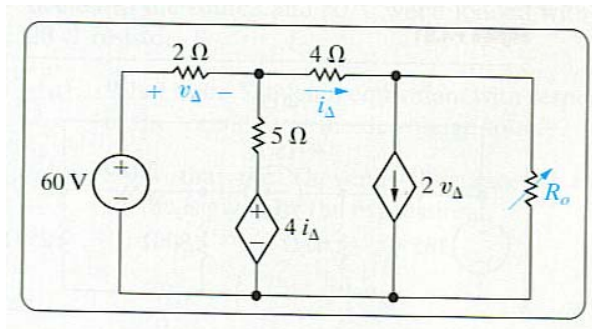


KING FAHD UNIVERSITY OF PETROLEUM & MINERALS
ELECTRICAL ENGINEERING DEPARTMENT
EE-201 ELECTRIC CIRCUITS
Dr. Ibrahim O. Habiballah


Sec: 9 Quiz # 3 Ser. # Name:

I.D.#

For the circuit shown below, find the maximum power transfer to R_o .



Solution

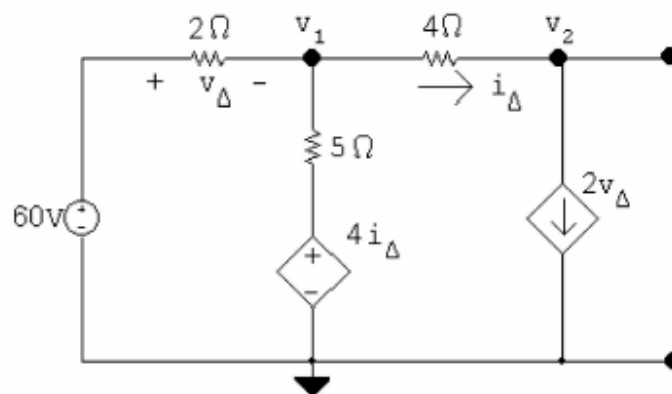

Node voltage equations:

$$\frac{v_1 - 60}{2} + \frac{v_1 - 4i_\Delta}{5} + \frac{v_1 - v_2}{4} = 0$$

$$\frac{v_2 - v_1}{4} + 2v_\Delta = 0$$

Constraint equations:

$$v_\Delta = 60 - v_1$$

$$i_\Delta = \frac{v_1 - v_2}{4}$$

Place the equations in standard form:

$$v_1 \left(\frac{1}{2} + \frac{1}{5} + \frac{1}{4} \right) + v_2 \left(-\frac{1}{4} \right) + i_{\Delta} \left(-\frac{4}{5} \right) + v_{\Delta}(0) = 30$$


$$v_1 \left(-\frac{1}{4} \right) + v_2 \left(\frac{1}{4} \right) + i_{\Delta}(0) + v_{\Delta}(2) = 0$$

$$v_1(1) + v_2(0) + i_{\Delta}(0) + v_{\Delta}(1) = 60$$

$$v_1(1) + v_2(-1) + i_{\Delta}(-4) + v_{\Delta}(0) = 0$$

Solving, $v_1 = 20 \text{ V}$; $v_2 = -300 \text{ V}$; $i_{\Delta} = 80 \text{ A}$; $v_{\Delta} = 40 \text{ V}$

Short circuit current:

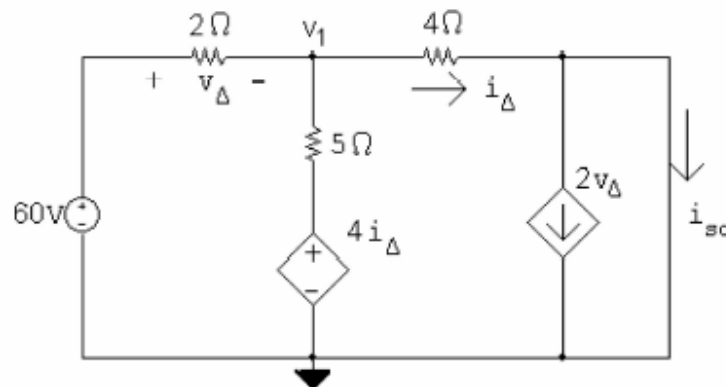

The node voltage equation:

$$\frac{v_1 - 60}{2} + \frac{v_1 - 4i_{\Delta}}{5} + \frac{v_1}{4} = 0$$

The constraint equation:

$$i_{\Delta} = v_1/4$$

Place these equations in standard form:

$$v_1 \left(\frac{1}{2} + \frac{1}{5} + \frac{1}{4} \right) + i_{\Delta} \left(-\frac{4}{5} \right) = 30$$


$$v_1 \left(\frac{1}{4} \right) + i_{\Delta}(-1) = 0$$

Solving, $v_1 = 40 \text{ V}$; $i_{\Delta} = 10 \text{ A}$

Then, $v_{\Delta} = 60 - 40 = 20 \text{ V}$

and $i_{sc} = i_{\Delta} - 2v_{\Delta} = 10 - 40 = -30 \text{ A}$

Thus, $R_{Th} = -300 / -30 = 10 \Omega$

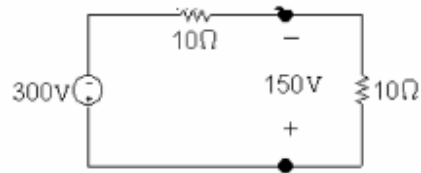

$$P_{\max} = \frac{(150)^2}{10} = 2250 \text{ W}$$