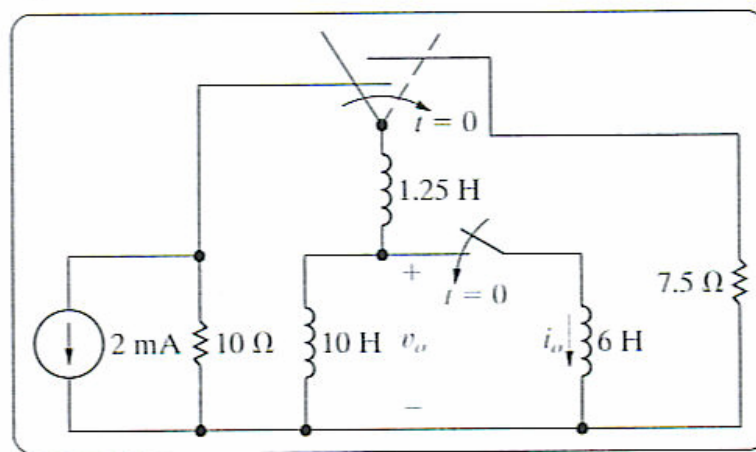


KING FAHD UNIVERSITY OF PETROLEUM & MINERALS
ELECTRICAL ENGINEERING DEPARTMENT
EE-201 ELECTRIC CIRCUITS
Dr. Ibrahim O. Habiballah

Sec: 8 Quiz # 5 Ser. # Name:


I.D.#

Find $v_o(t)$ for $t \geq 0$ in the circuit shown below




Solution


[a] $t < 0$:

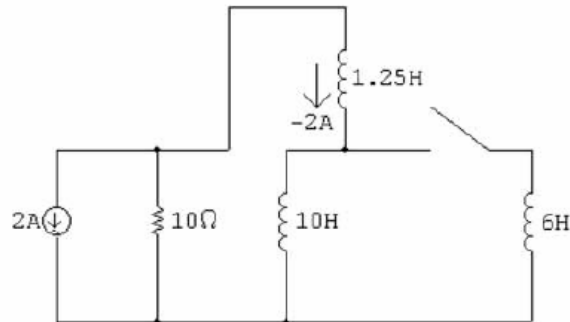

$t = 0^+$:

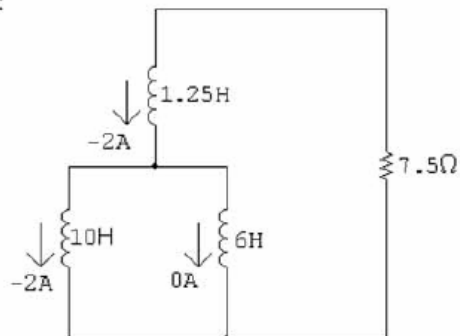


$t > 0$:

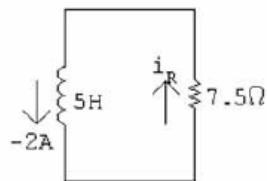

$$i_R = -2e^{-t/\tau} \text{ A}; \quad \tau = \frac{L}{R} = \frac{5}{7.5} = 666.67 \text{ ms} \quad \therefore \frac{1}{\tau} = 1.5$$

$$i_R = -2e^{-1.5t} \text{ A}$$

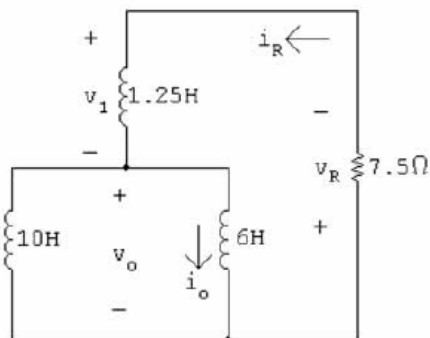

$$v_R = (7.5)(-2e^{-1.5t}) = -15e^{-1.5t} \text{ V}$$

$$v_1 = 1.25[(-1.5)(-2e^{-1.5t})] = 3.75e^{-1.5t} \text{ V},$$

$$v_o = -v_1 - v_R = 11.25e^{-1.5t} \text{ V} \quad t \geq 0^+$$