

KING FAHD UNIVERSITY OF PETROLEUM & MINERALS
ELECTRICAL ENGINEERING DEPARTMENT

Dr. Ibrahim O. Habiballah
 EE-360

Key Solution

Quiz # 3 Ser. # I.D.# Name:

A three-phase transformer bank is formed by interconnecting three single-phase transformers. The three-phase bank is designed to be rated at 300 MVA and 230/34.5 kV. Find the voltage, current, and kVA ratings of each single-phase transformer, both high-voltage and low-voltage windings, if the transformer bank is connected:

- a) delta – delta
- b) wye – delta
- c) wye – wye
- d) delta – wye

$$S = 300 \text{ MVA}$$

$$V_{2L} = 34.5 \text{ kV}$$

$$I_{2L} = \frac{300,000}{\sqrt{3}(34.5)} = 5 \text{ kA}$$

$$V_{1L} = 230 \text{ kV}$$

$$I_{1L} = \frac{300,000}{\sqrt{3}(230)} = 753 \text{ A}$$

Connection	V_{1p}	I_{1p}	MVA ₁	V_{2p}	I_{2p}	MVA ₂
$\Delta - \Delta$	230 kV	435 A	100	34.5 kV	2.9 kA	100
$Y - \Delta$	133 kV	753 A	100	34.5 kV	2.9 kA	100
$Y - Y$	133 kV	753 A	100	20 kV	5 kA	100
$\Delta - Y$	230 kV	435 A	100	20 kV	5 kA	100