

KING FAHD UNIVERSITY OF PETROLEUM & MINERALS
ELECTRICAL ENGINEERING DEPARTMENT

Dr. Ibrahim O. Habiballah
EE-463


Key Solution

Quiz # 3 Serial #

Name:

I.D.#

Consider the 4-bus system shown below. The generators are rated at 11 KV, 100 MVA with subtransient reactance of 10% each. The transformers are rated at 11/110 KV, 100 MVA with a leakage reactance of 5%. The reactances of the lines to a base of 100 MVA and 110 KV are indicated on the figure. Using Thevenin's method, find the short circuit solution (subtransient fault current) for a three-phase symmetrical solid fault at bus 4. Assume pre-fault voltages of 1.0 per unit, and pre-fault currents to be zero.

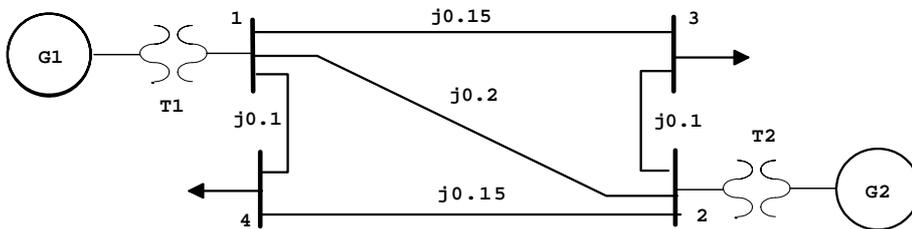

↓ $Z_F = 0$

Gen: $j0.15$ $j0.15$ $j0.15$ $j0.15$

Series $j0.15$ $j0.1$ $j0.2$ $j0.15$ Fault

\Rightarrow

$j0.15$ $j0.15$ $j0.15$ $j0.15$

$j0.1$ $j0.2$ $j0.15$

\Rightarrow

$A = \frac{0.1 * 0.11}{0.1 + 0.11 + 0.15} = \frac{0.1 * 0.11}{0.36} = 0.03055$

$B = \frac{0.11 * 0.15}{0.36} = 0.04583$

$C = \frac{0.1 * 0.15}{0.36} = 0.04166$

\Downarrow

$j0.15$ $j0.15$ $j0.15$ $j0.15$

$j0.18055$ $j0.03055$ $j0.04583$ $j0.04166$

\Rightarrow

$j0.19583$ $j0.19583$ $j0.04166$

$Z_t = j0.09394 + j0.04166 = j0.13560$

$I_{Fault} = \frac{1.0}{j0.13560} = -j7.37463 \text{ pu}$