

9-2  $A = 500 \text{ MCM} = 500,000 \text{ cm}^2/\text{s}$

$$R_{DC,20} = \frac{pL}{A} = \frac{(10.66)(5280)}{500,000} = 0.1126 \text{ } \Omega/\text{mi}$$

$$R_{DC,60} = \frac{M+T_{60}}{M+T_{20}} R_{DC,20} = \left( \frac{241.5+60}{241.5+20} \right) (0.1126) = 0.1298 \text{ } \Omega/\text{mi}$$

$$X = 0.0636 \sqrt{\frac{\mu f}{R_{DC}}} = 0.0636 \sqrt{\frac{(1)(50)}{0.1298}} = 1.24 \approx 12$$

From Table 5,  $\alpha = 1.0107$

$$R_{AC} = \alpha R_{DC} = (1.0107)(0.1298) = 0.1312 \text{ } \Omega/\text{mi}$$

9-4

$$r = \frac{1.5}{2} = 0.75 \text{ cm} = 0.0075 \text{ m}$$

$$r' = r e^{-1/4} = 0.0075 e^{-1/4} = 5.84 \times 10^{-3} \text{ m}$$

$$L_{\text{conductor}} = 2 \times 10^{-7} \ln \frac{D}{r'} = 2 \times 10^{-7} \ln \left( \frac{3}{5.84 \times 10^{-3}} \right) = 1.248 \times 10^{-6} \text{ H/m} = 1.248 \text{ mH/km}$$
$$= 2 \text{ mH/mi}$$

$$L_T = 2 L_{\text{conductor}} = (2)(2) = 4 \text{ mH/mi}$$

$$\underline{9-8} \quad r' = r e^{-1/4} = 0.015 e^{-1/4} = 0.01168 \text{ m}$$

$$\textcircled{a} \quad L_a = 2 \times 10^{-7} \ln \frac{D}{r'} = 2 \times 10^{-7} \ln \left( \frac{4}{0.01168} \right) = 1.167 \times 10^{-6} \text{ H/m}$$
$$= 1.167 \text{ mH/km} = 1.878 \text{ mH/mi}$$

$$\textcircled{b} \quad X_L = 2\pi f L = (2\pi \times 60)(1.167) = 0.44 \text{ } \Omega/\text{km} = 0.708 \text{ } \Omega/\text{mi}$$

9-19

$$r = \frac{d}{2} = \frac{0,25}{(2)(12)} = 0,0104 \text{ ft}$$

$$C_{an} = \frac{2\pi\epsilon}{\ln\left(\frac{D}{r}\right)} = \frac{(2\pi)(8,854 \times 10^{-12})}{\ln\left(\frac{10}{0,0104}\right)} = 8,1 \times 10^{-12} \text{ F/m}$$

9-24

$$\text{GMD} = \sqrt[3]{(7)(7)(10)} = 7,884 \text{ m}$$

$$r = \frac{d}{2} = \frac{5}{2} = 2,5 \text{ cm} = 0,025 \text{ m}$$

$$\textcircled{a} \quad C_{an} = \frac{2\pi\epsilon}{\ln\left(\frac{D}{r}\right)} = \frac{(2\pi)(8,854 \times 10^{-12})}{\ln\left(\frac{7,884}{0,025}\right)} = 9,67 \times 10^{-12} \text{ F/m} = 9,67 \times 10^{-9} \text{ F/km}$$

$$C_T = C_{an} l = (9,67 \times 10^{-9})(100) = 0,967 \times 10^{-6} \text{ F} = 0,967 \mu\text{F}$$

$$\textcircled{b} \quad X_c = \frac{1}{2\pi f C_T} = \frac{1}{(2\pi)(60)(0,967 \times 10^{-6})} = 2,743 \text{ k}\Omega$$

$$\textcircled{c} \quad Y = j \frac{1}{X_c} = j \frac{1}{2,743 \times 10^3} = j 0,364 \times 10^{-3} \text{ S}$$

$$I_{chg} = Y V_{ph} = (0,364 \times 10^{-3}) \left( \frac{138,000}{\sqrt{3}} \right) = 29 \text{ A}$$

9-29

$$l = 40 \text{ km (use short line model)}$$

$$Z = zl = (0.20 + j0.50)(40) = 8 + j20 \ \Omega$$

①  $A = 1.0$

$$B = Z = 8 + j20 = 21.54 \angle 68.2^\circ \ \Omega$$

$$C = 0$$

$$D = 1.0$$

②  $V_R = \frac{33,000}{\sqrt{3}} \angle 0^\circ = 19,052 \angle 0^\circ$

$$I_R = \frac{10,000}{\sqrt{3}(33)} \angle -\cos^{-1} 0.9 = 175 \angle -25.8^\circ \text{ A}$$

$$\begin{aligned} V_S &= AV_R + BI_R = (1.0)(19,052 \angle 0^\circ) + (8 + j20)(175 \angle -25.8^\circ) \\ &= 21,983 \angle 6.5^\circ \text{ V (line-to-neutral)} = 38.1 \text{ kV (line-to-line)} \end{aligned}$$

③  $I_R = \frac{10,000}{\sqrt{3}(33)} \angle \cos^{-1} 0.9 = 175 \angle 25.8^\circ \text{ A}$

$$\begin{aligned} V_S &= (1.0)(19,052 \angle 0^\circ) + (8 + j20)(175 \angle 25.8^\circ) \\ &= 19,162 \angle 11.5^\circ \text{ V (line-to-neutral)} = 33.2 \text{ kV (line-to-line)} \end{aligned}$$

9-31

$l = 200 \text{ km}$  (use medium length line model)

$$Z = zl = (0.10 + j0.35)(200) = 20 + j70 = 72.8 \angle 74^\circ \Omega$$

$$Y = yl = (j5 \times 10^{-6})(200) = j10^{-3} \text{ S}$$

$$\textcircled{a} \quad A = D = \frac{ZY}{2} + 1 = \frac{(20 + j70)(j10^{-3})}{2} + 1 = 0.965 \angle 0.6^\circ$$

$$B = Z = 20 + j70 = 72.8 \angle 74^\circ \Omega$$

$$C = Y \left( \frac{ZY}{4} + 1 \right) = (j10^{-3}) \left[ \frac{(20 + j70)(j10^{-3})}{4} + 1 \right] = 9.825 \times 10^{-4} \angle 90.3^\circ \text{ S}$$

$$\textcircled{b} \quad V_R = \frac{220,000}{\sqrt{3}} \angle 0^\circ = 127,017 \angle 0^\circ \text{ V}$$

$$I_R = \frac{250,000}{\sqrt{3}(220)(0.95)} \angle -\cos^{-1} 0.95 = 690.6 \angle -18.2^\circ$$

$$\begin{aligned} V_S &= AV_R + BI_R = (0.965 \angle 0.6^\circ)(127,017 \angle 0^\circ) + (20 + j70)(690.6 \angle -18.2^\circ) \\ &= 156,767 \angle 15.9^\circ \text{ V (line-to-neutral)} = 271.5 \text{ kV (line-to-line)} \end{aligned}$$

$$\begin{aligned} I_S &= CV_R + DI_R = (9.825 \times 10^{-4} \angle 90.3^\circ)(127,017 \angle 0^\circ) + (0.965 \angle 0.6^\circ)(690.6 \angle -18.2^\circ) \\ &= 639.2 \angle -6.9^\circ \text{ A} \end{aligned}$$

$$\textcircled{c} \quad \text{V.R.} = \frac{V_S/A - V_R}{V_R} = \frac{(156,767 / 0.965) - 127,017}{127,017} \times 100 \% = 27.9 \%$$

**9-34**  $l = 300 \text{ mi}$  (use long line model)

$$Z = 40 + j175 \ \Omega$$

$$Y = j10^{-3} \ \text{S}$$

$$Z_0 = \sqrt{\frac{Z}{Y}} = \sqrt{\frac{40 + j175}{j10^{-3}}} = 423.7 \angle -6.4^\circ$$

$$\gamma l = \sqrt{ZY} = \sqrt{(40 + j175)(j10^{-3})} = 0.4237 \angle 83.6^\circ = 0.0475 + j0.421$$

$$e^{\gamma l} = e^{0.0475 + j0.421} = 1.0486 \angle 24.1^\circ$$

$$e^{-\gamma l} = e^{-0.0475 - j0.421} = 0.9536 \angle -24.1^\circ$$

$$A = D = \cosh \gamma l = \frac{1}{2} (e^{\gamma l} + e^{-\gamma l}) = \frac{1}{2} (1.0486 \angle 24.1^\circ + 0.9536 \angle -24.1^\circ) \\ = 0.914 \angle 1.2^\circ$$

$$\sinh \gamma l = \frac{1}{2} (e^{\gamma l} - e^{-\gamma l}) = \frac{1}{2} (1.0486 \angle 24.1^\circ - 0.9536 \angle -24.1^\circ) \\ = 0.411 \angle 83.9^\circ$$

$$B = Z_0 \sinh \gamma l = (423.7 \angle -6.4^\circ)(0.411 \angle 83.9^\circ) = 174 \angle 77.5^\circ$$

$$C = \frac{1}{Z_0} \sinh \gamma l = \frac{0.411 \angle 83.9^\circ}{423.7 \angle -6.4^\circ} = 9.7 \times 10^{-4} \angle 90.3^\circ$$

(a)  $V_R = \frac{220}{\sqrt{3}} \angle 0^\circ = 127 \angle 0^\circ \ \text{kV}$

$$I_R = \frac{300}{\sqrt{3}(220)(0.9)} \angle -\cos^{-1} 0.9 = 0.875 \angle -25.8^\circ \ \text{kA}$$

$$V_S = AV_R + BI_R = (0.914 \angle 1.2^\circ)(127 \angle 0^\circ) + (174 \angle 77.5^\circ)(0.875 \angle -25.8^\circ) \\ = 242 \angle 29.6^\circ \ \text{kV (line-to-neutral)} = 419 \ \text{kV (line-to-line)}$$

$$I_S = CV_R + DI_R = (9.7 \times 10^{-4} \angle 90.3^\circ)(127 \angle 0^\circ) + (0.914 \angle 1.2^\circ)(0.875 \angle -25.8^\circ) \\ = 0.756 \angle -16.1^\circ \ \text{kA}$$



$$B = Z_0 \sinh \gamma l = (1.077 \angle -1^\circ) (0.371 \angle 83.3^\circ) = 0.3996 \angle 76.3^\circ$$

$$C = \frac{1}{Z_0} \sinh \gamma l = \left( \frac{1}{1.077 \angle -1^\circ} \right) (0.371 \angle 83.3^\circ) = 0.3445 \angle 90.3^\circ$$

$$\begin{aligned} V_s &= AV_R + BI_R = (0.931 \angle 1.05^\circ) (1.0 \angle 0^\circ) + (0.3996 \angle 76.3^\circ) (1.0 \angle 0^\circ) \\ &= 1.1027 \angle 21.56^\circ \text{ pu} = 253.6 \text{ kV} \end{aligned}$$

$$\begin{aligned} I_s &= CV_R + DI_R = (0.3445 \angle 90.3^\circ) (1.0 \angle 0^\circ) + (0.931 \angle 1.05^\circ) (1.0 \angle 0^\circ) \\ &= 0.9969 \angle 21.26^\circ \text{ pu} = (0.9969)(376.5) = 375.3 \text{ A} \end{aligned}$$

$$PF_s = \cos(21.56^\circ - 21.26^\circ) = \cos 0.3^\circ \approx 1.0$$

$$\begin{aligned} P_s &= V_s I_s \cos \theta_s = (1.1027)(0.9969) \cos 0.3^\circ = 1.0993 \text{ pu} \\ &= (1.0993)(150) = 165 \text{ MW} \end{aligned}$$