

KING FAHD UNIVERSITY OF PETROLEUM & MINERALS

ELECTRICAL ENGINEERING DEPARTMENT

Dr. Ibrahim O. Habiballah

EE-360

Quiz 4

ser#:

I.D.:

Name:

A 20-hp 240-V series dc motor has an internal series resistance $R_A + R_S$ equal to 0.25 ohm. At full load, it draws 80 A and runs at 750 r/min. What is the efficiency of the motor at full-load conditions.

Solution:

- (a) At full load, the internal generated voltage of this motor is

$$E_A = V_T - I_A (R_A + R_S)$$

$$E_A = 240 \text{ V} - (80 \text{ A}) (0.25 \Omega) = 220 \text{ V}$$

The output power of the motor is

$$P_{\text{OUT}} = (20 \text{ hp}) (746 \text{ W/hp}) = 14920 \text{ W}$$

The input power to this motor is

$$P_{\text{IN}} = V_T I_L = (240 \text{ V}) (80 \text{ A}) = 19200 \text{ W}$$

The efficiency of this motor at full load is

$$\eta = \frac{P_{\text{OUT}}}{P_{\text{IN}}} \times 100\% = \frac{14920 \text{ W}}{19200 \text{ W}} \times 100\% = 77.7\%$$

- (b) At 30 A, the flux is 52% of the full-load flux, so the internal generated voltage E_{AO} at a speed of 750 rev/min will be

$$E_{AO} = (0.52) (220 \text{ V}) = 114.4 \text{ V}$$

The actual internal generated voltage is

$$E_A = V_T - I_A (R_A + R_S) = 240 \text{ V} - (30 \text{ A}) (0.25 \Omega)$$

$$E_A = 232.5 \text{ V}$$

The actual speed of the motor when it is drawing 30 A is

$$n = \frac{E_A}{E_{AO}} n = \frac{232.5 \text{ V}}{114.4 \text{ V}} (750 \text{ rev/min}) = 1524 \text{ rev/min}$$