

Problem Session #1

Three-Phase Circuits


Problem 1 :

$$\bar{V}_{an} = 120 \angle 0^\circ \Rightarrow V_{ab} = \sqrt{3} 120 \angle 30^\circ$$

$$\bar{V}_{ab} = 208 \angle 30^\circ V$$

$$\bar{V}_{bc} = 208 \angle -90^\circ V$$
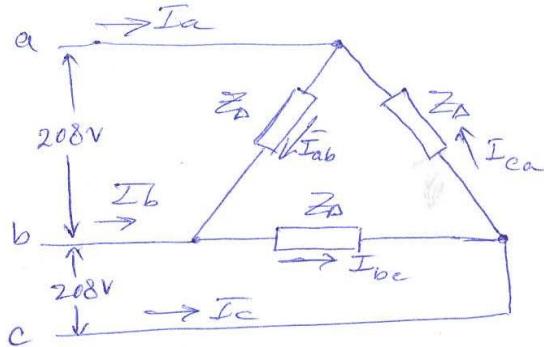
$$\bar{V}_{ca} = 208 \angle +150^\circ V$$



$$(a) \bar{I}_{ab} = \frac{\bar{V}_{ab}}{Z_D} = \frac{208 \angle 30^\circ}{20 \angle -30} = 10.4 \angle 60^\circ A$$

$$\bar{I}_{bc} = \frac{\bar{V}_{bc}}{Z_D} = \frac{208 \angle -90^\circ}{20 \angle -30} = 10.4 \angle -60^\circ A$$

$$\bar{I}_{ca} = \frac{\bar{V}_{ca}}{Z_D} = \frac{208 \angle 150^\circ}{20 \angle -30} = 10.4 \angle 180^\circ A$$

$$(b) \bar{I}_a = \sqrt{3} \bar{I}_{ab} \angle -30^\circ = \sqrt{3} 10.4 \angle 60^\circ \angle -30^\circ = 18 \angle 30^\circ A$$

$$\bar{I}_b = 18 \angle -90^\circ A$$

$$\bar{I}_c = 18 \angle 150^\circ A$$

$$(c) \text{PF} = \cos(-30^\circ) = 0.866 \text{ (leading)}$$

$$(d) S_{3\phi} = 3 V_{ph} \cdot I_{ph} = \sqrt{3} V_L I_L = \sqrt{3} 208 \times 18 = 6485 \text{ VA}$$

$$P_{3\phi} = 3 V_{ph} \cdot I_{ph} \cdot \cos \phi = \sqrt{3} V_L I_L \cos \phi = 3 \times 208 \times 10.4 \times 0.866$$

$$P_{3\phi} = 5.616 \text{ kW}$$

$$Q_{3\phi} = \sqrt{S_{3\phi}^2 - P_{3\phi}^2} = 3.243 \text{ kVAR}$$

Problem 2:

Part(I) The switch is open: $Z_{\Delta} = 10 \angle 30^\circ = 8.66 + j5 \Omega$
 $Z_Y = 2.5 \angle 36.9^\circ = 2 + j1.5 \Omega$

For the Δ -connected load $\Rightarrow V_{ph} = 480V$

$$I_{ph\Delta} = \frac{V_{ph}}{Z_{\Delta}} = \frac{480}{10} = 48 A$$

For the Y -connected load $\Rightarrow V_{ph} = \frac{480}{\sqrt{3}} = 277.1V$

$$I_{phY} = \frac{277.1}{2.5} = 110.85 A$$

(a) $P_{\Delta} = 3 I_{ph}^2 R_{\Delta} = 3 (48)^2 (8.66) = 59.86 \text{ kW}$

$$Q_{\Delta} = 3 I_{ph}^2 X_{\Delta} = 3 (48)^2 (5) = 34.56 \text{ kVAR}$$

$$P_Y = 3 I_{ph}^2 R_Y = 3 (110.85)^2 \times 2 = 73.73 \text{ kW}$$

$$Q_Y = 3 I_{ph}^2 X_Y = 3 (110.85)^2 \times 1.5 = 55.29 \text{ kVAR}$$

(b) $\begin{cases} P_T = P_{\Delta} + P_Y = (59.86 + 73.73) = 133.59 \text{ kW} \\ Q_T = Q_{\Delta} + Q_Y = (34.56 + 55.29) = 89.85 \text{ kVAR} \end{cases}$

(c) $PF_{\Delta} = \cos \theta_{\Delta} = \cos 30^\circ = 0.866 \text{ lagging}$

$$PF_Y = \cos \theta_Y = \cos 36.9^\circ = 0.80 \text{ lagging}$$

$$PF_T = \cos \theta_T, \quad \theta_T = \tan^{-1}\left(\frac{Q_T}{P_T}\right) = \tan^{-1}\left(\frac{89.85}{133.59}\right) = 33.9^\circ$$

$$PF_T = 0.829 \text{ lagging}$$

(d) $P_T = \sqrt{3} V_L I_L \cos \theta_T \Rightarrow I_L = \frac{P_T}{\sqrt{3} V_L \cos \theta_T} = \frac{133.59 \times 10}{\sqrt{3} \cdot 480 \cdot 0.829}$

$$\bar{I}_{tot} = 193.65 A \quad \begin{array}{l} \text{total line current} \\ \text{supplied by the utility} \end{array}$$

Continue ... Problem 2

$$Z_c = 3 \angle -90^\circ \Omega = -j3\Omega \Rightarrow X_c = 3\Omega$$

$$P_c = 0.0 \text{ W}, Q_c = \frac{3 V_{ph}^2}{X_c}, V_{ph} = \frac{480}{\sqrt{3}} = 277.1 \text{ V}$$

$$Q_c = \frac{3 (277.1)^2}{3} \Rightarrow Q_c = 76.8 \text{ KVAR supplied}$$

(a) $P_{tot} = 133.59 \text{ kW}$ supplied by the utility
(the Cap. doesn't absorb power)

$$Q_{tot} = Q_{load} - Q_c = (89.85 - 76.8) = 13.05 \text{ KVAR}$$

Supplied by the utility

(b) $PF_{tot} = \cos \Theta_{tot} \Rightarrow \Theta_{tot} = \tan^{-1} \frac{Q_{tot}}{P_{tot}} = \tan^{-1} \left(\frac{13.05}{133.59} \right)$
 $\Theta_{tot} = 5.6^\circ \Rightarrow PF_{tot} = \cos(5.6^\circ) = 0.995$ lagging

$$I_L = \frac{P_{tot}}{\sqrt{3} V_L \cos \Theta_{tot}} = \frac{133.59 \times 10^3}{\sqrt{3} 480 0.995} = 161.45 \text{ A}$$

$$\boxed{I_{L_{tot}} = 161.45 \text{ A}}$$

Problem 3:

$$\phi = 0.02 \text{ wb} \quad N = 1200$$

$$A = 200 \text{ cm}^2$$

$$B_c = \frac{20 \times 10^{-3}}{200 \times 10^{-4}} = 1 \text{ Tesla}$$

$$H_c = 800 \text{ A.t/m} / H_g = \frac{1}{4\pi 10^7} = 795.77 \times 10^3 \text{ A.t/m}$$

$$F_c = H_c l_c = 800 \times 0.1 = 80 \text{ A.t}$$


$$F_{g_1} = H_g l_{g_1} = 795.77 \times 10^3 \times 10^{-3} = 795.77 \text{ A.t} = F_{g_2}$$

$$B_L = B_r = 0.5 \text{ T} \Rightarrow H_L = H_r = 280 \text{ A.t/m}$$

$$F_L = F_r = 280 \times 0.2 = 56 \text{ A.t}$$

$$F_t = 2 \times F_g + F_c + F_L = 1727.54 \text{ A.t}$$
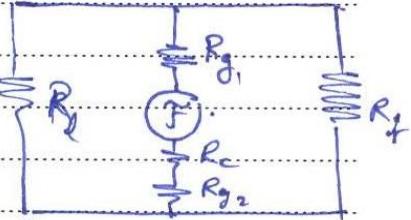
$$I = \frac{F_t}{N} = \frac{1727.54}{1200} = \underline{\underline{1.44 \text{ A}}}$$



Problem 4: Let R_1 be the reluctance of the left-hand portion of the core, R_2 be the reluctance of the left-hand air gap, R_3 be the reluctance of the right-hand portion of the core, R_4 be the reluctance of the right-hand air gap, and R_5 be the reluctance of the center leg of the core. The total reluctance of the coil is

$$R_{\text{tot}} = R_5 + \frac{(R_1 + R_2)(R_3 + R_4)}{R_1 + R_2 + R_3 + R_4}$$

$$R_1 = \frac{l_1}{\mu_r A_1} = \frac{l_1}{\mu_r M_0 A_1} = \frac{1.2 \text{ m}}{2000 \times 4\pi \times 10^7 (0.07 \text{ m})(0.10 \text{ m})} = 68.2 \text{ KA-t/wb}$$

$$R_2 = \frac{l_2}{\mu A_2} = \frac{l_2}{\mu_0 A_2} = \frac{0.0005}{4\pi \times 10^7 (0.07)(0.1)(1.05)} = 54.1 \text{ KA-t/wb}$$

$$R_3 = \frac{l_3}{\mu A_3} = \frac{l_3}{\mu_r M_0 A_3} = \frac{1.2}{2000 \times 4\pi \times 10^7 (0.07)(0.1)} = 68.2 \text{ KA-t/wb}$$

$$R_4 = \frac{l_4}{\mu A_4} = \frac{l_4}{\mu_0 A_4} = \frac{0.0007 \text{ m}}{4\pi \times 10^7 (0.07 \text{ m})(0.1 \text{ m})(1.05)} = 78.5 \text{ KA-t/wb}$$

$$R_5 = \frac{l_5}{\mu A_5} = \frac{l_5}{\mu_r M_0 A_5} = \frac{0.4 \text{ m}}{2000 \times 4\pi \times 10^7 (0.07 \text{ m})(0.1)} = 22.7 \text{ KA-t/wb}$$

$$R_{\text{tot}} = 22.7 + \frac{(68.2 + 54.1)(68.2 + 78.5)}{68.2 + 54.1 + 68.2 + 78.5} = 88.8 \text{ KA-t/wb}$$

$$\Phi_{\text{tot}} = \frac{\text{NI}}{R_{\text{tot}}} = \frac{NI}{88.8 \text{ KA-t/wb}} = [0.0034 \text{ wb}]$$

This is the flux in the center leg.

$$\Phi_{\text{left}} = \frac{R_3 + R_4}{R_1 + R_2 + R_3 + R_4} \Phi_{\text{tot}} = 0.0018 \text{ wb}$$

$$\Phi_{\text{right}} = \frac{R_1 + R_2}{R_1 + R_2 + R_3 + R_4} \Phi_{\text{tot}} = 0.0016 \text{ wb}$$

$$B_{g\text{left}} = \frac{\Phi_{\text{left}}}{A \times 1.05} = \frac{0.0018}{0.007 \times 1.05} = 0.245 \text{ T}$$

$$B_{g\text{right}} = \frac{\Phi_{\text{right}}}{A \times 1.05} = \frac{0.0016}{0.007 \times 1.05} = 0.22 \text{ T}$$