## **EE 360: Homework #6**

## Problems 9-2, 9-6, 9-29, and 9-30

$$\begin{array}{l} \textbf{3-2} \\ \textbf{A} = 500 \ \text{MCM} = 500,000 \ \text{ai mi/s} \\ \textbf{Ray zo} = \frac{9l}{A} = \frac{(10,60)(5280)}{500,000} = 0.1126 \ \text{sc/mi} \\ \textbf{Ray zo} = \frac{M+7_{60}}{M+7_{20}} \ \textbf{Ray zo} = \left(\frac{241.5+60}{241.5+26}\right)(0.1126) = 0.1298 \ \text{sc/mi} \\ \textbf{X} = 0.0636 \ \sqrt{\frac{Mf}{Roc}} = 0.0636 \ \sqrt{\frac{(1750)}{0.1298}} = 1.24 \approx 1.2 \\ \textbf{From Table 5}, \quad \textbf{X} = 1.0107 \\ \textbf{Re} = \textbf{XRoc} = (1.0107)(0.1298) = 0.1312 \ \text{sc/mi} \end{array}$$

9-6

(a) 
$$\Gamma' = \Gamma e^{-V/4} = 0.02 e^{-V/4} = 0.0156 \text{ m}$$

(b)  $GMR_b = \sqrt{d\Gamma'} = \sqrt{(0.08)(0.0156)} = 0.0353 \text{ m}$ 

(c)  $X_L = 0.2794 \left(\frac{f}{60}\right) \log \frac{GMD}{GMR_b} = 0.2794 \left(\frac{60}{60}\right) \log \left(\frac{608}{0.0253}\right) = 0.6248 \text{ s. lmi}$ 
 $= 0.3883 \text{ s. l/km}$ 
 $X_T = 2 \times L = (2)(0.3883) = 0.7766 \text{ s. l/km}$ 

1= 40 km (use short him model)

$$Z = 3l = (0,20+j0,50)(40) = 8+j20 \text{ s}$$

A = 1,0

$$B = Z = 8+j20 = 21.54 / 68.2^{\circ} \text{ s}$$

C = 0

$$D = 1,0$$

We =  $\frac{33,000}{\sqrt{3}} / \frac{10^{\circ}}{0} = 19,052 / \frac{10^{\circ}}{0}$ 

$$I_R = \frac{10,000}{\sqrt{3}(33)} / \frac{-\cos^{-7} aq}{2} = 175 / \frac{-25.8^{\circ}}{2} A$$

Vs =  $AV_R + BI_R = (1,0)(19,052 / \frac{10^{\circ}}{0}) + (8+j20)(175 / \frac{-25.8^{\circ}}{0})$ 

= 21,983 / 660° V (line-to-rubar) = 38.1 kV (line-to-line)

E I\_R =  $\frac{10,000}{\sqrt{5}(33)} / \frac{\cos^{-7} aq}{2} = 175 / \frac{85.8^{\circ}}{2} A$ 

$$V_S = (1,0)(19,052 / \frac{10^{\circ}}{2}) + (8+j20)(175 / \frac{125.8^{\circ}}{2})$$

= 19,162 / 11.5° V (line-to-reader) = 33.2 kV (line-to-line)

9-30
$$l = 80 \text{ mi } (NAR \text{ melum length line model})$$

$$A = D = \frac{ZY}{2} + 1 = \frac{(10+j50)(j30\times10^{-5})}{2} + 1 = 0.9925 \frac{10.1^{\circ}}{2}$$

$$B = Z = 10+j50 = 51 \frac{178.7^{\circ}}{2} \text{ s}$$

$$C = Y(\frac{ZY}{4} + 1) = (j30\times10^{-5}) \left[ \frac{(10+j50)(j30\times10^{-5})}{4} + 1 \right] = 2.99\times10^{-4} \frac{190^{\circ}}{4}$$

$$V_R = \frac{230,000}{\sqrt{2}} \frac{10^{\circ}}{2} = 132.790 \frac{10^{\circ}}{2}$$

$$I_{R} = \frac{V_{R}}{Z_{L}} = \frac{132,790 / 0^{\circ}}{150 / 36.9^{\circ}} = 885,3 / -36.9^{\circ} A$$

$$V_{S} = AV_{R} + BI_{R} = (0.9925 / 0.1^{\circ})(132,790 / 0^{\circ}) + (51 / 78.7^{\circ})(885,3 / -36.9^{\circ})$$

= 168, 208 /104° V (hni-to-neutral) = 291.34 KV (lmi-to-line)
$$I_{S} = CV_{R} + DI_{R} = (2.99 \times 10^{-4} / 90^{\circ})(132,790 / 10^{\circ}) + (0.9925 / 10.1^{\circ})(885,3 / -36.9^{\circ})$$
= 855,5 / -34.7° A

6) V.R. = 
$$\frac{V_5/A - V_R}{V_R} = \frac{(291.34/0.9925) - 230}{230} / 002 = 27.6\%$$

$$S_{s} = 3V_{s} \hat{I}_{s}^{*} = (3)(168,268 110.4°) (855,5 / -34.7°) * = 431,7 \times 10° / 45.1° VA$$

$$= (304.7 + j 305,8) MVA$$

$$P_{s} = 304.7 MW$$

$$Q_{s} = 305.8 MVAR$$

(1) 
$$P_R = 2 V_R I_R \cot \theta_R = (3 \times 0.32,790)(885.3) \cot 36.9 = 282 \times 10^6 W = 282 MW$$

$$N = \frac{P_R}{P_S} = \frac{282}{304.7} / 0.0 ?_s = 92.6 ?_s$$