

## EE-465 (Term 162)

I.O. Habiballah

### Solution of HW2

- 5.1 (a)  $\bar{A} = \bar{D} = 1.0 \angle 0^\circ \text{ pu}; \bar{C} = 0. \text{S}$   
 $\bar{B} = \bar{Z} = (0.19 + j0.34)25 = 9.737 \angle 60.8^\circ \Omega$
- (b)  $\bar{V}_R = \frac{33}{\sqrt{3}} \angle 0^\circ = 19.05 \angle 0^\circ \text{ kV}_{\text{LN}}$   
 $\bar{I}_R = \frac{S_R \angle -\cos^{-1}(pf)}{\sqrt{3} V_{R-L-L}} = \frac{10}{\sqrt{3}(33)} \angle -\cos^{-1}(0.9)$   
 $= 0.175 \angle -25.84^\circ \text{ kA}$   
 $\bar{V}_S = \bar{A}\bar{V}_R + \bar{B}\bar{I}_R = (1.0)(19.05) + (9.737 \angle 60.8^\circ)(0.175 \angle -25.84^\circ)$   
 $= 20.45 + j0.976 = 20.47 \angle 2.732^\circ \text{ kV}_{\text{L-N}}$   
 $V_{S-L-L} = 20.47\sqrt{3} = 35.45 \text{ kV}$
- (c)  $\bar{I}_R = 0.175 \angle 25.84^\circ$   
 $\bar{V}_S = \bar{A}\bar{V}_R + \bar{B}\bar{I}_R = (1.0)(19.05) + (9.737 \angle 60.8^\circ)(0.175 \angle 25.84^\circ)$   
 $= 19.15 + j1.701 = 19.23 \angle 5.076^\circ \text{ kV}_{\text{L-N}}$   
 $V_{S-L-L} = 19.23\sqrt{3} = 33.3 \text{ kV}$

$$5.2 \quad (a) \quad \bar{A} = \bar{D} = 1 + \frac{I \bar{Z}}{2} = 1 + \frac{1}{2} (3.33 \times 10^{-6} \times 200 \angle 90^\circ) (0.08 + j0.48) (200) \\ = 1 + (0.0324 \angle 170.5^\circ) = 0.968 + j0.00533 = 0.968 \angle 0.315^\circ \text{ pu}$$

$$\bar{C} = \bar{Y} \left( 1 + \frac{\bar{Y} \bar{Z}}{4} \right) = (6.66 \times 10^{-4} \angle 90^\circ) (1 + 0.0162 \angle 170.5^\circ) \\ = 6.553 \times 10^{-4} \angle 90.155^\circ \text{ S}$$

$$\bar{B} = \bar{Z} = 97.32 \angle 80.54^\circ \Omega$$

$$(b) \quad \bar{V}_R = \frac{220}{\sqrt{3}} \angle 0^\circ = 127 \angle 0^\circ \text{ kV}_{L-N}$$

$$\bar{I}_R = \frac{P_R \angle -\cos^{-1}(pf)}{\sqrt{3} V_{R-L-L} (pf)} = \frac{250 \angle -\cos^{-1} 0.99}{\sqrt{3} (220) (0.99)} = 0.6627 \angle -8.11^\circ \text{ kA}$$

$$\bar{V}_S = \bar{A} \bar{V}_R + \bar{B} \bar{I}_R = (0.968 \angle 0.315^\circ) (127 \angle 0^\circ) + (97.32 \angle 80.54^\circ) (0.6627 \angle -8.11^\circ) \\ = 142.4 + j62.16 = 155.4 \angle 23.58^\circ \text{ kV}_{L-N}$$

$$\bar{V}_{S-L-L} = 155.4 \sqrt{3} = 269.2 \text{ kV}$$

$$\bar{I}_S = \bar{C} \bar{V}_R + \bar{D} \bar{I}_R = (6.553 \times 10^{-4} \angle 90.155^\circ) (127) + (0.968 \angle -0.315^\circ) (0.6627 \angle -8.11^\circ) \\ = 0.6353 - j3.786 \times 10^{-3} = 0.6353 \angle -0.34^\circ \text{ kA}$$

$$(c) \quad V_{RNL} = V_S / A = 269.2 / 0.968 = 278.1 \text{ kV}_{LL}$$

$$\% VR = \frac{V_{RNL} - V_{RFL}}{V_{RFL}} \times 100 = \left( \frac{278.1 - 220}{220} \right) 100 = 26.4\%$$

$$5.7 \quad V_s = \frac{3300}{\sqrt{3}} = 1905.3 \text{ V (Line-to-neutral)}$$

$$0.5 \angle 53.13^\circ = 0.5(0.6 + j0.8) = 0.3 + j0.4$$

$$I = \frac{(900/3)10^3}{0.8 \times V_R} = \frac{375 \times 10^3}{V_R} \text{ A}$$

From the phasor diagram drawn below with  $\bar{I}$  as reference,

$$V_s^2 = (V_R \cos \phi_R + IR)^2 + (V_R \sin \phi_R + IX)^2 \quad (1)$$


$$(1905.3)^2 = \left( 0.8V_R + \frac{375 \times 10^3 \times 0.3}{V_R} \right)^2 + \left( 0.6V_R + \frac{375 \times 10^3 \times 0.4}{V_R} \right)^2$$

From which one gets  $V_R = 1805 \text{ V}$

(a) Line-to-line voltage at receiving end =  $1805\sqrt{3}$   
 $= 3126 \text{ V} \leftarrow$   
 $= 3.126 \text{ kV}$

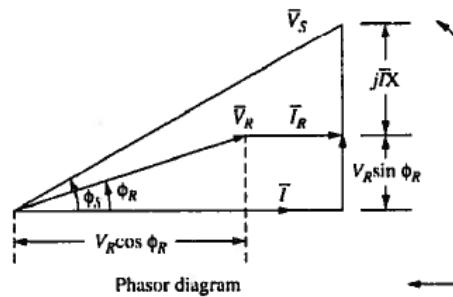(b) Line current is given by

$$I = \frac{375 \times 10^3}{1805} = 207.76 \text{ A} \leftarrow$$



$$5.14 \quad (a) \quad \bar{Z}_C = \sqrt{\frac{\bar{z}}{\bar{y}}} = \sqrt{\frac{0.03 + j0.35}{4.4 \times 10^{-6} \angle 90^\circ}} = 282.6 \angle -2.45^\circ \Omega$$

$$(b) \quad \bar{\gamma}l = \sqrt{\bar{z}\bar{y}}(l) = \sqrt{(0.35128 \angle 85.101^\circ)(4.4 \times 10^{-6} \angle 90^\circ)}(400) \\ = 0.4973 \angle 87.55^\circ = 0.02126 + j0.4968 \text{ pu}$$

$$(c) \quad \bar{A} = \bar{D} = \cosh \bar{\gamma}l = \cosh(0.02126 + j0.4968) \\ = (\cosh 0.02126)(\cos 0.4968 \text{ radians}) + j(\sinh 0.02126)(\sin 0.4968 \text{ radians}) \\ = (1.00023)(0.87911) + j(0.02126)(0.47661) \\ = 0.87931 + j0.01013 = 0.8794 \angle 0.66^\circ \text{ pu} \\ \sinh \bar{\gamma}l = \sinh(0.02126 + j0.4968) \\ = \sinh(0.02126)\cos(0.4968 \text{ radians}) + j(\cosh 0.02126)(\sin 0.4968 \text{ radians}) \\ = (0.02126)(0.87911) + j(1.00023)(0.47661) \\ = 0.01869 + j0.4767 = 0.4771 \angle 87.75^\circ \\ \bar{B} = \bar{Z}_C \sinh(\bar{\gamma}l) = (282.6 \angle -2.45^\circ)(0.4771 \angle 87.75^\circ) \\ = 134.8 \angle 85.3^\circ \Omega \\ \bar{C} = \frac{1}{\bar{Z}_C} \sinh(\bar{\gamma}l) = \frac{0.4771 \angle 87.75^\circ}{282.6 \angle -2.45^\circ} = 1.688 \times 10^{-3} \angle 90.2^\circ \text{ S}$$

$$5.26 \quad (a) \quad \bar{Z}_C = \sqrt{\frac{\bar{z}}{\bar{y}}} = \sqrt{\frac{j0.34}{j4.5 \times 10^{-6}}} = 274.9 \angle 0^\circ = 274.9 \Omega$$

$$(b) \quad \bar{\gamma}l = \sqrt{\bar{z}\bar{y}}(l) = \sqrt{(j0.34)(j4.5 \times 10^{-6})}(300) = j0.3711 \text{ pu}$$

$$(c) \quad \bar{\gamma}l = j(\beta l); \quad \beta l = 0.3711 \text{ pu}$$

$$A = D = \cos(\beta l) = \cos(0.3711 \text{ radians}) = 0.9319 \angle 0^\circ \text{ pu}$$

$$\bar{B} = j Z_C \sin(\beta l) = j(274.9) \sin(0.3711 \text{ radians}) \\ = j99.68 \Omega$$

$$\bar{C} = j \left( \frac{1}{\bar{Z}_C} \right) \sin(\beta l) = j \left( \frac{1}{274.9} \right) \sin(0.3711 \text{ radians}) \\ = j1.319 \times 10^{-3} \text{ S}$$

$$(d) \quad \beta = 0.3711 / 300 = 1.237 \times 10^{-3} \text{ radians/km}$$

$$\lambda = 2\pi / \beta = 5079 \text{ km}$$

$$(e) \quad \text{SIL} = \frac{V_{\text{rated } L-L}^2}{\bar{Z}_C} = \frac{(500)^2}{274.9} = 909.4 \text{ MW } (3\phi)$$

5.28 (a)  $V_R = V_S / A = 500 / 0.9319 = 536.5 \text{ kV}$

(b)  $V_R = V_S = 500 \text{ kV}$

(c)  $\bar{V}_S = \cos(\beta l) \cdot \bar{V}_R + (jZ_C \sin \beta l) \left( \frac{\bar{V}_R}{\frac{1}{Z_C}} \right)$

$$\bar{V}_S = |\cos \beta l + jZ \sin \beta l| V_R$$

$$V_S = 500 / |\cos 0.3711 \text{ radians} + j2 \sin 0.3711 \text{ radians}|$$

$$= 500 / 1.18 = 423.4 \text{ kV}$$

(d)  $P_{\max 3\phi} = \frac{V_S V_R}{X'} = \frac{(500)(500)}{99.68} = 2508 \text{ MW}$

5.38 From Problem 5.14

$$\bar{A} = 0.8794 \angle 0.66^\circ \text{ pu}; \quad A = 0.8794 \text{ and } \theta_A = 0.66^\circ$$

$$\bar{B} = \bar{Z}' = 134.8 \angle 85.3^\circ \Omega; \quad Z' = 134.8 \text{ and } \theta_z = 85.3^\circ$$

Using Eq. (5.5.6)

$$P_{R \max} = \frac{500 \times 500}{134.8} - \frac{(0.8794)(500)^2}{134.8} \cos(85.3^\circ - 0.66^\circ)$$

$$= 1854.6 - 152.4 = 1702 \text{ MW (3}\phi\text{)}$$

For this loading at unity power factor,

$$I_R = \frac{P_{R \max}}{\sqrt{3} V_{RLL} (PF)} = \frac{1702}{\sqrt{3} (500) (1.0)} = 1.966 \text{ kA / Phase}$$

From Table A.4, the thermal limit for 3 ACSR 1113 kcmil conductors is  $3 \times 1.11 = 3.33 \text{ kA/p hase}$ . The current 1.966 kA corresponding to the theoretical steady-state stability limit is well below the thermal limit of 3.33 kA.

5.48 (a)  $SIL = (345)^2 / 300 = 396.8 \text{ MW}$

Neglecting losses and using Eq. (5.4.29)

$$P = \frac{1 \times 0.95 (SIL) \sin 35^\circ}{\sin \left( \frac{2\pi(300)}{5000} \text{ radians} \right)} = 1.48 (SIL) = 1.48(396.8) = 587.3 \text{ MW/line}$$

$$\text{Number of 345-kV lines} = \frac{2000}{587.3} + 1 = 3.4 + 1 \approx 5 \text{ Lines}$$

(b) For 500-kV lines,  $SIL = \frac{(500)^2}{275} = 909.1 \text{ MW}$

$$P = 1.48 (SIL) = 1.48 \times 909.1 = 1345.6 \text{ MW/ Line}$$

$$\text{Number of 500-kV Lines} = \frac{2000}{1345.6} + 1 = 1.49 + 1 \approx 3 \text{ Lines}$$

(c) For 765-kV lines,  $SIL = \frac{(765)^2}{260} = 2250.9 \text{ MW}$

$$P = 1.48 (SIL) = 1.48 \times 2250.9 = 3331.3 \text{ MW/ Line}$$

$$\text{Number of 765-kV lines} = \frac{2200}{3331.3} + 1 = 0.6 + 1 = 2 \text{ Lines}$$

5.57 From Problem 5.23

$$\bar{Z}' = R' + jX' = (11.0 + j134.3) \Omega$$

Based on 40% series compensation, half at each end of the line, the impedance of each series capacitor is

$$\bar{Z}_{CAP} = -jX_{CAP} = -j \frac{1}{2} (0.4)(134.3) = -j26.86 \Omega / \text{phase (at each end)}$$

Using the  $\overline{ABCD}$  parameters from Problem 5.14, the equivalent  $\overline{ABCD}$  parameters of the compensated line are

$$\begin{array}{c} \left[ \begin{array}{c|c} A_{eq} & B_{eq} \\ \hline C_{eq} & D_{eq} \end{array} \right] = \left[ \begin{array}{c|c} 1 & -j26.86 \\ \hline 0 & 1 \end{array} \right] \left[ \begin{array}{c|c} 0.8794 \angle 0.66^\circ & 134.8 \angle 85.3^\circ \\ \hline 1.688 \times 10^{-3} \angle 90.2^\circ & 0.8794 \angle 0.66^\circ \end{array} \right] \\ \text{compensated line} \qquad \text{Sending-end} \qquad \qquad \qquad \text{uncompensated line} \\ \qquad \qquad \qquad \text{series capacitors} \end{array}$$

$$\left[ \begin{array}{c|c} 1 & -j26.86 \\ \hline 0 & 1 \end{array} \right] \\ \text{receiving-end} \\ \text{series capacitors}$$

$$\left[ \begin{array}{c|c} A_{eq} & B_{eq} \\ \hline C_{eq} & D_{eq} \end{array} \right] = \left[ \begin{array}{c|c} 0.9248 \angle 0.64^\circ & 86.66 \angle 82.31^\circ \\ \hline 1.688 \angle 90.2^\circ & 0.9248 \angle 0.64^\circ \end{array} \right]$$