

EE-465 (Term 162)

I.O. Habiballah

Solution of HW3

13.1 From the results of Example 13.2:



$$V(x,t) = \frac{E}{2} U_{-1} \left(t - \frac{x}{v} \right) + \frac{E}{2} U_{-1} \left(t + \frac{x}{v} - 2\tau \right)$$

$$i(x,t) = \frac{E}{2Z_c} U_{-1} \left(t - \frac{x}{v} \right) - \frac{E}{2Z_c} U_{-1} \left(t + \frac{x}{v} - 2\tau \right)$$

For $t = \tau/2 = \frac{l}{2v}$:



$$V \left(x, \frac{\tau}{2} \right) = \frac{E}{2} U_{-1} \left(\frac{l-x}{v} \right) + \frac{E}{2} U_{-1} \left(\frac{x-\frac{3}{2}l}{v} \right)$$
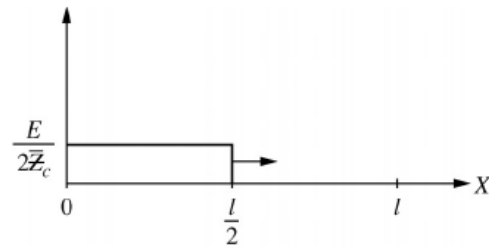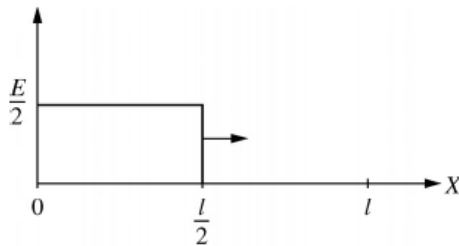
$$i \left(x, \frac{\tau}{2} \right) = \frac{E}{2Z_c} U_{-1} \left(\frac{l-x}{v} \right) - \frac{E}{2Z_c} U_{-1} \left(\frac{x-\frac{3}{2}l}{v} \right)$$




For $t = \tau = \frac{l}{v}$:
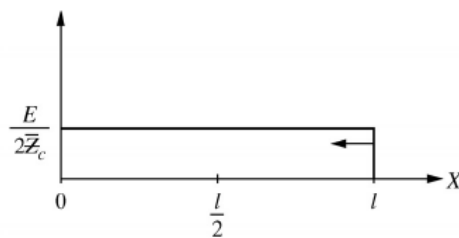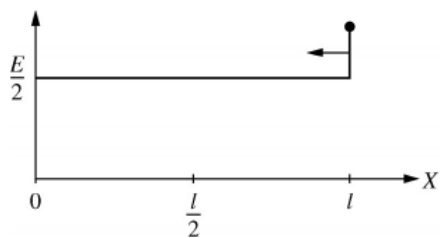
$$V(x,\tau) = \frac{E}{2} U_{-1} \left(\frac{l-x}{v} \right) + \frac{E}{2} U_{-1} \left(\frac{x-l}{v} \right) \quad i(x,\tau) = \frac{E}{2Z_c} U_{-1} \left(\frac{l-x}{v} \right) - \frac{E}{2Z_c} U_{-1} \left(\frac{x-l}{v} \right)$$



For $t = 2\tau = \frac{2l}{w}$:
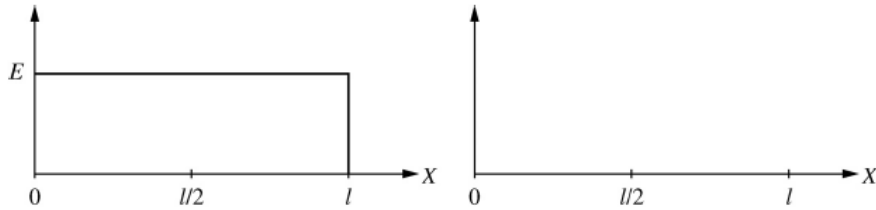
$$V(x, 2\tau) = \frac{E}{2} U_{-1}\left(\frac{2l-x}{v}\right) + \frac{E}{2} U_{-1}\left(\frac{x}{v}\right) \quad i(x, 2\tau) = \frac{E}{2Z_c} U_{-1}\left(\frac{2l-x}{v}\right) - \frac{E}{2Z_c} U_{-1}\left(\frac{x}{v}\right)$$



$$13.5 \quad \Gamma_R = \frac{4-1}{4+1} = 0.6 \quad \Gamma_S = \frac{\frac{1}{3}-1}{\frac{1}{3}+1} = -0.5$$

$$E_G(S) = \frac{E}{S}$$

$$V(x, S) = \frac{E}{S} \left[\frac{1}{\frac{1}{3}+1} \right] \left[\frac{e^{-\frac{Sx}{v}} + 0.6e^{s\left(\frac{x}{v}-2\tau\right)}}{1 - (0.6)(-0.5)e^{-2S\tau}} \right]$$

$$V(x, S) = \frac{3E}{4S} \left[\frac{e^{-\frac{Sx}{v}} + 0.6e^{s\left(\frac{x}{v}-2\tau\right)}}{1 + 0.3e^{-2S\tau}} \right]$$


$$V(x, S) = \frac{3E}{4S} \left[e^{-\frac{Sx}{v}} + 0.6e^{s\left(\frac{x}{v}-2\tau\right)} \right] \left[1 - 0.3e^{-2S\tau} + (0.3)^2 e^{-4S\tau} \dots \right]$$

$$V(x, S) = \frac{3E}{4S} \left[e^{-\frac{Sx}{v}} + 0.6e^{s\left(\frac{x}{v}-2\tau\right)} - 0.3e^{-s\left(\frac{x}{v}+2\tau\right)} - 0.18e^{s\left(\frac{x}{v}-4\tau\right)} \right. \\ \left. + 0.09e^{-s\left(\frac{x}{v}+4\tau\right)} + 0.054e^{s\left(\frac{x}{v}-6\tau\right)} \dots \right]$$


$$V(x,t) = \frac{3E}{4} \left[U_{-1} \left(t - \frac{x}{v} \right) + 0.6U_{-1} \left(t + \frac{x}{v} - 2\tau \right) - 0.3U_{-1} \left(t - \frac{x}{v} - 2\tau \right) - 0.18U_{-1} \left(t + \frac{x}{v} - 4\tau \right) + 0.09U_{-1} \left(t - \frac{x}{v} - 4\tau \right) + 0.054U_{-1} \left(t + \frac{x}{v} - 6\tau \right) \dots \right]$$



At the center of the line, where $x = \frac{l}{2}$:
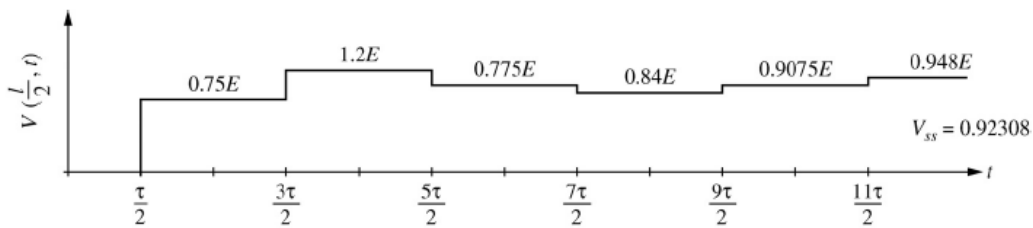
$$V\left(\frac{l}{2}, t\right) = \frac{3E}{4} \left[U_{-1} \left(t - \frac{\tau}{2} \right) + 0.6U_{-1} \left(t - \frac{3\tau}{2} \right) - 0.3U_{-1} \left(t - \frac{5\tau}{2} \right) - 0.18U_{-1} \left(t - \frac{7\tau}{2} \right) + 0.09U_{-1} \left(t - \frac{9\tau}{2} \right) + 0.054U_{-1} \left(t - \frac{11\tau}{2} \right) \dots \right]$$





13.9

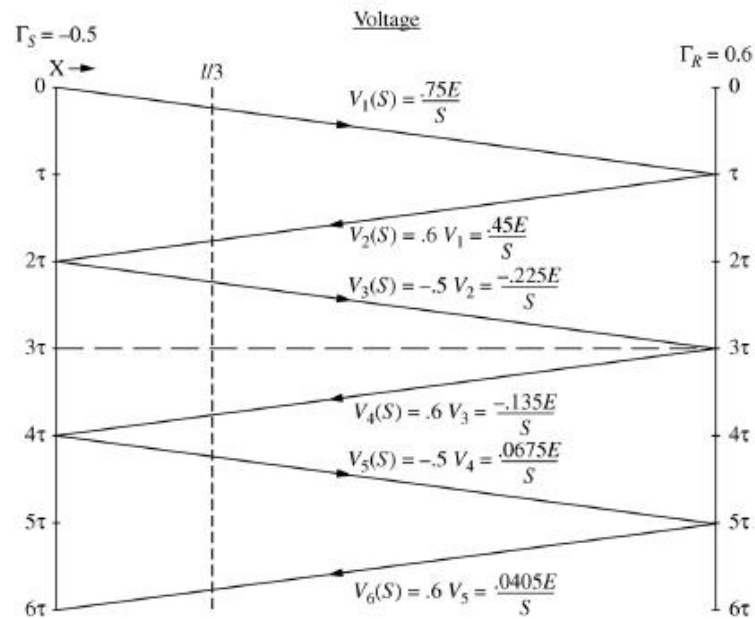

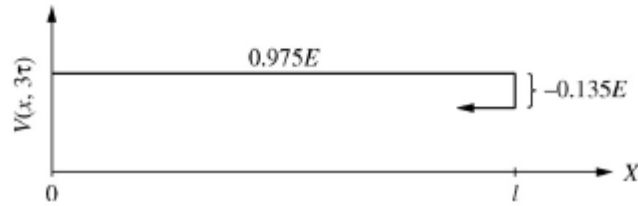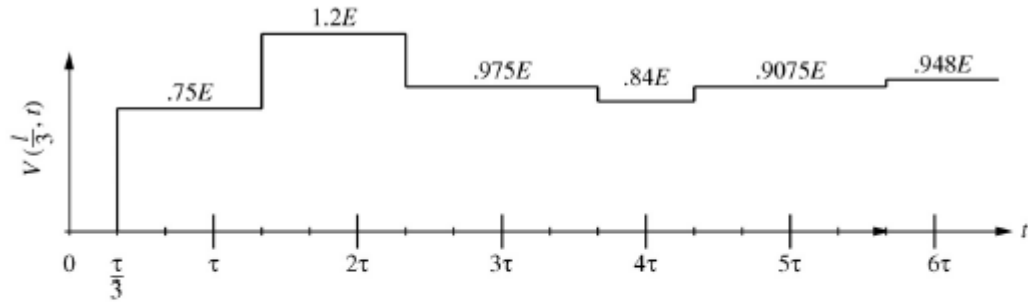

13.11

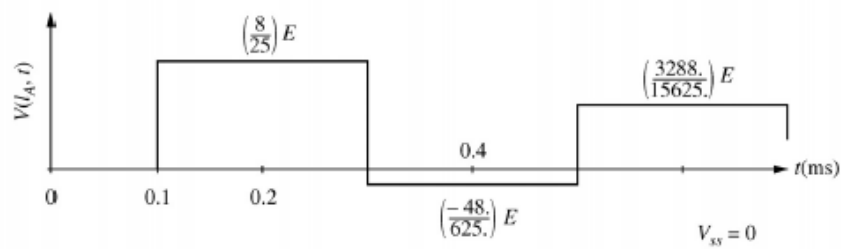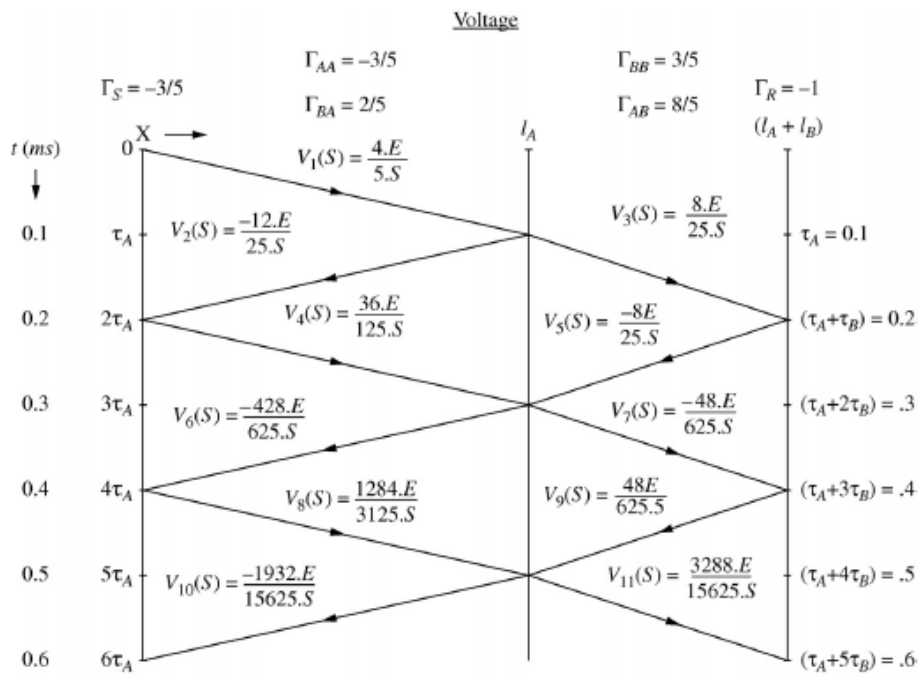

13.14 For a voltage wave V_A^+ arriving at the junction from line A,


$$\text{KVL } V_A^+ + V_A^- = V_B^+ \quad (1)$$

$$V_B^+ = V_C^+ \quad (2)$$

$$V_C^+ = V_D^+ \quad (3)$$

$$\text{KCL } I_A^+ + I_A^- = I_B^+ + I_C^+ + I_D^+ \quad (4)$$
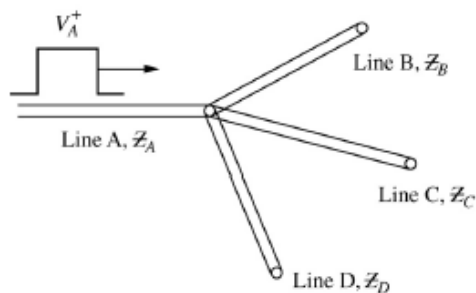
$$\frac{V_A^+}{Z_A} - \frac{V_A^-}{Z_A} = \frac{V_B^+}{Z_B} + \frac{V_C^+}{Z_C} + \frac{V_D^+}{Z_D}$$



Using Eqs (2) and (3) in Eq (4):

$$\frac{V_A^+}{Z_A} - \frac{V_A^-}{Z_A} = V_B^+ \left(\frac{1}{Z_B} + \frac{1}{Z_C} + \frac{1}{Z_D} \right) = \frac{V_B^+}{Z_{eq}} \quad (5)$$

$$\text{Where } Z_{eq} = Z_B // Z_C // Z_D = \frac{1}{\frac{1}{Z_B} + \frac{1}{Z_C} + \frac{1}{Z_D}}$$

Solving Eqs (1) and (5):

$$V_A^- = \left[\frac{\frac{Z_{eq}}{Z_A} - 1}{\left(\frac{Z_{eq}}{Z_A}\right) + 1} \right] V_A^+ = \Gamma_{AA} V_A^+ \quad V_B^+ = \left[\frac{2\left(\frac{Z_{eq}}{Z_A}\right)}{\left(\frac{Z_{eq}}{Z_A}\right) + 1} \right] V_A^+ = \Gamma_{BA} V_A^+$$

$$\text{Also } V_C^+ = \Gamma_{CA} V_A^+ \quad V_D^+ = \Gamma_{DA} V_A^+ \quad \Gamma_{CA} = \Gamma_{DA} = \Gamma_{BA}$$