

KING FAHD UNIVERSITY OF PETROLEUM & MINERALS
ELECTRICAL ENGINEERING DEPARTMENT
EE 306 – Term 192

HW # 3: Single Phase Transformers

Due Date: (UT-Classes, March 1st, 2020; MW-Classes, March 2nd, 2020)

Problem # 1:

- (a) A 480/240V, 4.8kV A, 60Hz, single-phase transformer is used to supply a 4.8kV A load with a 0.8 lagging power factor, at rated voltage (240V)
- (b) If the transformer were ideal, what would be the magnitude of the current on the primary (480V) side?
- (c) What is the impedance of the load under the ideal assumption?
- (d) Again, if the transformer is ideal, what would the impedance be as viewed from the primary side?

Problem # 2:

A 15-kVA 8000/230-V distribution transformer has an impedance referred to the primary of $80 + j300\Omega$. The components of the excitation branch referred to the primary side are $R_C = 350\text{ k}\Omega$ and $X_M = 70\text{ k}\Omega$.

- (a) If the primary voltage is 7967 V and the load impedance is $Z_L = 3.0 + j1.5\ \Omega$, what is the secondary voltage of the transformer? What is the voltage regulation of the transformer?
- (b) If the load is disconnected and a capacitor of $-j4.0\ \Omega$ is connected in its place, what is the secondary voltage of the transformer? What is its voltage regulation under these conditions?

Problem # 3:

A 250 kVA, 3600/240 V, single-phase transformer has the following test data:

	Voltage (V)	Current (A)	Power (W)
O/C Test	240	57.85	4985
S/C Test	187	69.45	4823

Find:

- (a) The approximate equivalent circuit referred to HV and LV side.
- (b) The voltage regulation and efficiency when the load takes 1100 A at 220 V and 0.6 lag pf. (NOTE: this is not rated load).
- (c) The voltage regulation and efficiency at rated load conditions and 0.8 lag pf.

Problem # 4:

A 1 ϕ , 25 kVA, 2300=230 V transformer has the following parameters:

$$Z_{eq,H} = 4.0 + j5.0 \ \Omega$$

$$R_{c,L} = 450 \ \Omega$$

$$X_{m,L} = 300 \ \Omega$$

- (a) The transformer is connected to a load whose power factor varies. Determine the worst-case voltage regulation for full-load output, and draw the phasor diagram of this case.
- (b) Determine efficiency when the transformer delivers full load at rated voltage and 0.85 power factor lagging.
- (c) Determine the percentage loading of the transformer at which the efficiency is a maximum and calculate this efficiency if the power factor is 0.85 and load voltage is 230 V.