

KING FAHD UNIVERSITY OF PETROLEUM & MINERALS
ELECTRICAL ENGINEERING DEPARTMENT

EE 306 – Term 192

HW # 4: DC Machines

Due Date: (UT-Classes, March 22, 2020; MW-Classes, March 23, 2020)

Problem # 1:

A 220 V shunt motor has armature and field resistance of 0.2 Ω and 220 Ω respectively. The motor is running at 1000 rpm and drawing 10 A current from the supply to drive a constant load torque. Calculate the new speed and armature current if an external armature resistance of value 5 Ω is placed in the armature circuit. Neglect armature reaction and saturation.

For initial operating point: $I_{L1} = 10$ A, $r_a = 0.2$ Ω and supply voltage $V = 220$ V.

$$\begin{aligned}\text{Field current } I_{f1} &= 220/220 \text{ A} = 1\text{A} \\ \text{Armature current } I_{a1} &= 10\text{A} - 1\text{A} = 9\text{A}\end{aligned}$$

Now we write down the expressions for the torque and back emf.

$$\begin{aligned}T_{e1} = k_t I_{f1} I_{a1} &= k_t \times 1 \times 9 = T_L \\ E_{b1} = k_g I_{f1} n &= k_g \times 1 \times 1000 = V - I_{a1} r_a = 220 - 9 \times 0.2 = 218.2\text{V} \\ k_g \times 1 \times 1000 &= 218.2\text{V}\end{aligned}$$

Since field resistance remains unchanged $I_{f2} = I_{f1} = 1$ A. Let the new steady armature current be I_{a2} and the new speed be n_2 . In this new condition the torque and back emf equations are

$$\begin{aligned}T_{e2} &= k_t \times 1 \times I_{a2} = T_L \\ E_{b2} &= k_g \times 1 \times n_2 \\ &= V - I_{a2}(r_a + R_{ext}) \\ \therefore k_g \times 1 \times n_2 &= 220 - I_{a2} \times 5.2 \text{ V}\end{aligned}$$

Taking the ratios of T_{e2} and T_{e1} we get,

$$\begin{aligned}\frac{T_{e2}}{T_{e1}} &= \frac{k_t \times 1 \times I_{a2}}{k_t \times 1 \times 9} \\ \text{Thus, } I_{a2} &= 9 \text{ A}\end{aligned}$$

Now taking the ratio emfs $\frac{E_{b2}}{E_{b1}}$, we get,

$$\frac{k_g \times 1 \times n_2}{k_g \times 1 \times 1000} = \frac{220 - I_{a2} \times 5.2}{218}$$

$$\frac{n_2}{1000} = \frac{220 - 9 \times 5.2}{218.2}$$

$$\text{or, } \frac{n_2}{1000} = \frac{173.2}{218.2}$$

$$\text{or, } n_2 = \frac{173.2 \times 1000}{218.2}$$

$$\therefore n_2 = 793.76 \text{ rpm}$$

Problem # 2:

Separately excited dc generator is rated for a load voltage of 150 V for a full load current of 20 A at 1500 rpm. With the load disconnected, the output voltage is 160 V.

a. Determine the voltage regulation, the load resistance, the armature resistance, and the developed torque at full load.

b. The speed of the generator is decreased to 1200 rpm, and the load resistance is unchanged. Determine the load current, the load voltage, and the developed power.

$$(a) \text{ voltage regulation} = \frac{V_{NL} - V_{FL}}{V_{FL}} \times 100\% = \frac{160 - 150}{150} \times 100\% = 6.667\%$$

$$R_L = \frac{V_L}{I_L} = \frac{150}{20} = 7.5 \Omega \quad R_A = \frac{V_{NL} - V_{FL}}{I_{FL}} = \frac{160 - 150}{20} = 0.5 \Omega$$

$$\omega_m = n_m \frac{2\pi}{60} = 157.1 \text{ rad/s} \quad T_{dev} = \frac{P_{dev}}{\omega_m} = \frac{E_A I_A}{\omega_m} = \frac{160 \times 20}{157.1} = 20.37 \text{ Nm}$$

(b)

$$V_{NL} = E_A = 160 \frac{1200}{1500} = 128 \text{ V} \quad I_L = \frac{E_A}{R_A + R_L} = \frac{128}{0.5 + 7.5} = 16 \text{ A}$$

$$V_L = R_L I_L = 120 \text{ V}$$

$$P_{dev} = E_A I_A = 2048 \text{ W}$$

Problem # 3:

A shunt-connected 5-hp dc motor is rated for operation at $V_T=200$ V, $I_L=23.3$ A, and $n_m=1500$ rpm. Furthermore, $I_F=$ and $R_A=0.4$ Ω . Under rated conditions find:

- A. the input power;
- B. the power supplied to the field circuit;
- C. the power lost in the armature resistance;
- D. the rotational loss;
- E. the efficiency

$$(a) \quad P_{in} = V_T I_L = 4660 \text{ W}$$

$$(b) \quad P_F = V_T I_F = 300 \text{ W}$$

$$(c) \quad I_A = I_L - I_F = 21.8 \text{ A}$$

$$P_{R_A} = R_A I_A^2 = 190.1 \text{ W}$$

$$(d) \quad P_{rot} = P_{in} - P_F - P_{R_A} - P_{out}$$
$$= 440 \text{ W}$$

$$(e) \quad \eta = \frac{P_{out}}{P_{in}} \times 100\% = 80.0\%$$

Problem # 4:

A 240V series motor. The armature resistance is 0.42Ω and a series field resistance is 0.18Ω . The speed is 500rev/min when the current is 36A. What is the motor speed when the load reduces the line current to 21A. Assume 3V brush drop and the flux is proportional to the current.

$$500 = \frac{240 - 3 - 36(0.6)}{K_a \phi} \Rightarrow K_a \phi = 0.431$$
$$n = \frac{240 - 3 - 21(0.6)}{\left(\frac{21}{36}\right)(0.431)} = 893 \text{ rpm}$$

Problem # 5:

A long-shunt DC generator running at 1000 rpm supplies 22 kW at a terminal voltage of 220 V. The armature, shunt, and series resistances are 0.05, 110, and 0.06Ω respectively. The efficiency of the generator is 88%. Find: -

- (a) Copper loss
- (b) Rotational loss
- (c) Input torque

Solution

$$I_L = \frac{22000}{220} = 100 \text{ A}$$

$$I_{sh} = \frac{220}{110} = 2 \text{ A}$$

$$I_a = 102 \text{ A}$$

$$\textcircled{a} P_{cu} = I_a^2(R_a + R_s) + I_{sh}^2 R_{sh} = 1584.5 \text{ W}$$

$$\textcircled{b} \eta = \frac{P_{o/p}}{P_{o/p} + P_{rot} + P_{cu}} \quad 0.88 = \frac{22000}{22000 + P_{rot} + 1584.5}$$

$$P_{rot} = 1415.5 \text{ W}$$

$$\textcircled{c} P_{i/p} = \frac{P_{o/p}}{\eta} = 25000 \text{ W} = T\omega$$

$$25000 = T * \frac{2\pi * 1000}{60}$$

