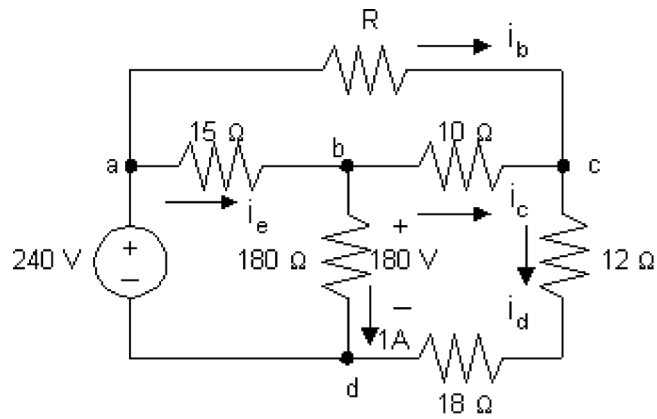


P 2.24



$$v_{ab} = 240 - 180 = 60 \text{ V}; \quad \text{therefore, } i_e = 60/15 = 4 \text{ A}$$

$$i_c = i_e - 1 = 4 - 1 = 3 \text{ A}; \quad \text{therefore, } v_{bc} = 10i_c = 30 \text{ V}$$

$$v_{cd} = 180 - v_{bc} = 180 - 30 = 150 \text{ V};$$

$$\text{therefore, } i_d = v_{cd}/(12 + 18) = 150/30 = 5 \text{ A}$$

$$i_b = i_d - i_c = 5 - 3 = 2 \text{ A}$$

$$v_{ac} = v_{ab} + v_{bc} = 60 + 30 = 90 \text{ V}$$

$$R = v_{ac}/i_b = 90/2 = 45 \Omega$$


$$\text{CHECK: } i_g = i_b + i_e = 2 + 4 = 6 \text{ A}$$

$$p_{\text{dev}} = (240)(6) = 1440 \text{ W}$$

$$\sum P_{\text{dis}} = 1(180) + 4(45) + 9(10) + 25(12) + 25(18) + 16(15) = 1440 \text{ W (CHECKS)}$$

P 2.28 [a] $i_o = 0$ because no current can exist in a single conductor connecting two parts of a circuit.

[b]

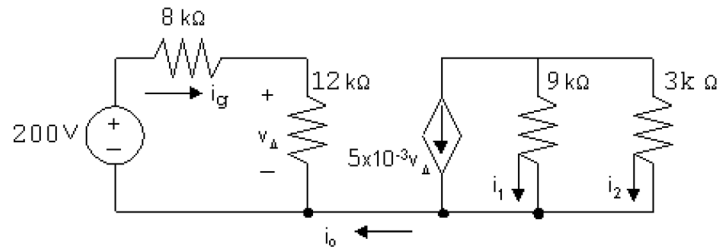

$$-200 + 8000i_g + 12,000i_g = 0 \quad \text{so} \quad i_g = 200/20,000 = 10 \text{ mA}$$

$$v_{\Delta} = (12 \times 10^3)(10 \times 10^{-3}) = 120 \text{ V}$$

$$5 \times 10^{-3}v_{\Delta} = 0.6 \text{ A}$$

$$9000i_1 = 3000i_2 \quad \text{so} \quad i_2 = 3i_1$$

$$0.6 + i_1 + i_2 = 0 \quad \text{so} \quad 0.6 + i_1 + 3i_1 = 0 \quad \text{thus} \quad i_1 = -0.15 \text{ A}$$

[c] $i_2 = 3i_1 = -0.45 \text{ A}$

P 2.26 [a] Start with the $22.5\ \Omega$ resistor. Since the voltage drop across this resistor is $90\ \text{V}$, we can use Ohm's law to calculate the current:

$$i_{22.5\ \Omega} = \frac{90\ \text{V}}{22.5\ \Omega} = 4\ \text{A}$$

Next we can calculate the voltage drop across the $15\ \Omega$ resistor by writing a KVL equation around the outer loop of the circuit:

$$-240\ \text{V} + 90\ \text{V} + v_{15\ \Omega} = 0 \quad \text{so} \quad v_{15\ \Omega} = 240 - 90 = 150\ \text{V}$$

Now that we know the voltage drop across the $15\ \Omega$ resistor, we can use Ohm's law to find the current in this resistor:

$$i_{15\ \Omega} = \frac{150\ \text{V}}{15\ \Omega} = 10\ \text{A}$$

Write a KCL equation at the middle right node to find the current through the $5\ \Omega$ resistor. Sum the currents entering:

$$4\ \text{A} - 10\ \text{A} + i_{5\ \Omega} = 0 \quad \text{so} \quad i_{5\ \Omega} = 10\ \text{A} - 4\ \text{A} = 6\ \text{A}$$

Write a KVL equation clockwise around the upper right loop, starting below the $4\ \Omega$ resistor. Use Ohm's law to express the voltage drop across the resistors in terms of the current through the resistors:

$$-v_{4\ \Omega} + 90\ \text{V} + (5\ \Omega)(-6\ \text{A}) = 0 \quad \text{so} \quad v_{4\ \Omega} = 90\ \text{V} - 30\ \text{V} = 60\ \text{V}$$

Using Ohm's law we can find the current through the $4\ \Omega$ resistor:

$$i_{4\ \Omega} = \frac{60\ \text{V}}{4\ \Omega} = 15\ \text{A}$$


Write a KCL equation at the middle node. Sum the currents entering:

$$15\ \text{A} - 6\ \text{A} - i_{20\ \Omega} = 0 \quad \text{so} \quad i_{20\ \Omega} = 15\ \text{A} - 6\ \text{A} = 9\ \text{A}$$

Use Ohm's law to calculate the voltage drop across the $20\ \Omega$ resistor:

$$v_{20\ \Omega} = (20\ \Omega)(9\ \text{A}) = 180\ \text{V}$$

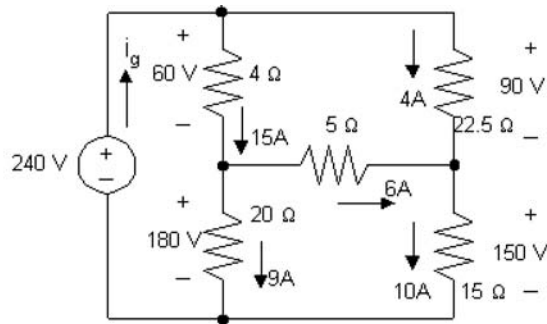All of the voltages and currents calculated above are shown in the figure below:



Calculate the power dissipated by the resistors using the equation $p_R = Ri_R^2$:

$$p_{4\Omega} = (4)(15)^2 = 900 \text{ W} \quad p_{20\Omega} = (20)(9)^2 = 1620 \text{ W}$$

$$p_{5\Omega} = (5)(6)^2 = 180 \text{ W} \quad p_{22.5\Omega} = (22.5)(4)^2 = 360 \text{ W}$$

$$p_{15\Omega} = (15)(10)^2 = 1500 \text{ W}$$

[b] We can calculate the current in the voltage source, i_g by writing a KCL equation at the top middle node:

$$i_g = 15 \text{ A} + 4 \text{ A} = 19 \text{ A}$$

Now that we have both the voltage and the current for the source, we can calculate the power supplied by the source:

$$p_g = -240(19) = -4560 \text{ W} \quad \text{thus} \quad p_g \text{ (supplied)} = 4560 \text{ W}$$

[c] $\sum P_{\text{dis}} = 900 + 1620 + 180 + 360 + 1500 = 4560 \text{ W}$


Therefore,

$$\sum P_{\text{supp}} = \sum P_{\text{dis}}$$

P 2.29 First note that we know the current through all elements in the circuit except the $200\ \Omega$ resistor (the current in the three elements to the left of the $200\ \Omega$ resistor is i_β ; the current in the three elements to the right of the $200\ \Omega$ resistor is $49i_\beta$). To find the current in the $200\ \Omega$ resistor, write a KCL equation at the top node:

$$i_\beta + 49i_\beta = i_{200\ \Omega} = 50i_\beta$$

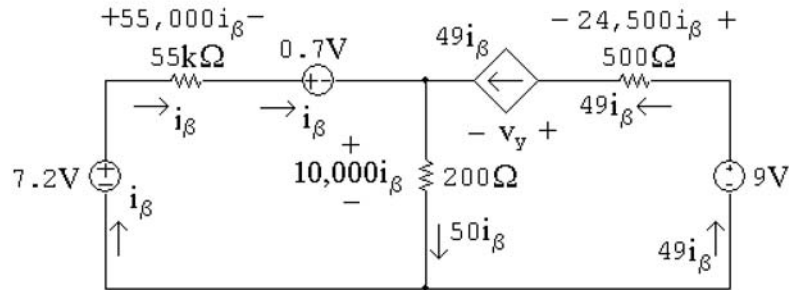We can then use Ohm's law to find the voltages across each resistor in terms of i_β . The results are shown in the figure below:



[a] To find i_β , write a KVL equation around the left-hand loop, summing voltages in a clockwise direction starting below the 7.2V source:

$$-7.2\text{ V} + 55,000i_\beta + 0.7\text{ V} + 10,000i_\beta = 0$$

Solving for i_β

$$55,000i_\beta + 10,000i_\beta = 6.5\text{ V} \quad \text{so} \quad 65,000i_\beta = 6.5\text{ V}$$

Thus,

$$i_\beta = \frac{6.5}{65,000} = 100\ \mu\text{A}$$

Now that we have the value of i_β , we can calculate the voltage for each component except the dependent source. Then we can write a KVL equation for the right-hand loop to find the voltage v_y of the dependent source. Sum the voltages in the clockwise direction, starting to the left of the dependent source:

$$-v_y - 24,500i_\beta + 9\text{ V} - 10,000i_\beta = 0$$

Thus,

$$v_y = 9\text{ V} - 34,500i_\beta = 9\text{ V} - 34,500(100 \times 10^{-6}) = 9\text{ V} - 3.45\text{ V} = 5.55\text{ V}$$

[b] We now know the values of voltage and current for every circuit element. Let's construct a power table:

Element	Current (μA)	Voltage (V)	Power Equation	Power (μW)
7.2 V	100	7.2	$p = -vi$	-720
55 k Ω	100	5.5	$p = Ri^2$	550
0.7 V	100	0.7	$p = vi$	70
200 Ω	5000	1	$p = Ri^2$	5000
Dep. source	4900	5.55	$p = vi$	27,195
500 Ω	4900	2.45	$p = Ri^2$	12,005
9 V	4900	9	$p = -vi$	-44,100

The total power generated in the circuit is the sum of the negative power values in the power table:

$$-720 \mu\text{W} + -44,100 \mu\text{W} = -44,820 \mu\text{W}$$

Thus, the total power generated in the circuit is 44,820 μW . The total power absorbed in the circuit is the sum of the positive power values in the power table:

$$550 \mu\text{W} + 70 \mu\text{W} + 5000 \mu\text{W} + 27,195 \mu\text{W} + 12,005 \mu\text{W} = 44,820 \mu\text{W}$$

Thus, the total power absorbed in the circuit is 44,820 μW and the power in the circuit balances.