

$$\text{P 3.26} \quad i_{300\Omega} = \frac{1000 + 200}{1000 + 200 + 300 + 300} (15 \times 10^{-3}) = 10 \text{ mA}$$

$$v_{300\Omega} = (300)(10 \times 10^{-3}) = 3 \text{ V}$$

$$i_{200\Omega} = i_{1 \text{ k}\Omega} = 15 \times 10^{-3} - i_{300\Omega} = 5 \text{ mA}$$

$$v_{1\text{k}} = (1000)(5 \times 10^{-3}) = 5 \text{ V}$$

$$v_o = 3 - 5 = -2 \text{ V}$$

$$\text{P 3.24 [a]} \quad v_{20k} = \frac{20}{20+5}(45) = 36 \text{ V}$$

$$v_{90k} = \frac{90}{90+60}(45) = 27 \text{ V}$$

$$v_x = v_{20k} - v_{90k} = 36 - 27 = 9 \text{ V}$$

$$\text{[b]} \quad v_{20k} = \frac{20}{25}(V_s) = 0.8V_s$$

$$v_{90k} = \frac{90}{150}(V_s) = 0.6V_s$$

$$v_x = 0.8V_s - 0.6V_s = 0.2V_s$$

$$\text{P 3.56} \quad 18 + 2 = 20 \Omega$$

$$20 \parallel 80 = 16 \Omega$$

$$16 + 4 = 20 \Omega$$

$$20 \parallel 30 = 12 \Omega$$

$$12 + 8 = 20 \Omega$$

$$20 \parallel 60 = 15 \Omega$$

$$15 + 5 = 20 \Omega$$


$$i_g = \frac{240 \text{ V}}{20 \Omega} = 12 \text{ A}$$

$$i_o = \frac{60}{60 + 20}(12 \text{ A}) = 9 \text{ A}$$

$$i_{30\Omega} = \frac{20}{20 + 30}(9 \text{ A}) = 3.6 \text{ A}$$

$$p_{30\Omega} = (30)(3.6)^2 = 388.8 \text{ W}$$

P 4.21

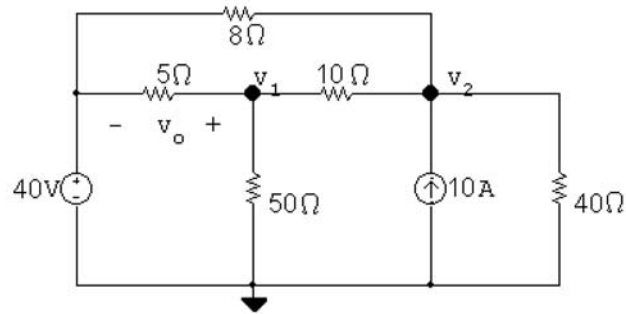

The two node voltage equations are:

$$\frac{v_1 - 40}{5} + \frac{v_1}{50} + \frac{v_1 - v_2}{10} = 0$$

$$\frac{v_2 - v_1}{10} - 10 + \frac{v_2}{40} + \frac{v_2 - 40}{8} = 0$$

Place these equations in standard form:

$$v_1 \left(\frac{1}{5} + \frac{1}{50} + \frac{1}{10} \right) + v_2 \left(-\frac{1}{10} \right) = \frac{40}{5}$$

$$v_1 \left(-\frac{1}{10} \right) + v_2 \left(\frac{1}{10} + \frac{1}{40} + \frac{1}{8} \right) = 10 + \frac{40}{8}$$

Solving, $v_1 = 50 \text{ V}$; $v_2 = 80 \text{ V}$.

Thus, $v_o = v_1 - 40 = 50 - 40 = 10 \text{ V}$.

POWER CHECK:

$$i_g = (50 - 40)/5 + (80 - 40)/8 = 7 \text{ A}$$

$$p_{40\text{V}} = (40)(7) = 280 \text{ W (abs)}$$

$$p_{5\Omega} = (50 - 40)^2/5 = 20 \text{ W (abs)}$$

$$p_{8\Omega} = (80 - 40)^2/8 = 200 \text{ W (abs)}$$

$$p_{10\Omega} = (80 - 50)^2/10 = 90 \text{ W (abs)}$$


$$p_{50\Omega} = 50^2/50 = 50 \text{ W (abs)}$$

$$p_{40\Omega} = 80^2/40 = 160 \text{ W (abs)}$$

$$p_{10\text{A}} = -(80)(10) = -800 \text{ W (del)}$$

$$\sum p_{\text{abs}} = 280 + 20 + 200 + 90 + 50 + 160 = 800 \text{ W} = \sum p_{\text{del}}$$

P 4.19

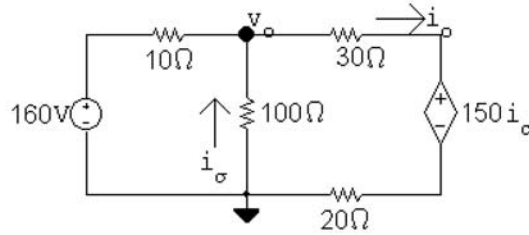

The node voltage equation is

$$\frac{v_o - 160}{10} + \frac{v_o}{100} + \frac{v_o - 150i_\sigma}{30 + 20} = 0$$

The dependent source constraint equation is:

$$i_\sigma = -\frac{v_o}{100}$$

Place these equations in standard form:

$$v_o \left(\frac{1}{10} + \frac{1}{100} + \frac{1}{50} \right) + i_\sigma \left(-\frac{150}{50} \right) = \frac{160}{10}$$

$$v_o \left(\frac{1}{100} \right) + i_\sigma(1) = 0$$

Solving, $v_o = 100 \text{ V}$; $i_\sigma = -1 \text{ A}$


Now find the power:

$$i_o = \frac{160 - 100}{10} - 1 = 5 \text{ A}$$

$$p_{ds} = [150(-1)](5) = -750 \text{ W.}$$

Thus, the dependent source delivers 750 W

P 4.27

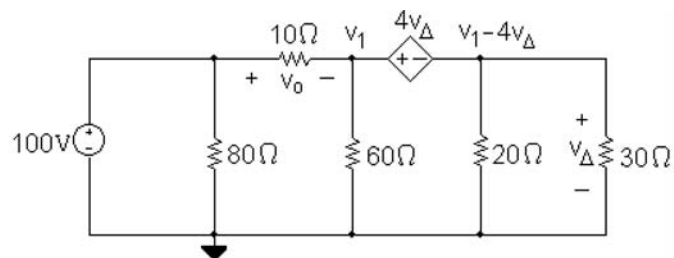

The supernode equation is:

$$\frac{v_1 - 100}{10} + \frac{v_1}{60} + \frac{v_1 - 4v_\Delta}{20} + \frac{v_1 - 4v_\Delta}{30} = 0$$

The constraint equation for the dependent source is:

$$4v_\Delta = v_1 - v_\Delta$$

Place these equations in standard form:

$$v_1 \left(\frac{1}{10} + \frac{1}{60} + \frac{1}{20} + \frac{1}{30} \right) + v_\Delta \left(-\frac{4}{20} - \frac{4}{30} \right) = \frac{100}{10}$$

$$v_1(1) + v_\Delta(-5) = 0$$

Solving, $v_1 = 75 \text{ V}$; $v_\Delta = 15 \text{ V}$

Thus, $v_o = 100 - v_1 = 25 \text{ V}$