

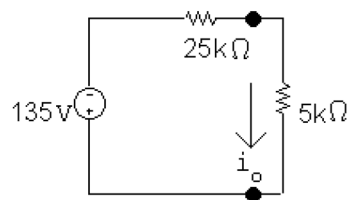
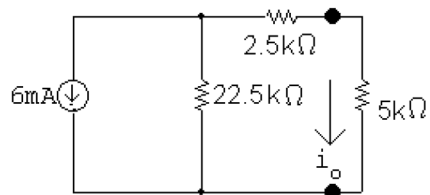
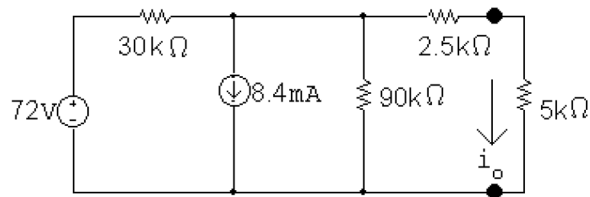
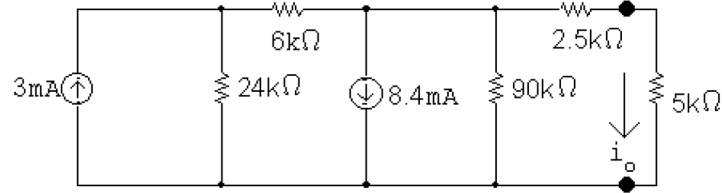


P 4.56 [a]

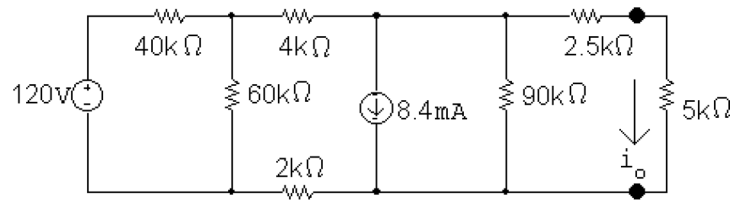

$$i_o = -135/30,000 = -4.5 \text{ mA}$$

[b]

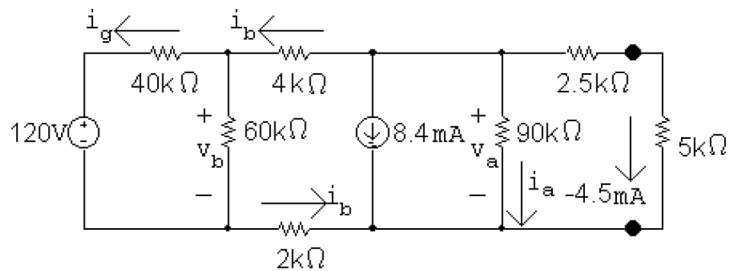

$$v_a = (7500)(-0.0045) = -33.75 \text{ V}$$

$$i_a = \frac{v_a}{90,000} = \frac{-33.75}{90,000} = -0.375 \text{ mA}$$

$$i_b = -8.4 \times 10^{-3} + 0.375 \times 10^{-3} + 4.5 \times 10^{-3} = -3.525 \text{ mA}$$

$$v_b = (6000)(3.525 \times 10^{-3}) - 33.75 = -12.6 \text{ V}$$

$$i_g = \frac{-12.6 - 120}{40,000} = -3.315 \text{ mA}$$

$$p_{120V} = (120)(-3.315 \times 10^{-3}) = -397.8 \text{ mW}$$


Check:

$$p_{8.4mA} = (-33.75)(8.4 \times 10^{-3}) = -283.5 \text{ mW}$$


$$\sum P_{\text{dev}} = 397.8 + 283.5 = 681.3 \text{ mW}$$

$$\begin{aligned} \sum P_{\text{dis}} &= (40,000)(-3.315 \times 10^{-3})^2 + \frac{(-12.6)^2}{60,000} + \frac{(-33.75)^2}{90,000} \\ &\quad + (6000)(-3.525 \times 10^{-3})^2 + (7500)(-4.5 \times 10^{-3})^2 \\ &= 681.3 \text{ mW} \end{aligned}$$

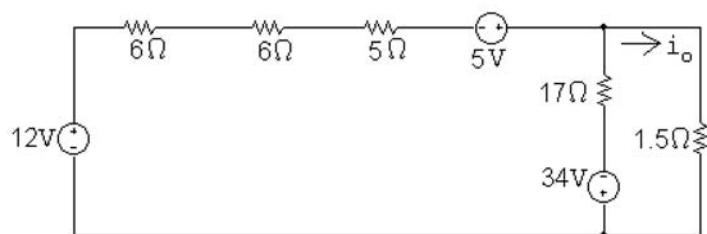
P 4.58 [a] Applying a source transformation to each current source yields



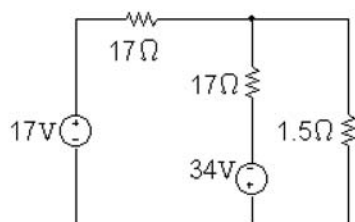
Now combine the 12 V and 5 V sources into a single voltage source and the 6 Ω, 6 Ω and 5 Ω resistors into a single resistor to get



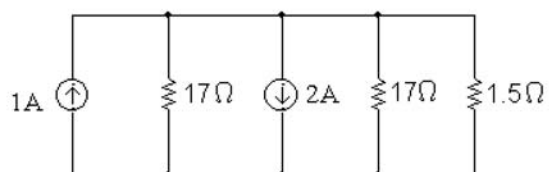Now use a source transformation on each voltage source, thus




which can be reduced to

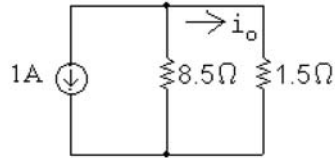

$$\therefore i_o = \frac{8.5}{10}(-1) = -0.85 \text{ A}$$

[b]

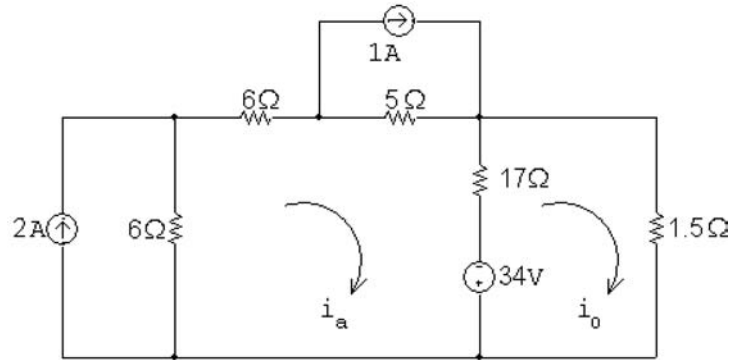

The mesh current equations are:

$$6(i_a - 2) + 6i_a + 5(i_a - 1) + 17(i_a - i_o) - 34 = 0$$

$$1.5i_o + 34 + 17(i_o - i_a) = 0$$

Put these equations in standard form:

$$i_a(6 + 6 + 5 + 17) + i_o(-17) = 12 + 5 + 34$$

$$i_a(-17) + i_o(1.5 + 17) = -34$$

Solving, $i_a = 1.075 \text{ A}; \quad i_o = -0.85 \text{ A}$