

AP 5.2 From Assessment Problem 5.1

$$\begin{aligned}v_o &= (-R_f/R_i)v_s = (-R_x/16,000)v_s \\ &= (-R_x/16,000)(-0.640) = 0.64R_x/16,000 = 4 \times 10^{-5} R_x\end{aligned}$$

Use the negative power supply value to determine one limit on the value of  $R_x$ :

$$4 \times 10^{-5} R_x = -15 \quad \text{so} \quad R_x = -15/4 \times 10^{-5} = -375 \text{ k}\Omega$$

Since we cannot have negative resistor values, the lower limit for  $R_x$  is 0. Now use the positive power supply value to determine the upper limit on the value of  $R_x$ :

$$4 \times 10^{-5} R_x = 10 \quad \text{so} \quad R_x = 10/4 \times 10^{-5} = 250 \text{ k}\Omega$$

Therefore,

$$0 \leq R_x \leq 250 \text{ k}\Omega$$

AP 5.4 [a] Write a node voltage equation at  $v_n$ ; remember that for an ideal op amp, the current into the op amp at the inputs is zero:

$$\frac{v_n}{4500} + \frac{v_n - v_o}{63,000} = 0$$

Solve for  $v_o$  in terms of  $v_n$  by multiplying both sides by 63,000 and collecting terms:

$$14v_n + v_n - v_o = 0 \quad \text{so} \quad v_o = 15v_n$$

Now use voltage division to calculate  $v_p$ . We can use voltage division because the op amp is ideal, so no current flows into the non-inverting input terminal and the 400 mV divides between the 15 k $\Omega$  resistor and the  $R_x$  resistor:

$$v_p = \frac{R_x}{15,000 + R_x}(0.400)$$

Now substitute the value  $R_x = 60 \text{ k}\Omega$ :

$$v_p = \frac{60,000}{15,000 + 60,000}(0.400) = 0.32 \text{ V}$$

Finally, remember that for an ideal op amp,  $v_n = v_p$ , so substitute the value of  $v_p$  into the equation for  $v_o$

$$v_o = 15v_n = 15v_p = 15(0.32) = 4.8 \text{ V}$$

[b] Substitute the expression for  $v_p$  into the equation for  $v_o$  and set the resulting equation equal to the positive power supply value:

$$v_o = 15 \left( \frac{0.4R_x}{15,000 + R_x} \right) = 5$$

$$15(0.4R_x) = 5(15,000 + R_x) \quad \text{so} \quad R_x = 75 \text{ k}\Omega$$

AP 5.5 **[a]** Since this is a difference amplifier, we can use the expression for the output voltage in terms of the input voltages and the resistor values given in Eq. 5.22:

$$v_o = \frac{20(60)}{10(24)}v_b - \frac{50}{10}v_a$$

Simplify this expression and substitute in the value for  $v_b$ :

$$v_o = 5(v_b - v_a) = 20 - 5v_a$$

Set this expression for  $v_o$  to the positive power supply value:

$$20 - 5v_a = 10 \text{ V} \quad \text{so} \quad v_a = 2 \text{ V}$$

Now set the expression for  $v_o$  to the negative power supply value:

$$20 - 5v_a = -10 \text{ V} \quad \text{so} \quad v_a = 6 \text{ V}$$

Therefore  $2 \leq v_a \leq 6 \text{ V}$

**[b]** Begin as before by substituting the appropriate values into Eq. 5.22:

$$v_o = \frac{8(60)}{10(12)}v_b - 5v_a = 4v_b - 5v_a$$

Now substitute the value for  $v_b$ :

$$v_o = 4(4) - 5v_a = 16 - 5v_a$$

Set this expression for  $v_o$  to the positive power supply value:

$$16 - 5v_a = 10 \text{ V} \quad \text{so} \quad v_a = 1.2 \text{ V}$$

Now set the expression for  $v_o$  to the negative power supply value:

$$16 - 5v_a = -10 \text{ V} \quad \text{so} \quad v_a = 5.2 \text{ V}$$

Therefore  $1.2 \leq v_a \leq 5.2 \text{ V}$

P 5.7 [a] The circuit shown is a non-inverting amplifier.

[b] We assume the op amp to be ideal, so  $v_n = v_p = 3\text{V}$ . Write a KCL equation at  $v_n$ :

$$\frac{3}{40,000} + \frac{3 - v_o}{80,000} = 0$$

Solving,

$$v_o = 9 \text{ V.}$$

P 5.16 [a] This circuit is an example of an inverting summing amplifier.

$$\text{[b]} \quad v_o = -\frac{220}{33}v_a - \frac{220}{22}v_b - \frac{220}{80}v_c = -8 + 15 - 11 = -4 \text{ V}$$

$$\text{[c]} \quad v_o = -19 - 10v_b = \pm 6$$

$$\therefore v_b = -1.3 \text{ V} \quad \text{when} \quad v_o = -6 \text{ V};$$

$$v_b = -2.5 \text{ V} \quad \text{when} \quad v_o = 6 \text{ V}$$

$$\therefore -2.5 \text{ V} \leq v_b \leq -1.3 \text{ V}$$

P 5.20 [a]  $v_p = v_s$ ,  $v_n = \frac{R_1 v_o}{R_1 + R_2}$ ,  $v_n = v_p$

Therefore  $v_o = \left( \frac{R_1 + R_2}{R_1} \right) v_s = \left( 1 + \frac{R_2}{R_1} \right) v_s$

[b]  $v_o = v_s$

[c] Because  $v_o = v_s$ , thus the output voltage follows the signal voltage.