

P 6.3 Note – the initial current should be 1 A.

$$0 \leq t \leq 2 \text{ s}$$

$$i_L = \frac{1}{2.5 \times 10^{-4}} \int_0^t 3 \times 10^{-3} e^{-4x} dx + 0 = 1.2 \frac{e^{-4x}}{-4} \Big|_0^t + 0$$



$$= 0.3 - 0.3e^{-4t} \text{ A}, \quad 0 \leq t \leq 2 \text{ s}$$

$$i_L(2) = 0.3 \text{ A}$$

$$2 \text{ s} < t < \infty$$

$$i_L = -1.2 \left(\frac{e^{-4(x-2)}}{-4} \Big|_2^t + 0.3 \right)$$
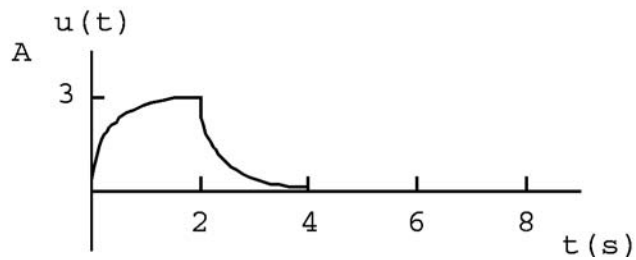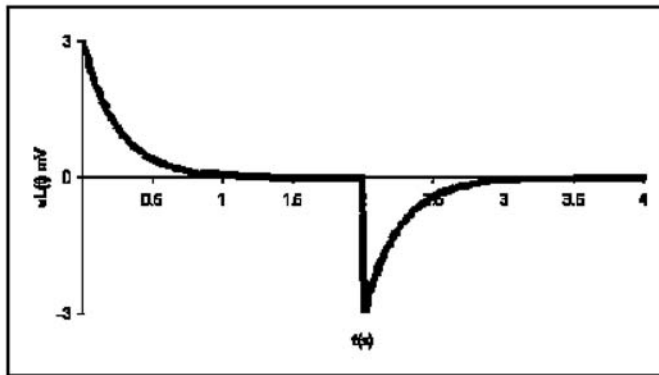
$$= 0.3e^{-4(t-2)} \text{ A}, \quad 2 \text{ s} \leq t < \infty$$



P 6.4 [a] $v = L \frac{di}{dt}$

$$\frac{di}{dt} = 18[t(-10e^{-10t}) + e^{-10t}] = 18e^{-10t}(1 - 10t)$$

$$v = (50 \times 10^{-6})(18)e^{-10t}(1 - 10t) \\ = 0.9e^{-10t}(1 - 10t) \text{ mV}, \quad t > 0$$

[b] $p = vi$

$$v(200 \text{ ms}) = 0.9e^{-2}(1 - 2) = -121.8 \mu\text{V}$$

$$i(200 \text{ ms}) = 18(0.2)e^{-2} = 487.2 \text{ mA}$$

$$p(200 \text{ ms}) = (-121.8 \times 10^{-6})(487.2 \times 10^{-3}) = -59.34 \mu\text{W}$$

[c] delivering

[d] $w = \frac{1}{2}Li^2 = \frac{1}{2}(50 \times 10^{-6})(487.2 \times 10^{-3})^2 = 5.93 \mu\text{J}$

[e] The energy is a maximum where the current is a maximum:

$$\frac{di_L}{dt} = 18[t(-10)e^{-10t} + e^{-10t}] = 18e^{-10t}(1 - 10t)$$

$$\frac{di_L}{dt} = 0 \quad \text{when} \quad t = 0.1 \text{ s}$$

$$i_{\max} = 18(0.1)e^{-1} = 662.2 \text{ mA}$$

$$w_{\max} = \frac{1}{2}(50 \times 10^{-6})(662.2 \times 10^{-3})^2 = 10.96 \mu\text{J}$$

$$\text{P 6.21} \quad 30 \parallel 20 = 12 \text{ H}$$


$$80 \parallel (8 + 12) = 16 \text{ H}$$

$$60 \parallel (14 + 16) = 20 \text{ H}$$


$$15 \parallel (20 + 10) = 20 \text{ H}$$

$$L_{ab} = 5 + 10 = 15 \text{ H}$$

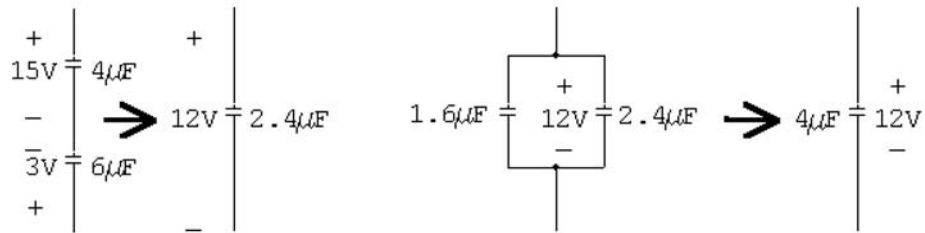
P 6.25 $\frac{1}{4} + \frac{1}{6} = \frac{5}{12} \therefore C_{eq} = 2.4 \mu\text{F}$



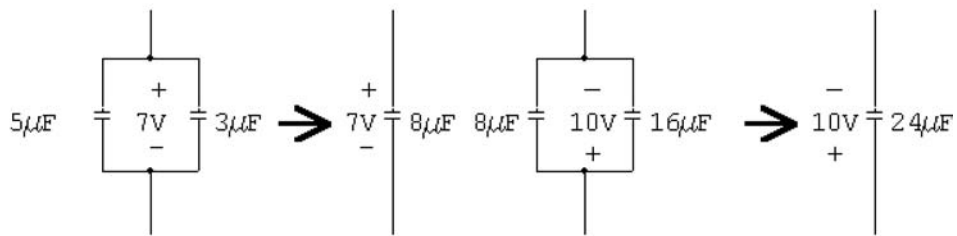$\frac{1}{4} + \frac{1}{12} = \frac{4}{12} \therefore C_{eq} = 3 \mu\text{F}$



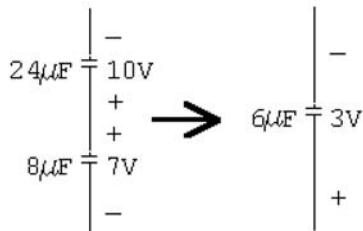$\frac{1}{24} + \frac{1}{8} = \frac{4}{24} \therefore C_{eq} = 6 \mu\text{F}$



P 7.4 [a] $\frac{v}{i} = R = \frac{400e^{-5t}}{10e^{-5t}} = 40 \Omega$

[b] $\tau = \frac{1}{5} = 200 \text{ ms}$

[c] $\tau = \frac{L}{R} = 200 \times 10^{-3}$

$$L = (200 \times 10^{-3})(40) = 8 \text{ H}$$

[d] $w(0) = \frac{1}{2}L[i(0)]^2 = \frac{1}{2}(8)(10)^2 = 400 \text{ J}$

[e] $w_{\text{diss}} = \int_0^t 4000e^{-10x} dx = 400 - 400e^{-10t}$

$$0.8w(0) = (0.8)(400) = 320 \text{ J}$$

$$400 - 400e^{-10t} = 320 \quad \therefore e^{10t} = 5$$

Solving, $t = 160.9 \text{ ms}$.

P 7.5 [a] $i_L(0) = \frac{12}{6} = 2 \text{ A}$

$$i_o(0^+) = \frac{12}{2} - 2 = 6 - 2 = 4 \text{ A}$$

$$i_o(\infty) = \frac{12}{2} = 6 \text{ A}$$

[b] $i_L = 2e^{-t/\tau}; \quad \tau = \frac{L}{R} = \frac{1}{4} \text{ s}$

$$i_L = 2e^{-4t} \text{ A}$$


$$i_o = 6 - i_L = 6 - 2e^{-4t} \text{ A}, \quad t \geq 0^+$$

[c] $6 - 2e^{-4t} = 5$

$$1 = 2e^{-4t}$$

$$e^{6t} = 2 \quad \therefore t = 173.3 \text{ ms}$$


P 7.9 For $t < 0^+$

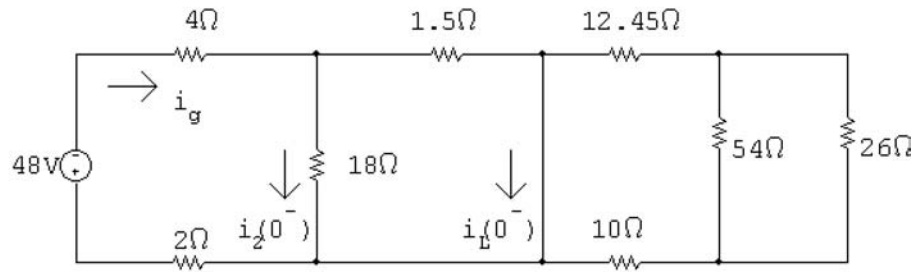

$$i_g = \frac{-48}{6 + (18 \parallel 1.5)} = -6.5 \text{ A}$$

$$i_L(0^-) = \frac{18}{18 + 1.5}(-6.5) = -6 \text{ A} = i_L(0^+)$$

For $t > 0$

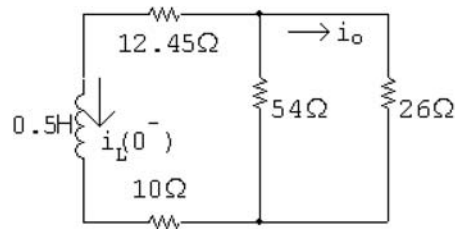


$$i_L(t) = i_L(0^+)e^{-t/\tau} \text{ A}, \quad t \geq 0$$

$$\tau = \frac{L}{R} = \frac{0.5}{10 + 12.45 + (54 \parallel 26)} = 0.0125 \text{ s}; \quad \frac{1}{\tau} = 80$$

$$i_L(t) = -6e^{-80t} \text{ A}, \quad t \geq 0$$


$$i_o(t) = \frac{54}{80}(-i_L(t)) = \frac{54}{80}(6e^{-80t}) = 4.05e^{-80t} \text{ V}, \quad t \geq 0^+$$

P 7.13 $t < 0$

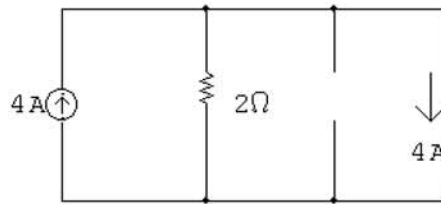


$$i_L(0^-) = i_L(0^+) = 4 \text{ A}$$

$t > 0$

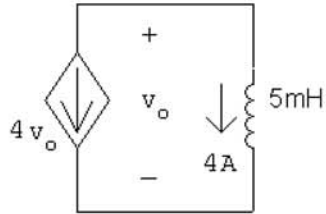


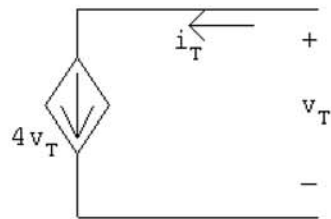Find Thévenin resistance seen by inductor



$$i_T = 4v_T; \quad \frac{v_T}{i_T} = R_{Th} = \frac{1}{4} = 0.25 \Omega$$
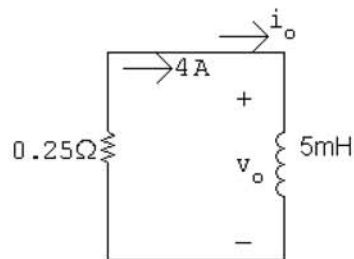
$$\tau = \frac{L}{R} = \frac{5 \times 10^{-3}}{0.25} = 20 \text{ ms}; \quad 1/\tau = 50$$




$$i_o = 4e^{-50t} \text{ A}, \quad t \geq 0$$

$$v_o = L \frac{di_o}{dt} = (5 \times 10^{-3})(-200e^{-50t}) = -e^{-50t} \text{ V}, \quad t \geq 0^+$$


P 7.21 [a] $v_1(0^-) = v_1(0^+) = 40 \text{ V}$ $v_2(0^+) = 0$
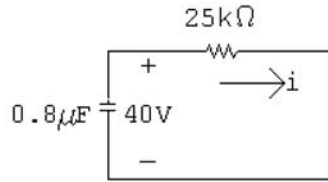
$$C_{\text{eq}} = (1)(4)/5 = 0.8 \mu\text{F}$$



$$\tau = (25 \times 10^3)(0.8 \times 10^{-6}) = 20 \text{ ms}; \quad \frac{1}{\tau} = 50$$
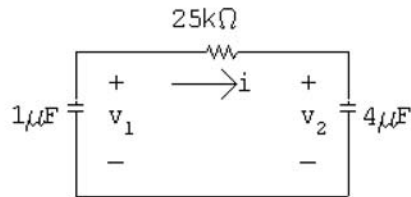
$$i = \frac{40}{25,000} e^{-50t} = 1.6 e^{-50t} \text{ mA}, \quad t \geq 0^+$$



$$v_1 = \frac{-1}{10^{-6}} \int_0^t 1.6 \times 10^{-3} e^{-50x} dx + 40 = 32e^{-50t} + 8 \text{ V}, \quad t \geq 0$$

$$v_2 = \frac{1}{4 \times 10^{-6}} \int_0^t 1.6 \times 10^{-3} e^{-50x} dx + 0 = -8e^{-50t} + 8 \text{ V}, \quad t \geq 0$$

[b] $w(0) = \frac{1}{2}(10^{-6})(40)^2 = 800 \mu\text{J}$


[c] $w_{\text{trapped}} = \frac{1}{2}(10^{-6})(8)^2 + \frac{1}{2}(4 \times 10^{-6})(8)^2 = 160 \mu\text{J}.$

The energy dissipated by the 25 kΩ resistor is equal to the energy dissipated by the two capacitors; it is easier to calculate the energy dissipated by the capacitors (final voltage on the equivalent capacitor is zero):

$$w_{\text{diss}} = \frac{1}{2}(0.8 \times 10^{-6})(40)^2 = 640 \mu\text{J}.$$

Check: $w_{\text{trapped}} + w_{\text{diss}} = 160 + 640 = 800 \mu\text{J}; \quad w(0) = 800 \mu\text{J}.$


P 7.25 [a] $t < 0$:

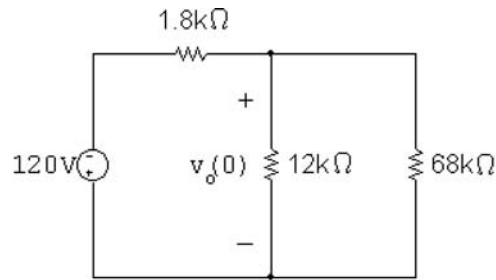

$$R_e = 12 \text{ k} \parallel 68 \text{ k} = 10.2 \text{ k}\Omega$$

$$v_o(0) = \frac{10,200}{10,200 + 1800}(-120) = -102 \text{ V}$$

$t > 0$:

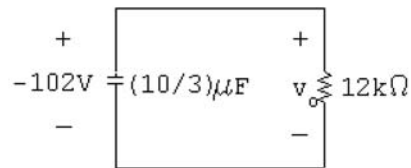

$$\tau = [(10/3) \times 10^{-6}](12,000) = 40 \text{ ms}; \quad \frac{1}{\tau} = 25$$

$$v_o = -102e^{-25t} \text{ V}, \quad t \geq 0$$

$$p = \frac{v_o^2}{12,000} = 867 \times 10^{-3} e^{-50t} \text{ W}$$

$$\begin{aligned} w_{\text{diss}} &= \int_0^{12 \times 10^{-3}} 867 \times 10^{-3} e^{-50t} dt \\ &= 17.34 \times 10^{-3} (1 - e^{-50(12 \times 10^{-3})}) = 7.82 \text{ mJ} \end{aligned}$$


$$\text{[b]} \quad w(0) = \left(\frac{1}{2}\right) \left(\frac{10}{3}\right) (102)^2 \times 10^{-6} = 17.34 \text{ mJ}$$

$$0.75w(0) = 13 \text{ mJ}$$


$$\int_0^{t_o} 867 \times 10^{-3} e^{-50x} dx = 13 \times 10^{-3}$$

$$\therefore 1 - e^{-50t_o} = 0.75; \quad e^{50t_o} = 4; \quad \text{so } t_o = 27.73 \text{ ms}$$

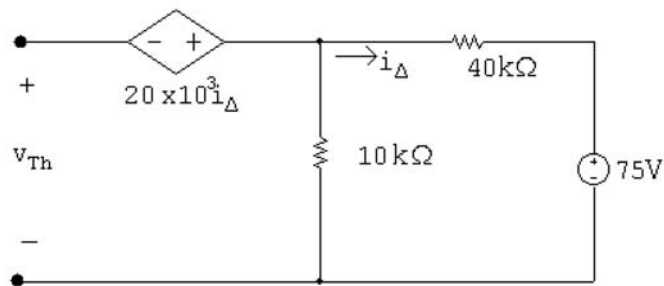P 7.55 For $t < 0$, $v_o(0) = (-3 \text{ m})(15 \text{ k}) = -45 \text{ V}$
 $t > 0$:



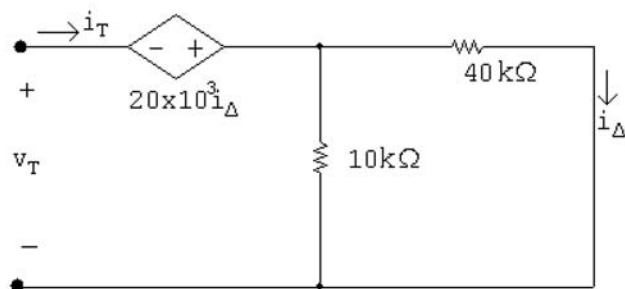
$$V_{Th} = -20 \times 10^3 i_{\Delta} + \frac{10}{50}(75) = -20 \times 10^3 \left(\frac{-75}{50 \times 10^3} \right) + 15 = 45 \text{ V}$$



$$v_T = -20 \times 10^3 i_{\Delta} + 8 \times 10^3 i_T = -20 \times 10^3 (0.2) i_T + 8 \times 10^3 i_T = 4 \times 10^3 i_T$$

$$R_{Th} = \frac{v_T}{i_T} = 4 \text{ k}\Omega$$

$t > 0$

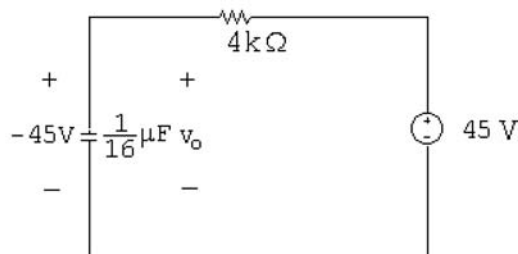


$$v_o = 45 + (-45 - 45)e^{-t/\tau}$$


$$\tau = RC = (4000) \left(\frac{1}{16} \times 10^{-6} \right) = 250 \mu\text{s}; \quad \frac{1}{\tau} = 4000$$

$$v_o = 45 - 90e^{-4000t} \text{ V}, \quad t \geq 0$$

P 7.60 [a] $t < 0$

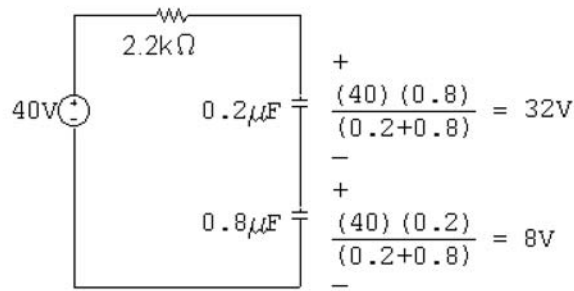

$t > 0$

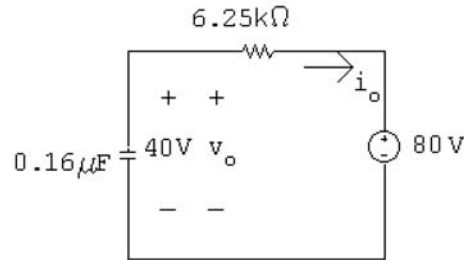

$$v_o(0^-) = v_o(0^+) = 40\text{ V}$$

$$v_o(\infty) = 80\text{ V}$$

$$\tau = (0.16 \times 10^{-6})(6.25 \times 10^3) = 1\text{ ms}; \quad 1/\tau = 1000$$

$$v_o = 80 - 40e^{-1000t}\text{ V}, \quad t \geq 0$$


$$\begin{aligned} \text{[b]} \quad i_o &= -C \frac{dv_o}{dt} = -0.16 \times 10^{-6} [40,000e^{-1000t}] \\ &= -6.4e^{-1000t}\text{ mA}; \quad t \geq 0^+ \end{aligned}$$

$$\begin{aligned} \text{[c]} \quad v_1 &= \frac{-1}{0.2 \times 10^{-6}} \int_0^t -6.4 \times 10^{-3} e^{-1000x} dx + 32 \\ &= 64 - 32e^{-1000t}\text{ V}, \quad t \geq 0 \end{aligned}$$

$$\begin{aligned} \text{[d]} \quad v_2 &= \frac{-1}{0.8 \times 10^{-6}} \int_0^t -6.4 \times 10^{-3} e^{-1000x} dx + 8 \\ &= 16 - 8e^{-1000t}\text{ V}, \quad t \geq 0 \end{aligned}$$

$$\text{[e]} \quad w_{\text{trapped}} = \frac{1}{2}(0.2 \times 10^{-6})(64)^2 + \frac{1}{2}(0.8 \times 10^{-6})(16)^2 = 512\text{ }\mu\text{J}.$$

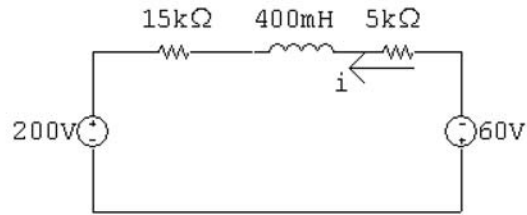
- P 7.63 [a] For $t < 0$, calculate the Thévenin equivalent for the circuit to the left and right of the 400-mH inductor. We get



$$i(0^-) = \frac{-60 - 200}{15\text{ k} + 5\text{ k}} = -13\text{ mA}$$

$$i(0^-) = i(0^+) = -13\text{ mA}$$

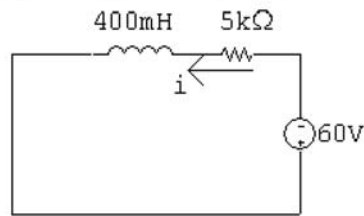- [b] For $t > 0$, the circuit reduces to



$$\text{Therefore } i(\infty) = -60/5,000 = -12\text{ mA}$$

[c] $\tau = \frac{L}{R} = \frac{400 \times 10^{-3}}{5000} = 80\ \mu\text{s}$

[d] $i(t) = i(\infty) + [i(0^+) - i(\infty)]e^{-t/\tau}$
 $= -12 + [-13 + 12]e^{-12,500t} = -12 - e^{-12,500t}\text{ mA}, \quad t \geq 0$