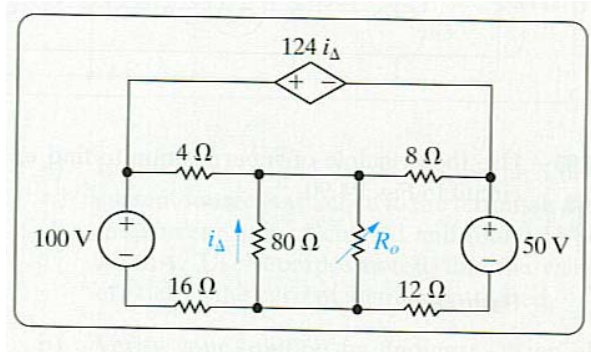


KING FAHD UNIVERSITY OF PETROLEUM & MINERALS
ELECTRICAL ENGINEERING DEPARTMENT
EE-201 ELECTRIC CIRCUITS
Dr. Ibrahim O. Habiballah


Sec: 8 Quiz # 3 Ser. # Name:

I.D.#

For the circuit shown below, find the maximum power transfer to R_o .



Solution

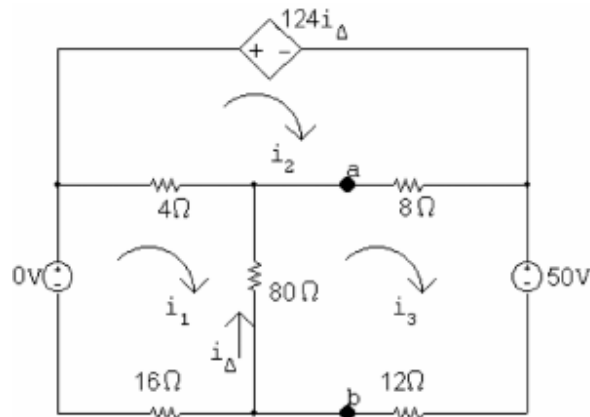

The mesh current equations are:

$$-100 + 4(i_1 - i_2) + 80(i_1 - i_3) + 16i_1 = 0$$

$$124i_\Delta + 8(i_2 - i_3) + 4(i_2 - i_1) = 0$$

$$50 + 12i_3 + 80(i_3 - i_1) + 8(i_3 - i_2) = 0$$

The constraint equation is:

$$i_\Delta = i_3 - i_1$$

Place these equations in standard form:

$$i_1(4 + 80 + 16) + i_2(-4) + i_3(-80) + i_{\Delta}(0) = 100$$

$$i_1(-4) + i_2(8 + 4) + i_3(-8) + i_{\Delta}(124) = 0$$


$$i_1(-80) + i_2(-8) + i_3(12 + 80 + 8) + i_{\Delta}(0) = -50$$

$$i_1(1) + i_2(0) + i_3(-1) + i_{\Delta}(1) = 0$$

Solving, $i_1 = 4.7 \text{ A}$; $i_2 = 10.5 \text{ A}$; $i_3 = 4.1 \text{ A}$; $i_{\Delta} = -0.6 \text{ A}$

Also, $V_{Th} = v_{ab} = -80i_{\Delta} = 48 \text{ V}$

Now find the short-circuit current.

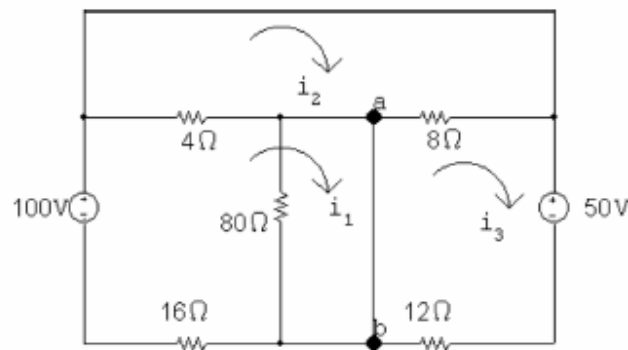

Note with the short circuit from a to b that i_{Δ} is zero, hence $124i_{\Delta}$ is also zero.

The mesh currents are:

$$-100 + 4(i_1 - i_2) + 16i_1 = 0$$

$$8(i_2 - i_3) + 4(i_2 - i_1) = 0$$

$$50 + 12i_3 + 8(i_3 - i_2) = 0$$

Place these equations in standard form:

$$i_1(4 + 16) + i_2(-4) + i_3(0) = 100$$


$$i_1(-4) + i_2(8 + 4) + i_3(-8) = 0$$

$$i_1(0) + i_2(-8) + i_3(12 + 8) = -50$$

Solving, $i_1 = 5 \text{ A}$; $i_2 = 0 \text{ A}$; $i_3 = -2.5 \text{ A}$

Then, $i_{sc} = i_1 - i_3 = 7.5 \text{ A}$

$$R_{Th} = 48/7.5 = 6.4 \Omega$$

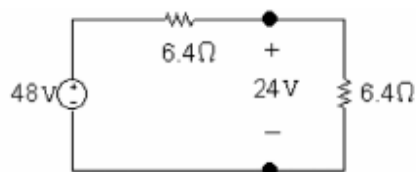

For maximum power transfer $R_o = R_{Th} = 6.4 \Omega$

$$p_{max} = \frac{24^2}{6.4} = 90 \text{ W}$$