


**KING FAHD UNIVERSITY OF PETROLEUM & MINERALS**  
**ELECTRICAL ENGINEERING DEPARTMENT**  
**EE-201 ELECTRIC CIRCUITS**  
**Dr. Ibrahim O. Habiballah**

Sec: 8    Quiz # 4    Ser. #    Name:

I.D.#

For the circuit shown below calculates

- a)  $v_o$
- b)  $i_o$

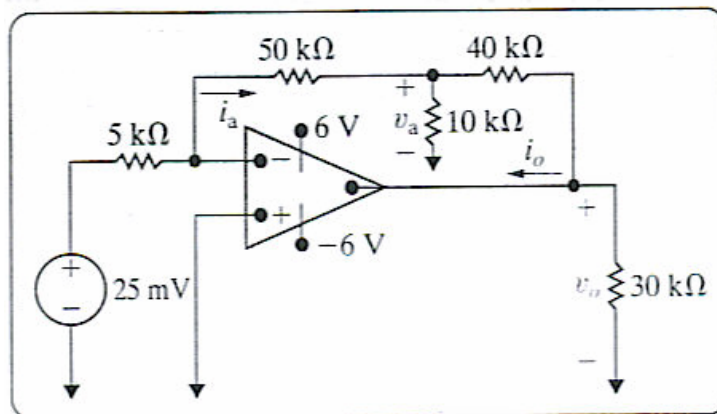

$$i_a = \frac{25 \times 10^{-3}}{5000} = 5 \mu\text{A}$$

$$v_a = -50 \times 10^3 i_a = -250 \text{ mV}$$

$$\frac{v_a}{50,000} + \frac{v_a}{10,000} + \frac{v_a - v_o}{40,000} = 0$$

$$\therefore 4v_a + 20v_a + 5v_a - 5v_o = 0$$

$$\therefore v_o = 29v_a/5 = -1.45 \text{ V}$$

$$i_o = \frac{-v_o}{30,000} + \frac{v_a - v_o}{40,000} = 78.33 \mu\text{A}$$

