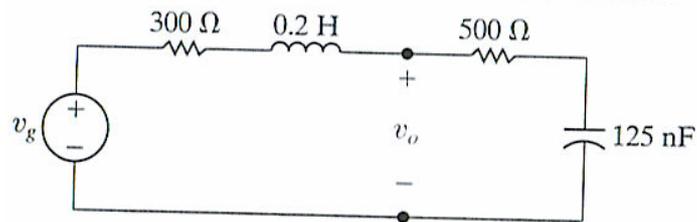


KING FAHD UNIVERSITY OF PETROLEUM & MINERALS
ELECTRICAL ENGINEERING DEPARTMENT
EE-201 ELECTRIC CIRCUITS
Dr. Ibrahim O. Habiballah

Sec: 8 Quiz # 7 Ser. # Name:

I.D.#

Find $v_o(t)$ by voltage divider; $v_g(t) = 100 \cos 8000t$ V.



Solution

$$\mathbf{V}_o = \mathbf{V}_g \frac{Z_o}{Z_T} = \frac{500 - j1000}{300 + j1600 + 500 - j1000} (100 \angle 0^\circ) = 111.8 \angle -100.3^\circ \text{ V}$$

$$v_o = 111.8 \cos(8000t - 100.3^\circ) \text{ V}$$