

KING FAHD UNIVERSITY OF PETROLEUM & MINERALS
ELECTRICAL ENGINEERING DEPARTMENT

Dr. Ibrahim O. Habiballah

EE-360

Key Solution

Quiz 1

ser#:

I.D.:

Name:

A three-phase substation bus supplies two wye-connected loads that are connected in parallel through a three-phase feeder with impedance of $0.5 + j 2.0$ Ohm per phase. Load 1 draws 50 kW at 0.866 lagging power factor, and load 2 draws 36 kVA at 0.9 leading power factor. The line-to-line voltage at the loads is 460 V.

1) Impedance of each load is

- a. $Z_{L1} = 3.66 \angle 30^\circ \Omega$; $Z_{L2} = 5.88 \angle -25.8^\circ \Omega$
- b. $Z_{L1} = 3.66 \angle 30^\circ \Omega$; $Z_{L2} = 5.29 \angle -25.8^\circ \Omega$
- c. $Z_{L1} = 6.34 \angle 30^\circ \Omega$; $Z_{L2} = 10.18 \angle -25.8^\circ \Omega$
- d. $Z_{L1} = 3.66 \angle -30^\circ \Omega$; $Z_{L2} = 5.88 \angle 25.8^\circ \Omega$

2) Line-to-line voltage at the substation bus is

- a. $V = 693.2 \angle 58.2^\circ \Omega$
- b.** $V = 696.5 \angle 59.5^\circ \Omega$
- c. $V = 696.5 \angle 29.5^\circ \Omega$
- d. $V = 693.2 \angle 28.2^\circ \Omega$