

KING FAHD UNIVERSITY OF PETROLEUM & MINERALS
ELECTRICAL ENGINEERING DEPARTMENT

Dr. Ibrahim O. Habiballah

EE-360

Key Solution

Quiz 1 ser#: I.D.: Name:

A three-phase substation bus supplies two wye-connected loads that are connected in parallel through a three-phase feeder with impedance of $0.5 + j 2.0$ Ohm per phase. Load 1 draws 50 kW at 0.866 lagging power factor, and load 2 draws 36 kVA at 0.9 leading power factor. The line-to-line voltage at the loads is 460 V.

1) Total line current flowing through the feeder is

- a. $I = 104.8 \angle -9.1^\circ \Omega$
- b. $I = 101.13 \angle -10.7^\circ \Omega$
- c. $I = 157.3 \angle -13.64^\circ \Omega$
- d. $I = 100.75 \angle 9.46^\circ \Omega$

2) Total real and reactive power supplied by the substation bus is

- a. $P = 98.8 \text{ kW}$; $Q = 78.9 \text{ kVAR}$ (capacitive)
- b. $P = 98.8 \text{ kW}$; $Q = 78.9 \text{ kVAR}$ (inductive)**
- c. $P = 80.9 \text{ kW}$; $Q = 71.01 \text{ kVAR}$ (capacitive)
- d. $P = 80.9 \text{ kW}$; $Q = 71.01 \text{ kVAR}$ (inductive)