

KING FAHD UNIVERSITY OF PETROLEUM & MINERALS
ELECTRICAL ENGINEERING DEPARTMENT

Dr. Ibrahim O. Habiballah
EE-360

Key Solution

Quiz # 3 Ser. # I.D.# Name:

A 5 kVA, 480/120 V transformer is connected as a step-down autotransformer.

1) The autotransformer ratings are

- a- 6.25 kVA ; 600/480 V
- b- 25 kVA ; 600/480 V**
- c- 25 kVA ; 600/120 V
- d- 6 kVA ; 600/120 V

2) The amount of kVA transferred by conduction is

- a- 1.25
- b- 5
- c- 20**
- d- 1