

**KING FAHD UNIVERSITY OF PETROLEUM & MINERALS**  
**ELECTRICAL ENGINEERING DEPARTMENT**  
**Dr. Ibrahim O. Habiballah**  
**EE 360**

Quiz # 5    Serial #

Name:

I.D.#

**Key Solution**

1) The terminal voltage of a shun DC generator can be controlled as follows:

a-  $n \uparrow \Rightarrow E_A \downarrow \Rightarrow V_T \uparrow$

b-  $R_F \downarrow \Rightarrow I_F \uparrow \Rightarrow E_A \downarrow \Rightarrow V_T \uparrow$

**c-  $R_F \uparrow \Rightarrow I_F \downarrow \Rightarrow E_A \downarrow \Rightarrow V_T \downarrow$**

d- None of above

2) A long-shunt differentially compounded 240 V DC generator has armature, shunt field, and series field winding resistances of 0.2 Ohm, 200 Ohm, 0.1 Ohm, respectively. If the generator delivers 11.7 kW, the back EMF (i.e.,  $E_A$ ) of the generatos is

a- 254.3 V

b- 225 V

**c- 255 V**

d- 225.7 V