

KING FAHD UNIVERSITY OF PETROLEUM & MINERALS

ELECTRICAL ENGINEERING DEPARTMENT

EE-463-1 Project

Semester (011)

The line-data and bus-data of a 9-bus system are given below.

Line-Data

From-To	Impedance (per unit)	Total Line Charging (per unit)	Tap Position (per unit)	MVA Rating
1-4	$j0.0576$		1.02	150
2-7	$j0.00625$			200
3-9	$j0.0586$		1.01	150
4-5	$0.01+j0.085$	$j0.088*2$		100
4-6	$0.017+j0.092$	$j0.079*2$		50
5-7	$0.032+j0.161$	$j0.153*2$		150
7-8	$0.0085+j0.072$	$j0.1045*2$		100
8-9	$0.0119+j0.1008$	$j0.1045*2$		75
6-9	$0.039+j0.17$	$j0.179$		100

The impedances are on 100 MVA base.

Bus-Data

Bus Code	Bus Voltage (per unit)	P_G (MW)	Q_G (MVAR)	P_L (MW)	Q_L (MVAR)	Q_{min} (MVAR)	Q_{max} (MVAR)
1	$1.04+j0.0$	-	-				
2	1.025	163	-				60
3	1.025	85	0				20
5	-			125	50		
6	-			90	30		
8				100	35		

Use the Power World Simulation Package (the latest version can be downloaded from www.powerworld.com) to simulate the above system indicating the following:

- The single line diagram of the system including the circuit breaker at both ends of every line.
- The voltage (p.u.), generation (MW and MVAR), and load (MW and MVAR) for each bus, where applicable.
- The line-flows (MW and MVAR) at both ends of every line.
- The line-flow pie chart at both ends of every line.

Perform the following tasks:

- Run your **own case** ** for a simulation time of 2 hours (7200 seconds) and simulation speedup of 60 seconds.
- Use the load variation graph to simulate a varying load from 100% (using the base case) to 200%.
- Show the animated flows on the single-line diagram.
- Enforce the line overloads to check the line limits.
- Detect and record any system's abnormality during the simulation time (e.g., bus voltages outside 5% range of the nominal values, overloaded lines, ...etc.).

Introduce at least two different remedies for the problems detected earlier to ensure a normal operation of the system during the simulation time.

Write a formal typed-report showing the following items:

- The single-line diagram of the original case.
- The single-line diagram of the modified cases (the two solutions).
- Statement on the problems faced during the simulation time.
- Statements on the suggested solutions with clear explanation and justification.
- Comparison and discussion of the best solution.

Due dates:

November 5, 2000	The single-line diagram of the original case.	(10%)
November 24, 2000	The single-line diagram of the modified cases.	(20%)
December 3, 2000	Final Report including the above items.	(60%)
December 29-31, 2000	Oral Exam.	(10%)

** Your own case is as follows:

	Line-resistance	Line-reactance	MVA Rating	$P_L + j Q_L$
odd	x 1.4	x 1.2	x 1.(ser# + 9)	same
even	x 1.5	x 1.1	same	x 1.(ser# + 9)

