

## ELECTRICAL ENGINEERING DEPARTMENT

### EE-466 Project Semester (062)

**Objective:** Design the protective scheme of the power system shown below. It is required to size all the CTs, define type of protection and relay setting.

**Procedure:** You may use ETAP or EDSA software programs.


- Steps**
1. Draw the network with all the data as provided.
  2. Run a load flow to determine your steady state conditions.
  3. Perform short circuit analysis at different buses.
  4. Select and size all CT
  5. Connect relays where appropriate
  6. Carry out . coordinating studies to adjust relay settings.
  7. Check for relay operation for selected fault locations.

**Report** : Prepare a detailed report of your work.

**Presentation** : Prepare a PowerPoint presentation about your work. Presentations will be scheduled at a later time.

**Power Grid**

1000 MVA<sub>sc</sub>  
X/R = 22

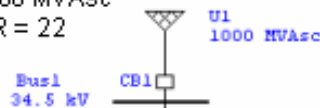

**Cable1**


ICEA 15kV 3/C CU,  
100%  
Size= 250  
Length= 400 ft

**Gen1**

10 MW  
Voltage Control  
Design:  
%Pf= 85  
MW = 5  
Max Q = 4  
Min Q = -1

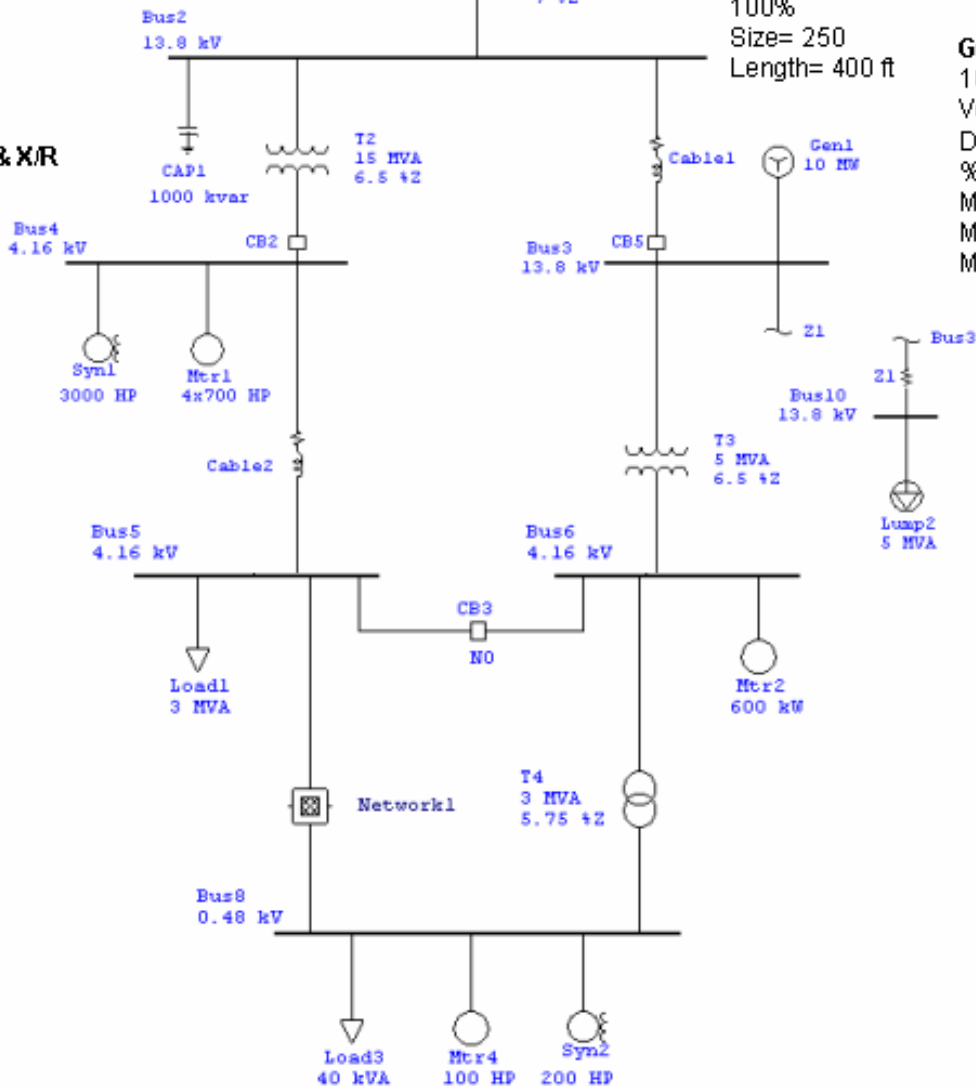**Transformers**

T1 = 30 MVA  
T2 = 15 MVA  
T3 = 5 MVA  
T4 = 3 MVA  
T5 = 5 MVA  
Select typical %Z & X/R




**Impedance**

Z1  
13.8 kV  
100MVA  
% Z = 0.01 + j1

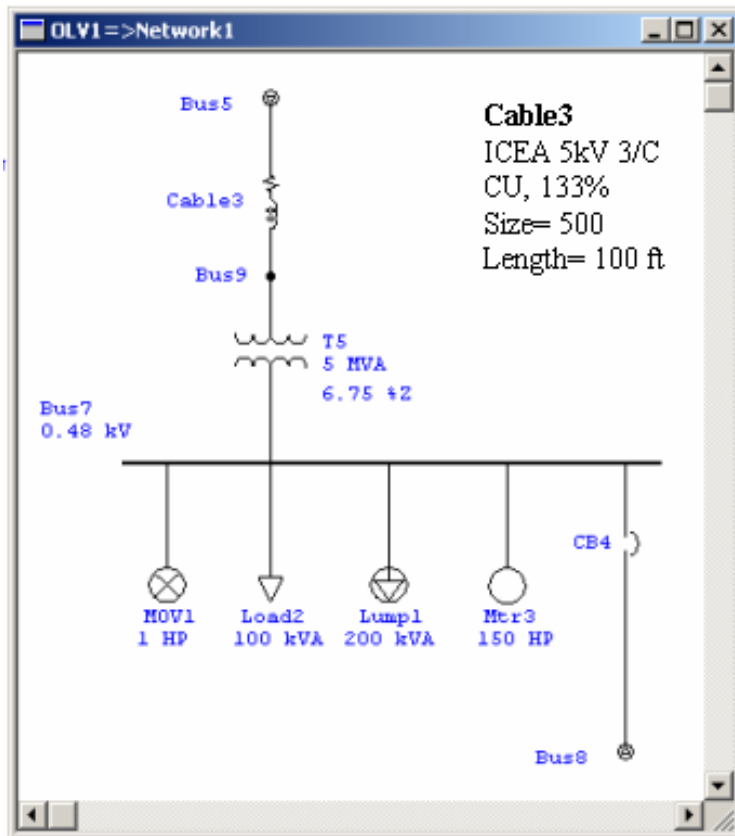**Cable2**

KERITE 5kV 3/C  
CU, 100%  
Size= 500  
Length= 300 ft



**NB. You may work in a group of two but no more**

**Report Submission May 31, 2007**