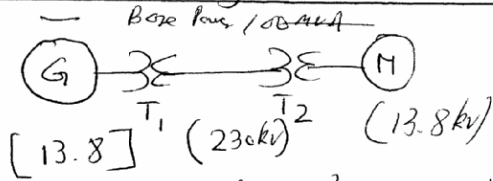



Solution Assignment #1

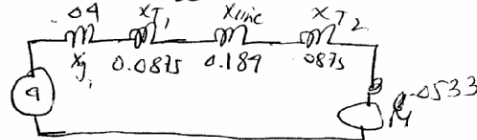Q1



$$X_{g1} = 0.04 \frac{(100)}{(100)} \cdot \frac{13.8^2}{13.8^2} = 0.04 ; X_M = 0.04 \frac{(100)}{775} \cdot \frac{13.8^2}{13.8^2} = 0.0533$$

$$X_{T1} = X_{T2} = 0.07 \frac{(100)}{80} = 0.0875 ; X_{line} = \frac{100(100)}{230^2} = 0.189$$



Q2

$$\begin{bmatrix} V_0 \\ V_1 \\ V_2 \end{bmatrix} \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} 177 \angle 0 \\ 156 \angle -10 \\ 105 \angle 20 \end{bmatrix} = \begin{bmatrix} 19.96 - j63.86 \\ 98.58 + j62.09 \\ 48.865 + j31.27 \end{bmatrix} ; \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} 0 + j2.0 \\ -0.8 - j2.6 \\ 0 - j2.2 \end{bmatrix} = \begin{bmatrix} 0.8 - j7.6 \\ 0.066 - j0.1 \\ -1.66 - j2.4 \end{bmatrix}$$

Q3

Q3 Two generators are connected through two transformers to a high voltage bus which supplies a line. The line is open-circuited at the remote. The pre-fault voltage at the end of the line is 515 KV. The system is shown below and the system data is given in the following a table.


Table 2 System data

| Equipment | Rated power (MVA) | Rated voltage (KV) | X ₁ Per unit | X ₂ Per unit | X ₀ Per unit |
|-------------------|-------------------|--------------------|-------------------------|-------------------------|-------------------------|
| G ₁ | 1000 | 20 | 0.1 | 0.1 | 0.05 |
| G ₂ | 800 | 22 | 0.15 | 0.15 | 0.08 |
| T ₁ | 1000 | 500Y/20Δ | 0.175 | 0.175 | 0.175 |
| T ₂ | 800 | 500Y/22Y | 0.16 | 0.16 | 0.16 |
| Transmission Line | 1500 | 500 | 0.15 | 0.15 | 0.07 |

Work on a base power of 1000 MVA and base voltage 500 kV on the transmission line. The neutral of Generator G₁ is grounded through a reactance of 0.04 Ohms.

Find the value of the fault current in amperes for the faults at the end of line for the following cases:

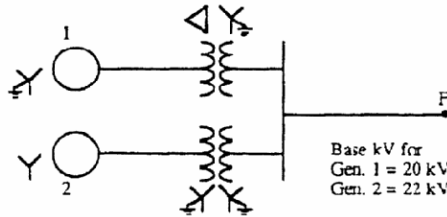- Single-line-ground
- Line-line
- Line-line-ground



$$X_{G2} = 0.15 \times \frac{1000}{800} = 0.1875$$

$$X_{T2} = 0.16 \times \frac{1000}{800} = 0.2$$




$$X_{line} = 0.15 \times \frac{1500}{500} = 0.45; \quad X_0 = 0.07 \times \frac{1500}{500} = 0.21$$

$$Z_1 = 0.261; \quad Z_2 = 0.261; \quad Z_0 = 0.442$$

a) $I_1 = \frac{1.03}{\sum Z} = -j4.33; \quad I_F = 15200A$

b) $I_1 = I_2 = \frac{1.03}{Z_1 + Z_2} = -j1.973; \quad I_B = (\alpha^2 - \alpha)I_1 = 3.417 p.u. = 3958A$

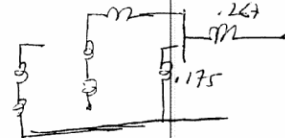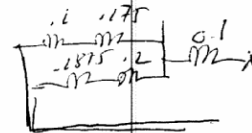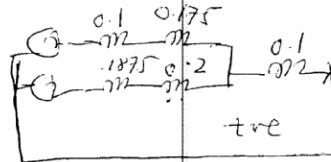c) $I_1 = \frac{1.03}{Z_1 + (Z_2 // Z_0)} = \frac{1.03}{0.261 + 0.164} = 2.42 p.u.; \quad I_2 = 1.52; \quad I_0 = 0.898$




$$I_{base} = \frac{1000 \times 10^3}{\sqrt{3} \times 500} = 1154.73$$

- Q4. (a) Draw the zero sequence impedance diagram of the following network. The zero sequence impedance of each component is given in per cent to the same base.

| Equipment | Reactance (per unit) |
|-----------|----------------------|
| G_1-G_3 | 0.1 |
| T_1-T_6 | 0.05 |
| X_n | 0.05 |
| X_{112} | 0.80 |
| X_{113} | 0.40 |
| X_{123} | 0.55 |

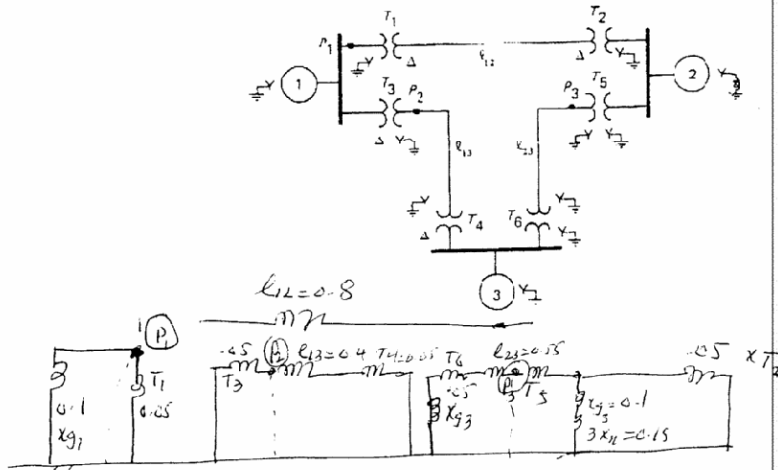- (b) Obtain the Thevenin equivalent zero sequence impedance for faults at points P1, P2 and P3.



$$P_1 \quad Z_0 = 0.1 // 0.05 = \underline{\underline{0.0333}}$$

$$P_2 \quad Z_0 = 0.05 // (0.45) = \underline{\underline{0.045}}$$

$$P_3 = (0.05 // 0.1) // \left(0.05 + (0.25 // 0.05) \right) = \underline{\underline{0.081}}$$