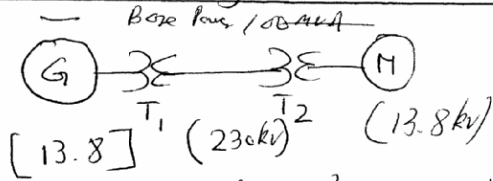



Solution Assignment #1

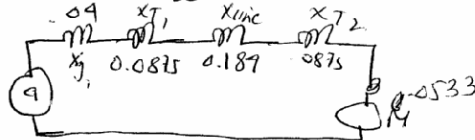Q1



$$X_{g1} = 0.04 \frac{(100)}{(100)} \cdot \frac{13.8^2}{13.8^2} = 0.04 ; X_M = 0.04 \frac{(100)}{775} \cdot \frac{13.8^2}{13.8^2} = 0.0533$$

$$X_{T1} = X_{T2} = 0.07 \frac{(100)}{80} = 0.0875 ; X_{line} = \frac{100(100)}{230^2} = 0.189$$



Q2

$$\begin{bmatrix} V_0 \\ V_1 \\ V_2 \end{bmatrix} \frac{1}{3} \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} 177 \angle 0 \\ 156 \angle -10 \\ 105 \angle 20 \end{bmatrix} = \begin{bmatrix} 19.96 - j63.86 \\ 98.58 + j62.09 \\ 48.865 + j31.27 \end{bmatrix} ; \begin{bmatrix} I_a \\ I_b \\ I_c \end{bmatrix} = \begin{bmatrix} 1 & 1 & 1 \\ 1 & a^2 & a \\ 1 & a & a^2 \end{bmatrix} \begin{bmatrix} 0 + j2.0 \\ -0.8 - j2.6 \\ 0 - j2.2 \end{bmatrix} = \begin{bmatrix} 0.8 - j7.6 \\ 0.066 - j0.1 \\ -1.66 - j2.4 \end{bmatrix}$$

Q3

03 Two generators are connected through two transformers to a high voltage bus which supplies a line. The line is open-circuited at the remote. The pre-fault voltage at the end of the line is 515 KV. The system is shown below and the system data is given in the following a table.


Table 2 System data

Equipment	Rated power (MVA)	Rated voltage (KV)	X ₁ Per unit	X ₂ Per unit	X ₀ Per unit
G ₁	1000	20	0.1	0.1	0.05
G ₂	800	22	0.15	0.15	0.08
T ₁	1000	500Y/20Δ	0.175	0.175	0.175
T ₂	800	500Y/22Y	0.16	0.16	0.16
Transmission Line	1500	500	0.15	0.15	0.07

Work on a base power of 1000 MVA and base voltage 500 kV on the transmission line. The neutral of Generator G₁ is grounded through a reactance of 0.04 Ohms.

Find the value of the fault current in amperes for the faults at the end of line for the following cases:

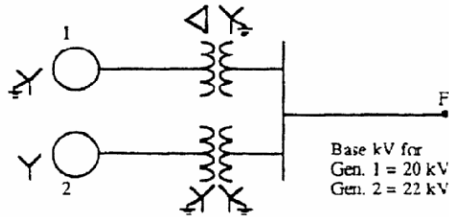- (i) Single-line-ground
- (ii) Line-line
- (iii) Line-line-ground



$$X_{G2} = 0.15 \times \frac{1000}{800} = 0.1875$$

$$X_{T2} = 0.16 \times \frac{1000}{800} = 0.2$$




$$X_{line} = 0.15 \times \frac{1500}{500} = 0.45; X_0 = 0.07 \times \frac{1500}{500} = 0.21$$

$$Z_1 = 0.261; Z_2 = 0.261; Z_0 = 0.442$$

a) $I_1 = \frac{1.03}{\sum Z} = -j4.33; I_F = 15200A$

b) $I_1 = I_2 = \frac{1.03}{Z_1 + Z_2} = -j1.973; I_B = (\alpha^2 - \alpha)I_1 = 3.417 p.u. = 3958A$

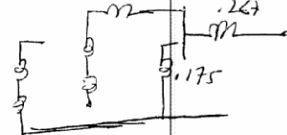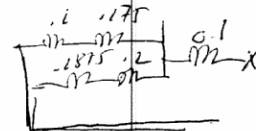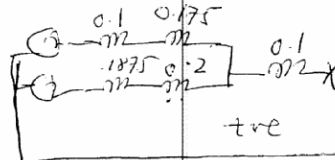c) $I_1 = \frac{1.03}{Z_1 + (Z_2 // Z_0)} = \frac{1.03}{0.261 + 0.164} = 2.42 p.u.; I_2 = 1.52; I_0 = 0.898$




$$I_{base} = \frac{1000 \times 10^3}{\sqrt{3} \times 500} = 1154.73$$

- Q4. (a) Draw the zero sequence impedance diagram of the following network. The zero sequence impedance of each component is given in per cent to the same base.

Equipment	Reactance (per unit)
G_1-G_3	0.1
T_1-T_6	0.05
X_n	0.05
X_{112}	0.80
X_{113}	0.40
X_{123}	0.55

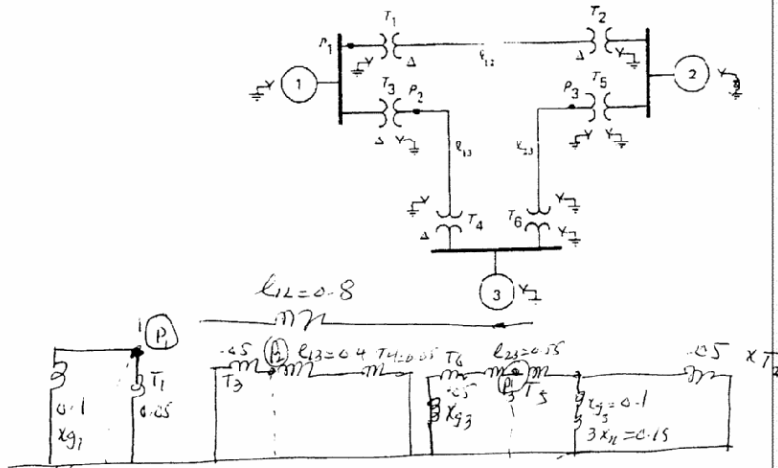- (b) Obtain the Thevenin equivalent zero sequence impedance for faults at points P1, P2 and P3.



$$P_1 \quad Z_0 = 0.1 // 0.05 = \underline{\underline{0.0333}}$$

$$P_2 \quad Z_0 = 0.05 // (0.45) = \underline{\underline{0.045}}$$

$$P_3 = (0.05 // 0.1) // (0.05 + (0.25 // 0.05)) = \underline{\underline{0.081}}$$