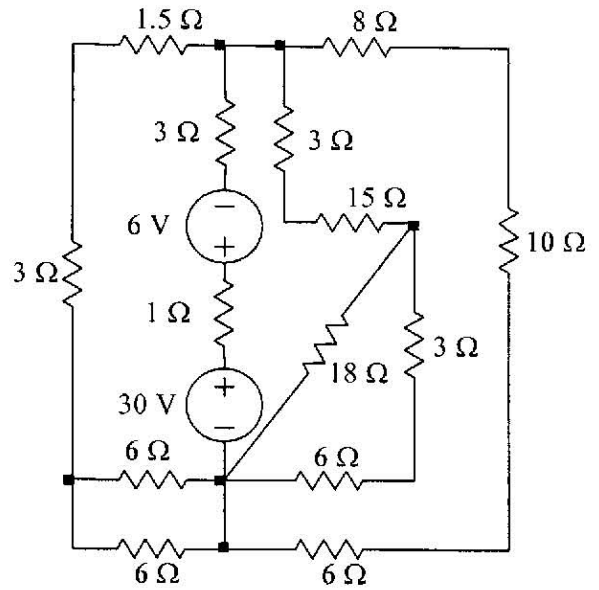


Problem2:




In the circuit shown, find the power absorbed by the 1.5Ω resistor $P_{1.5\Omega}$.

(Note: no need to find the power of the other resistors except the 1.5Ω resistor)

$V_{DR} \Rightarrow$
 $V = 12.858V$
 $\Rightarrow i = \frac{V}{7.5} = \frac{12.858}{7.5} = 1.714A$
 $\Rightarrow P_{1.5\Omega} = i^2(1.5) = (1.714)^2(1.5)$
 $= 4.41W$





reduce \Downarrow

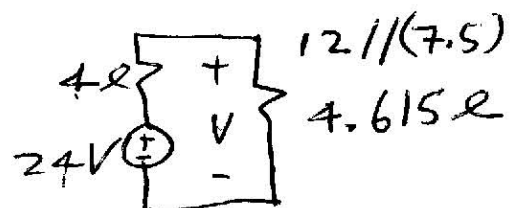
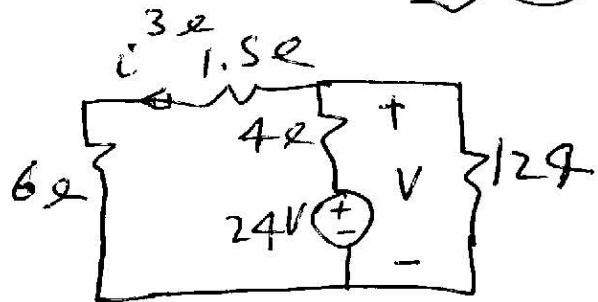
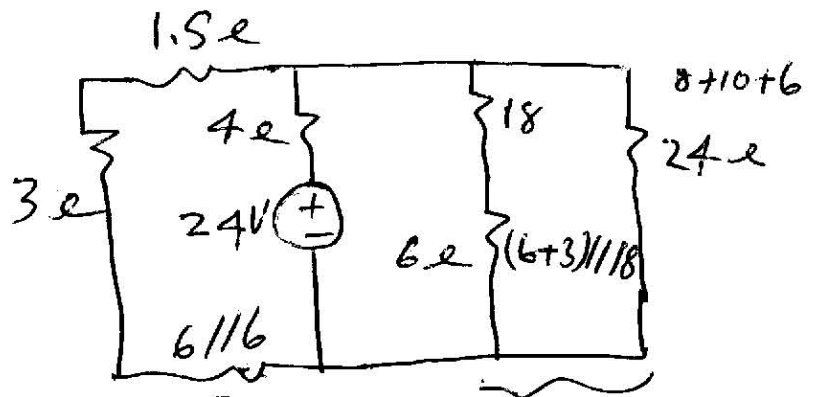


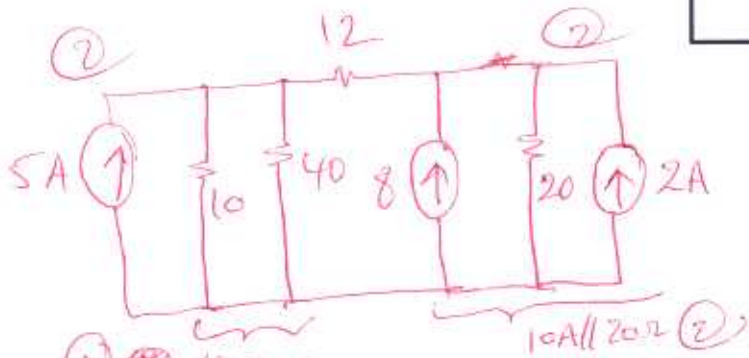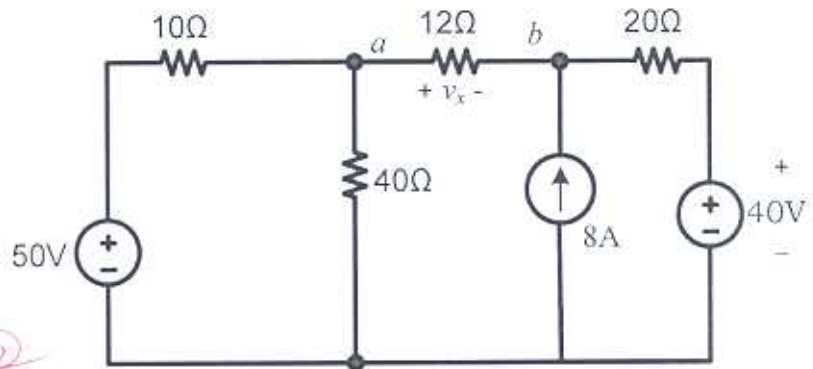Problem 3:

Apply source transformations to reduce the circuit shown to a single loop, then find v_x .



① $\frac{400}{50} = 8$

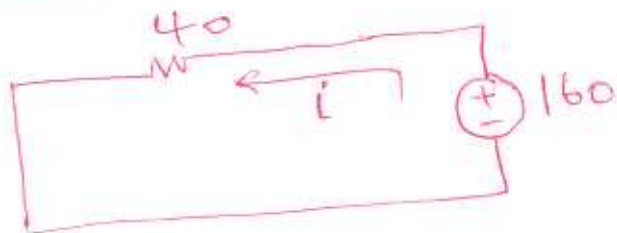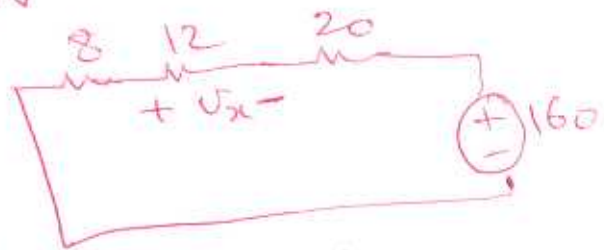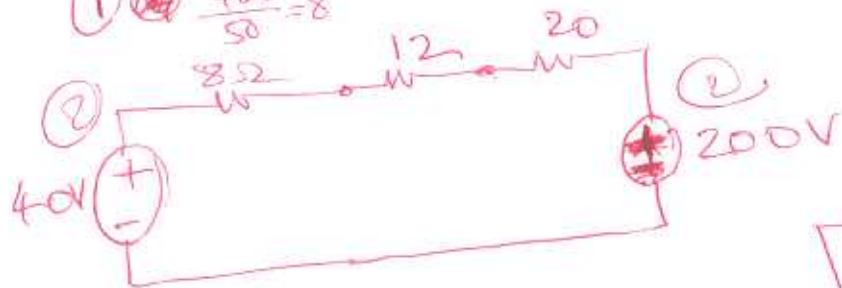

② $i = \frac{160}{40} = 4A$


$$v_x = -i \cdot 12$$

$$= -4 \times 12 = \underline{\underline{-48V}}$$
 ③


15 points

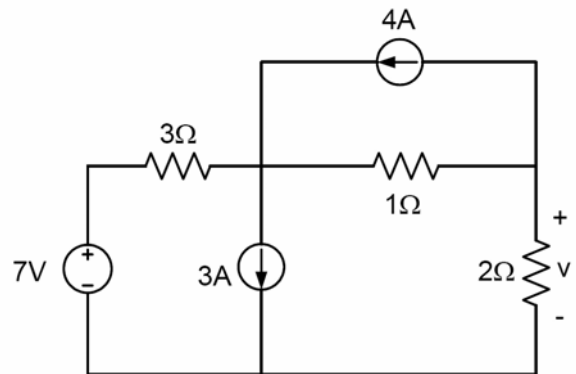Problem 4:


Apply the superposition principle to determine the voltage v in the circuit shown.


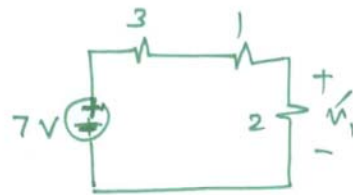
$$\hat{v}_1 = \frac{2}{6} \times 7 = \frac{14}{6} \text{ Volt}$$




$$i_1 = \frac{1}{6} \times 4 \text{ A}$$

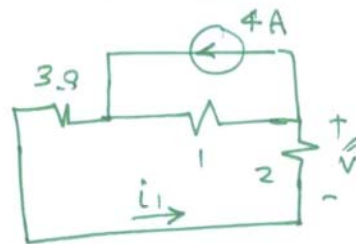

$$\therefore \hat{v} = -2i_1 = -\frac{8}{6} \text{ V}$$
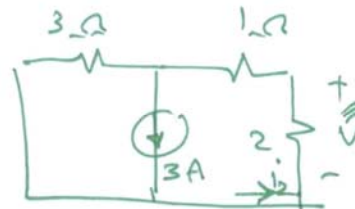
$$i_2 = \frac{3}{6} \approx 3 = \frac{3}{2} \text{ A}$$



$$\therefore \hat{v} = -2i_2 = -3 \text{ V}$$

$$\therefore v = \hat{v} + \hat{v} + \hat{v} = \frac{14}{6} - \frac{8}{6} - 3$$

$$= -2 \text{ Volt}$$

