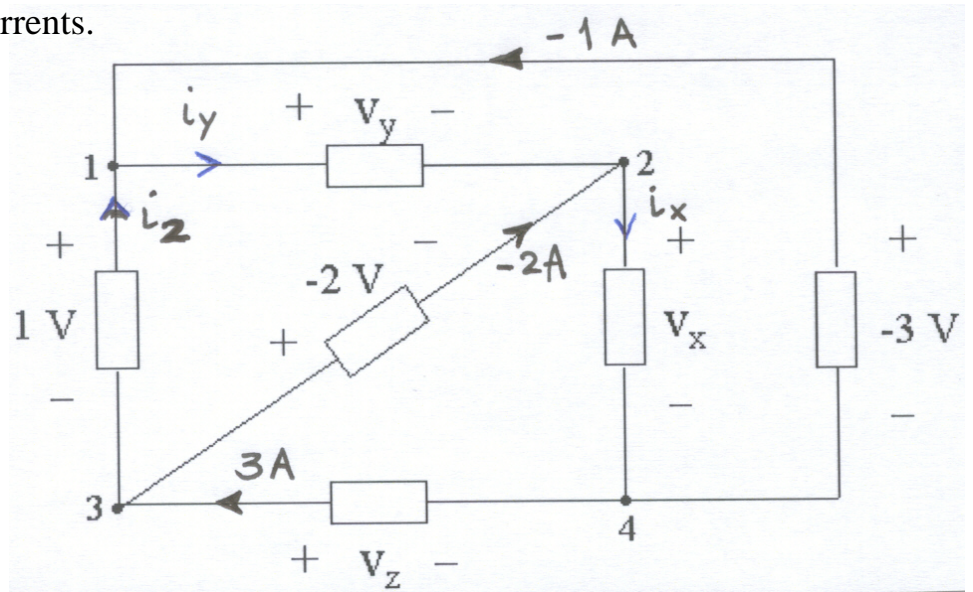


Find all unknown voltages and currents.



$V_x =$	$V_y =$	$V_z =$
$i_x =$	$i_y =$	$i_2 =$