

KING FAHD UNIVERSITY OF PETROLEUM AND MINERALS
ELECTRICAL ENGINEERING DEPARTMENT

COURSE
SECTION
EXAM
PLACE
DATE
TIME
INSTRUCTOR

EE#205
1,2,3,4
MAJOR I
March 25,2008
8:30 P.M.

STUDENT NAME

STUDENT I.D.

PROBLEM 1	
PROBLEM 2	
PROBLEM 3	
TOTAL	


Q-1

For a positive sequence 3 phase balanced Y - Δ network, the open circuit terminals voltage of the generator of phase a-n is given by $V_g = 360 \angle 0^\circ$ volts. The phase BC at the load has a voltage $V_{BC} = 300 \angle -105^\circ$. Given that: $Z_g = 1-j7$ and $Z_{line} = 3+j1$, find:

- 1- The line current I_{aA} .
- 2- The load impedance per phase Z_Δ .
- 3- The total complex power delivered to the three loads.

$$V_{BC} = V_{AB} \angle -120 = 300 \angle -105^\circ$$
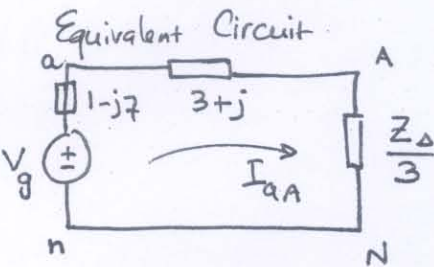
$$\therefore V_{AB} = 300 \angle 15^\circ \quad (1.5)$$



$$V_{AB} = \sqrt{3} V_{AN} \angle 30^\circ$$

$$\Rightarrow V_{AN} = \frac{V_{AB}}{\sqrt{3} \angle 30^\circ} = \frac{300}{\sqrt{3}} \angle -15^\circ = 173.2 \angle -15^\circ \quad (1.5)$$


From KVL

$$I_{aA} = \frac{V_g - V_{AN}}{4 - j6} = \frac{27.43 \angle 69.4^\circ}{4 - j6} \quad (2) \quad (3)$$

$$\frac{Z_\Delta}{3} = \frac{V_{AN}}{I_{aA}} = \frac{173.2 \angle -15^\circ}{27.43 \angle 69.4^\circ} = 6.313 \angle -84.4^\circ$$

$$\therefore Z_\Delta = 18.939 \angle -84.4^\circ = 1.848 - j18.85 \Omega = R_\Delta - jX_\Delta \quad (3)$$
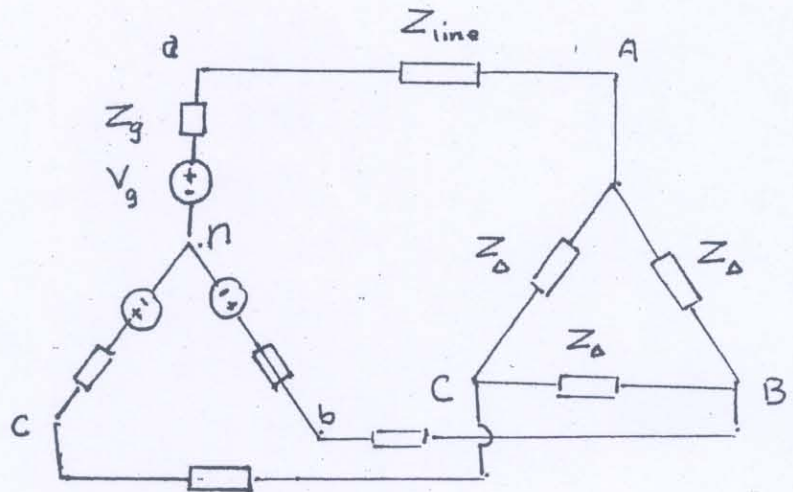
$$\text{OR } Z_\Delta = \frac{V_{AB}}{I_{AB}} = \frac{300 \angle 15^\circ}{15.836 \angle 99.4^\circ} = 18.939 \angle -84.4^\circ$$



$$S = 3 V_{AB} I_{AB}^*$$

$$I_{AB} = \frac{I_{aA}}{\sqrt{3}} \angle 30^\circ = \frac{15.836 \angle 69.4^\circ}{\sqrt{3}} \angle 30^\circ = 15.836 \angle 99.4^\circ \quad (4)$$

$$S = 3 (300 \angle 15^\circ) (15.836 \angle 99.4^\circ)^* = 14253 \angle -84.4^\circ$$

$$= 1390.8 - j14184.9 \text{ VA}$$

Also

$$S = 3 \left[|I_{AB}|^2 R_\Delta - j |I_{AB}|^2 X_\Delta \right]$$

$$= 3 \times (15.836)^2 \times 1.848 - j 3 \times (15.836)^2 \times 18.85$$



$$= 1390.8 - j14184.9 \text{ VA}$$

Q-2

The switch S is closed for a long time and then opened at $t=0$.

1- Find $V_C(0)$ and $I_L(0)$.

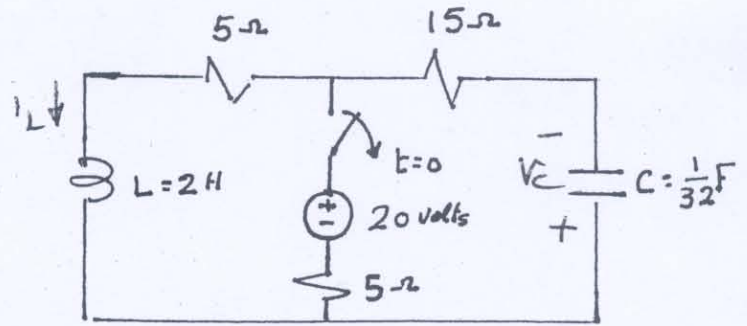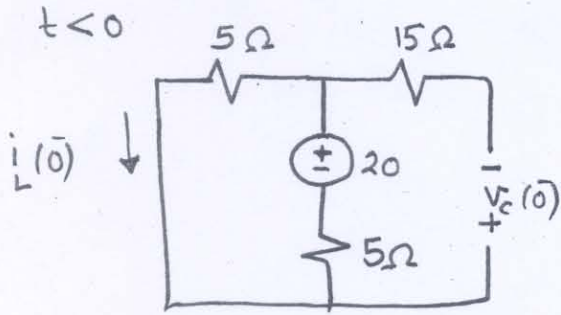2- Obtain an expression for the inductor current $I_L(t)$ for any time $t > 0$.



$$i_L(\bar{0}) = \frac{20}{10} = 2 \text{ A} \quad (1.5), \quad V_C(\bar{0}) = 10 - 20 = -10 \text{ V} \quad (1.5)$$

Series RLC circuit

$$L \frac{di_L}{dt} + V_C + R i_L = 0$$

$$L \frac{di_L}{dt} + \frac{1}{C} \int i_L dt + R i_L = 0$$

$$\therefore \frac{d^2 i_L}{dt^2} + \frac{R}{L} \frac{di_L}{dt} + \frac{1}{LC} i_L(t) = 0 \Rightarrow 2\alpha = \frac{R}{L} = 10$$

$$\omega_0^2 = \frac{1}{LC} = 16$$

$$\alpha = 5, \quad \omega_0 = 4 \Rightarrow \alpha > \omega_0 \Rightarrow \text{overdamped}$$

$$\text{Ch. Eqn: } s^2 + 10s + 16 = (s+2)(s+8) = 0$$

$$\therefore s = -2, -8 \quad (4)$$

$$i_L(t) = A_1 e^{-2t} + A_2 e^{-8t}$$

$$\frac{di_L}{dt}(t) = -2A_1 e^{-2t} - 8A_2 e^{-8t}$$

Using Initial Conditions

$$A_1 + A_2 = 2 \Rightarrow 2A_1 + 2A_2 = 4$$

$$-2A_1 - 8A_2 = -15$$

$$\therefore -6A_2 = -11 \Rightarrow A_2 = \frac{11}{6}, \quad A_1 = \frac{1}{6}$$

$$\therefore i_L(t) = \frac{1}{6} e^{-2t} + \frac{11}{6} e^{-8t}$$

$$V_L(0^+) + V_R(0^+) + V_C(0) = 0$$

$$V_L(0^+) = -40 + 10 = -30$$

$$\therefore \frac{di_L}{dt}(0^+) = \frac{-30}{2} = -15 \quad (2)$$

For the following circuit:

- Find the **state equations**
- Write them in a matrix form (**matrix state equation**)

KCL @ node ①

$$C_2 \frac{dv_{c2}}{dt} = 3i + i_L \quad \text{--- (1)}$$

KCL @ node ②


$$i_L + C_1 \frac{dv_{c1}}{dt} = i \quad \text{--- (2)}$$

KVL @ Loop I

$$Ri + v_{c1} = 0 \quad \text{--- (3)}$$

KVL @ Loop II
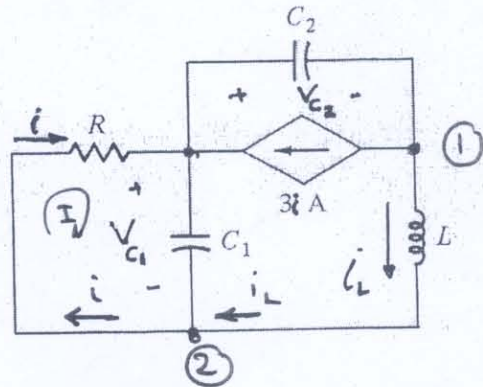
$$v_{c2} + L \frac{di_L}{dt} - v_{c1} = 0 \quad \text{--- (4)}$$



$$\frac{di_L}{dt} = \frac{1}{L} v_{c1} - \frac{1}{L} v_{c2}$$

from (3) $\Rightarrow i = -\frac{1}{R} v_{c1}$

from (2) $\Rightarrow \frac{dv_{c1}}{dt} = -\frac{1}{C_1} i_L + \frac{1}{C_1} i = -\frac{1}{C_1} i_L + \frac{1}{C_1} \left(-\frac{1}{R} v_{c1}\right)$

$$\therefore \frac{dv_{c1}}{dt} = -\frac{1}{C_1} i_L - \frac{1}{RC_1} v_{c1}$$

from (1) $\frac{dv_{c2}}{dt} = \frac{1}{C_2} i_L + \frac{3}{C_2} i$

$$\frac{dv_{c2}}{dt} = \frac{1}{C_2} i_L + \frac{3}{C_2} \left(-\frac{1}{R} v_{c1}\right) = \frac{1}{C_2} i_L - \frac{3}{RC_2} v_{c1}$$

$$\frac{d}{dt} \begin{bmatrix} i_L \\ v_{c1} \\ v_{c2} \end{bmatrix} = \begin{bmatrix} 0 & \frac{1}{L} & -\frac{1}{L} \\ -\frac{1}{C_1} & -\frac{1}{RC_1} & 0 \\ \frac{1}{C_2} & -\frac{3}{RC_2} & 0 \end{bmatrix} \begin{bmatrix} i_L \\ v_{c1} \\ v_{c2} \end{bmatrix}$$