

P 11.7

SOLUTION OF HOMEWORK 1 FOR EE205

$$Z_{ga} + Z_{la} + Z_{La} = 60 + j80\Omega$$

$$Z_{gb} + Z_{lb} + Z_{Lb} = 40 + j30\Omega$$

$$Z_{gc} + Z_{lc} + Z_{Lc} = 20 + j15\Omega$$

$$\frac{\mathbf{V}_N - 240}{60 + j80} + \frac{\mathbf{V}_N - 240/120^\circ}{40 + j30} + \frac{\mathbf{V}_N - 240/-120^\circ}{20 + j15} + \frac{\mathbf{V}_N}{10} = 0$$

Solving for \mathbf{V}_N yields

$$\mathbf{V}_N = 42.94/\underline{-156.32^\circ} \text{ V}$$

$$\mathbf{I}_o = \frac{\mathbf{V}_N}{10} = 4.29/\underline{-156.32^\circ} \text{ A}$$

$$\text{P 11.11 [a] } \mathbf{I}_{AB} = \frac{480}{60 + j45} = 6.4/\underline{-36.87^\circ} \text{ A}$$

$$\mathbf{I}_{BC} = 6.4/\underline{-156.87^\circ} \text{ A}$$


$$\mathbf{I}_{CA} = 6.4/\underline{83.13^\circ} \text{ A}$$

$$\text{[b] } \mathbf{I}_{aA} = \sqrt{3}/\underline{-30^\circ} \mathbf{I}_{AB} = 11.09/\underline{-66.87^\circ} \text{ A}$$

$$\mathbf{I}_{bB} = 11.09/\underline{173.13^\circ} \text{ A}$$

$$\mathbf{I}_{cC} = 11.09/\underline{53.13^\circ} \text{ A}$$

P 11.20 [a]

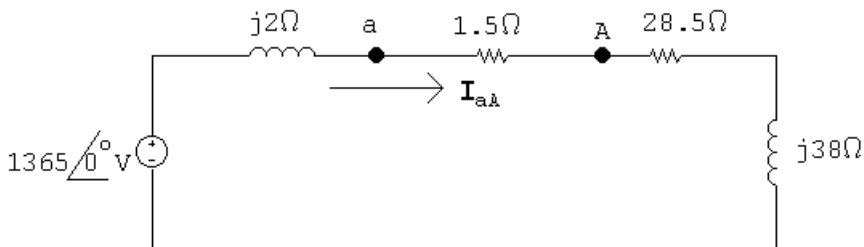

$$\mathbf{I}_{aA} = \frac{1365\angle 0^\circ}{30 + j40} = 27.3\angle -53.13^\circ \text{ A}$$

$$\mathbf{I}_{CA} = \frac{\mathbf{I}_{aA}}{\sqrt{3}}\angle 150^\circ = 15.76\angle 96.87^\circ \text{ A}$$

[b] $S_{g/\phi} = -1365\mathbf{I}_{aA}^* = -22,358.7 - j29,811.6 \text{ VA}$

$$\therefore P_{\text{developed/phase}} = 22.359 \text{ kW}$$

$$P_{\text{absorbed/phase}} = |\mathbf{I}_{aA}|^2 28.5 = 21.241 \text{ kW}$$

$$\% \text{ delivered} = \frac{21.241}{22.359}(100) = 95\%$$

P 11.21 Let p_a , p_b , and p_c represent the instantaneous power of phases a, b, and c, respectively. Then assuming a positive phase sequence, we have

$$p_a = v_{an}i_{aA} = [V_m \cos \omega t][I_m \cos(\omega t - \theta_\phi)]$$

$$p_b = v_{bn}i_{bB} = [V_m \cos(\omega t - 120^\circ)][I_m \cos(\omega t - \theta_\phi - 120^\circ)]$$

$$p_c = v_{cn}i_{cC} = [V_m \cos(\omega t + 120^\circ)][I_m \cos(\omega t - \theta_\phi + 120^\circ)]$$


The total instantaneous power is $p_T = p_a + p_b + p_c$, so

$$p_T = V_m I_m [\cos \omega t \cos(\omega t - \theta_\phi) + \cos(\omega t - 120^\circ) \cos(\omega t - \theta_\phi - 120^\circ) \\ + \cos(\omega t + 120^\circ) \cos(\omega t - \theta_\phi + 120^\circ)]$$

Now simplify using trigonometric identities. In simplifying, collect the coefficients of $\cos(\omega t - \theta_\phi)$ and $\sin(\omega t - \theta_\phi)$. We get

$$p_T = V_m I_m [\cos \omega t (1 + 2 \cos^2 120^\circ) \cos(\omega t - \theta_\phi) \\ + 2 \sin \omega t \sin^2 120^\circ \sin(\omega t - \theta_\phi)] \\ = 1.5 V_m I_m [\cos \omega t \cos(\omega t - \theta_\phi) + \sin \omega t \sin(\omega t - \theta_\phi)] \\ = 1.5 V_m I_m \cos \theta_\phi$$

P 11.24

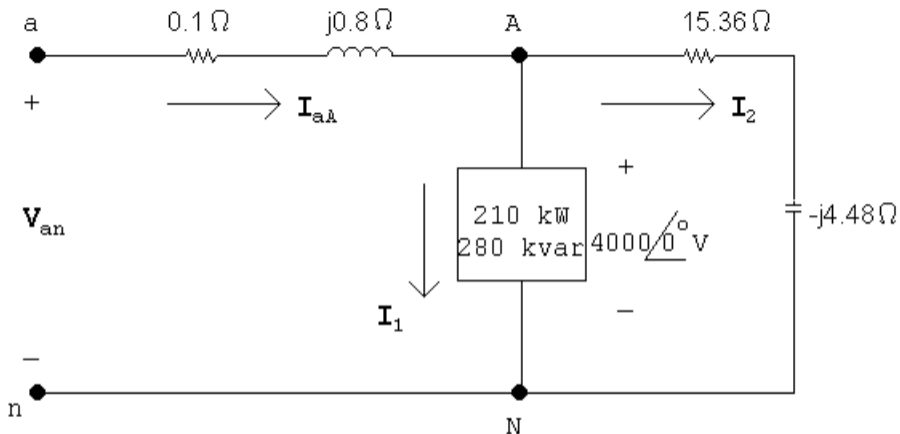

$$4000 \mathbf{I}_1^* = (210 + j280) 10^3$$

$$\mathbf{I}_1^* = \frac{210}{4} + j\frac{280}{4} = 52.5 + j70 \text{ A}$$

$$\mathbf{I}_1 = 52.5 - j70 \text{ A}$$


$$\mathbf{I}_2 = \frac{4000 \angle 0^\circ}{15.36 - j4.48} = 240 + j70 \text{ A}$$

$$\therefore \mathbf{I}_{aA} = \mathbf{I}_1 + \mathbf{I}_2 = 292.5 + j0 \text{ A}$$

$$\mathbf{V}_{an} = 4000 + j0 + 292.5(0.1 + j0.8) = 4036.04 \angle 3.32^\circ \text{ V}$$

$$|\mathbf{V}_{ab}| = \sqrt{3}|\mathbf{V}_{an}| = 6990.62 \text{ V}$$

P 11.27 [a]

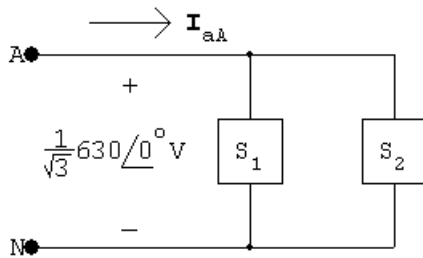

$$S_{s/\phi} = \frac{1}{3}(60)(0.96 - j0.28) \times 10^3 = 19.2 - j5.6 \text{ kVA}$$

$$S_{1/\phi} = 15 \text{ kVA}$$


$$S_{2/\phi} = S_{s/\phi} - S_{1/\phi} = 4.2 - j5.6 \text{ kVA}$$

$$\therefore \mathbf{I}_2^* = \frac{4200 - j5600}{630/\sqrt{3}} = 11.547 - j15.396 \text{ A}$$

$$\mathbf{I}_2 = 11.547 + j15.396 \text{ A}$$


$$Z_y = \frac{630\angle 0^\circ / \sqrt{3}}{\mathbf{I}_2} = 11.34 - j15.12 \Omega$$
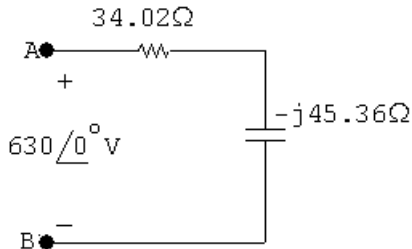
$$Z_\Delta = 3Z_y = 34.02 - j45.36 \Omega$$



$$[b] R = \frac{(630/\sqrt{3})^2}{4200} = 31.5 \Omega; \quad R_{\Delta} = 3R = 94.5 \Omega$$
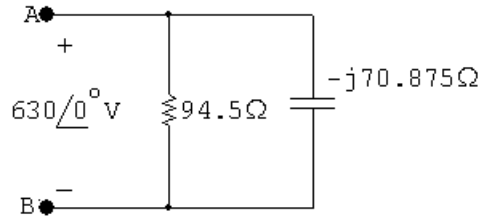
$$X_L = \frac{(630/\sqrt{3})^2}{-5600} = -23.625 \Omega; \quad X_{\Delta} = 3X_L = -70.875 \Omega$$




P 11.28 Assume a Δ -connect load (series):

$$S_{\phi} = \frac{1}{3}(96 \times 10^3)(0.8 + j0.6) = 25,600 + j19,200 \text{ VA}$$


$$Z_{\Delta\phi}^* = \frac{|480|^2}{25,600 + j19,200} = 5.76 - j4.32 \Omega$$

$$Z_{\Delta\phi} = 5.76 + j4.32 \Omega$$

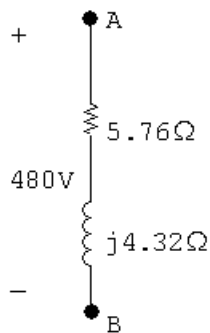

Now assume a Y-connected load (series):
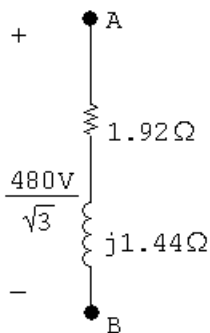
$$Z_{Y\phi} = \frac{1}{3}Z_{\Delta\phi} = 1.92 + j1.44 \Omega$$




Now assume a Δ -connected load (parallel):

$$P_\phi = \frac{|480|^2}{R_\Delta}$$

$$R_{\Delta\phi} = \frac{|480|^2}{25,600} = 9 \Omega$$

$$Q_\phi = \frac{|480|^2}{X_\Delta}$$

$$X_{\Delta\phi} = \frac{|480|^2}{19,200} = 12 \Omega$$

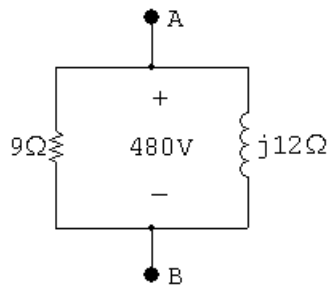

Now assume a Y-connected load (parallel):

$$R_{Y\phi} = \frac{1}{3}R_{\Delta\phi} = 3 \Omega$$

$$X_{Y\phi} = \frac{1}{3}X_{\Delta\phi} = 4 \Omega$$

