

P 1.13 [a] Looking from A to B the current i is in the direction of the voltage rise across the 12 V battery, therefore $p = vi = -12(30) = -360$ W.

Thus the power flow is from B to A, and Car A has the "dead" battery.

$$\begin{aligned} \text{[b]} \quad w &= \int_0^t p \, dx = \int_0^t 360 \, dx \\ w &= 360t = 360(1 \times 60) = 21.6 \text{ kJ} \end{aligned}$$

P 1.15 [a] $p = vi = 30e^{-500t} - 30e^{-1500t} - 40e^{-1000t} + 50e^{-2000t} - 10e^{-3000t}$
 $p(1 \text{ ms}) = 3.1 \text{ mW}$

$$\begin{aligned} \text{[b]} \quad w(t) &= \int_0^t (30e^{-500x} - 30e^{-1500x} - 40e^{-1000x} + \\ &\quad 50e^{-2000x} - 10e^{-3000x}) \, dx \\ &= 21.67 - 60e^{-500t} + 20e^{-1500t} + 40e^{-1000t} - \\ &\quad 25e^{-2000t} + 3.33e^{-3000t} \, \mu\text{J} \\ w(1 \text{ ms}) &= 1.24 \, \mu\text{J} \end{aligned}$$

P 1.21 [a] $p = vi$

$$\begin{aligned} &= 400 \times 10^3 t^2 e^{-800t} + 700t e^{-800t} + 0.25e^{-800t} \\ &= e^{-800t} [400,000t^2 + 700t + 0.25] \end{aligned}$$

$$\begin{aligned} \frac{dp}{dt} &= \{e^{-800t} [800 \times 10^3 t + 700] - 800e^{-800t} [400,000t^2 + 700t + 0.25]\} \\ &= 3,200,000t^2 - 2400t - 5 \end{aligned}$$

Therefore, $\frac{dp}{dt} = 0$ when $3,200,000t^2 - 2400t - 5 = 0$
 so p_{\max} occurs at $t = 1.68 \text{ ms}$.

$$\begin{aligned} \text{[b]} \quad p_{\max} &= [400,000(.00168)^2 + 700(.00168) + 0.25]e^{-800(.00168)} \\ &= 666 \text{ mW} \end{aligned}$$

$$\begin{aligned} \text{[c]} \quad w &= \int_0^t p \, dx \\ w &= \int_0^t 400,000x^2 e^{-800x} \, dx + \int_0^t 700x e^{-800x} \, dx + \int_0^t 0.25e^{-800x} \, dx \\ &= \frac{400,000e^{-800x}}{-512 \times 10^6} [64 \times 10^4 x^2 + 1600x + 2] \Big|_0^t + \\ &\quad \frac{700e^{-800x}}{64 \times 10^4} (-800x - 1) \Big|_0^t + 0.25 \frac{e^{-800x}}{-800} \Big|_0^t \end{aligned}$$

When $t = \infty$ all the upper limits evaluate to zero, hence

$$w = \frac{(400,000)(2)}{512 \times 10^6} + \frac{700}{64 \times 10^4} + \frac{0.25}{800} = 2.97 \text{ mJ.}$$

P 2.6 The interconnection is valid because it does not violate Kirchhoff's laws.

$$i_{\Delta} = -25 \text{ A}; \quad 6i_{\Delta} = -150 \text{ V}$$

$$-200 + 50 - (-150) = 0$$

P 2.9 The interconnection is valid because it does not violate Kirchhoff's laws:

$$p_{V\text{-sources}} = (100 - 60)(5) = 200 \text{ W.}$$

P 2.12 [a] $v_o = 8i_u + 14i_u + 18i_u = 40(20) = 800 \text{ V}$

$$800 = 10i_o$$

$$i_o = 800/10 = 80 \text{ A}$$

[b] $i_g = i_u + i_o = 20 + 80 = 100 \text{ A}$

[c] $p_g(\text{delivered}) = (100)(800) = 80,000 \text{ W} = 80 \text{ kW}$