

**Homework #1**  
**EE 201 (012)**  
**Dr. J.M.Bakhashwain**

Problem #1: Consider figure 1 shown below:

- (a) Determine the values of the currents  $i_1$  and  $i_3$  and of the voltages  $v_2$  and  $v_4$  .  
 (b) Determine the power absorbed by each element.

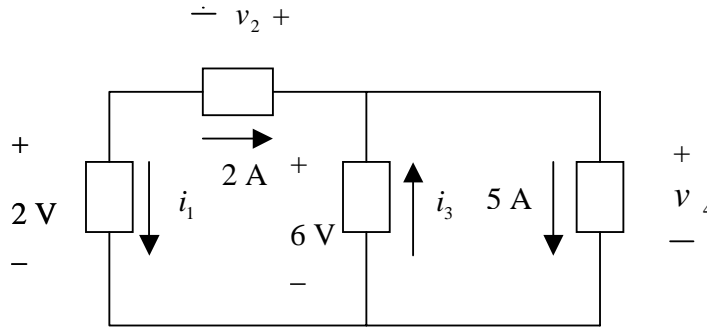


Figure 1

Answer: (a)  $i_1 = -2A$ ,  $i_3 = 3A$ ,  $v_2 = 4V$ ,  $v_4 = 6V$  .

(b)  $p_1 = -4W$ ,  $p_2 = -8W$ ,  $p_3 = -18W$ ,  $p_4 = 30W$

Problem #2: For the circuit shown in Figure 2, find the following:

- (a) The values of the currents  $i_3, i_4, i_5, i_7$ , and  $i_8$  and of the voltages  $v_1, v_2, v_6$  and  $v_9$  .  
 (b) The power associated with each element and show that total power is zero.

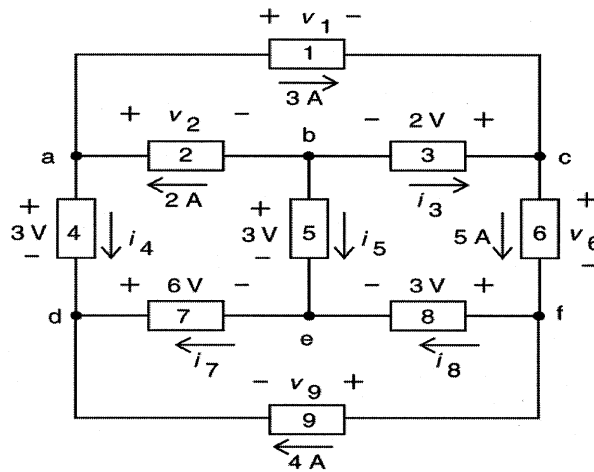


Figure 2

Answer:

(a)  $i_3 = 2A$ ,  $i_4 = -1A$ ,  $i_5 = -4A$ ,  $i_7 = -3A$ ,  $i_8 = 1A$ ,  $v_1 = 4V$ ,  $v_2 = 6V$ ,  $v_6 = 2V$  and  $v_9 = -3V$  .

(b)  $p_1 = 12W$ ,  $p_2 = -12W$ ,  $p_3 = -4W$ ,  $p_4 = -3W$ ,  $p_5 = -12W$ ,  $p_6 = 10W$ ,  $p_7 = 18W$ ,  $p_8 = 3W$ ,  $p_9 = -12W$