

Electric Circuits II

Balanced Three Phase Circuits

Lecture # 01

The material to be covered in this lecture is as follows:

- Introduction of three-phase circuit concept
- Balanced Three Phase Voltages.
- Positive Sequence Voltages
- Negative Sequence Voltages

After finishing this lecture, you should be able to:

- Identify the main components of three-phase circuit.
- Understand the role of each main components of three-phase circuit.
- Differentiate between the balanced voltages phases
- Imagine the positive and negative sequence voltages opposite direction.

## Introduction of three-phase circuit concept

- The three-phase circuit is the main circuit structure used in power system.
- The electrical power generation is accomplished through three-phase circuit.
- The three phase connection lines transmit power over long distance.
- The energy is distributed and consumed at the load level through three phase and single phase
- Generating, Transmitting, Distributing and consuming electric power is achieved through the three phase circuit
- The basic structure of a three phase system consists of voltage source, transformers, transmission line and connected loads

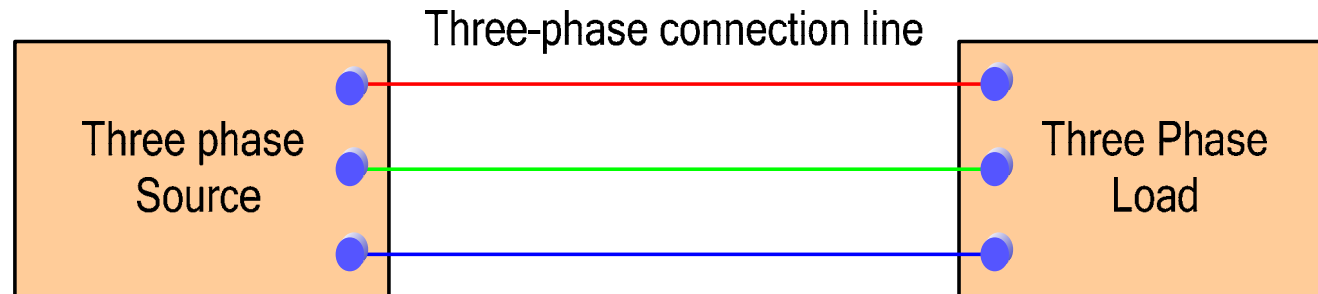


Figure 1. Three phase Circuit Components

## Balanced Three Phase Voltages

- Three sinusoidal voltages form a set of balanced voltages when they have the same amplitudes and frequency.
- These voltages are shifted in phase by  $120^\circ$  with each other.
- The standard practice is to name those phases by **a**, **b** and **c** and use phase **a** as reference.
- These voltages represent **phase a voltage**, **phase b voltage** and **phase c voltage**.

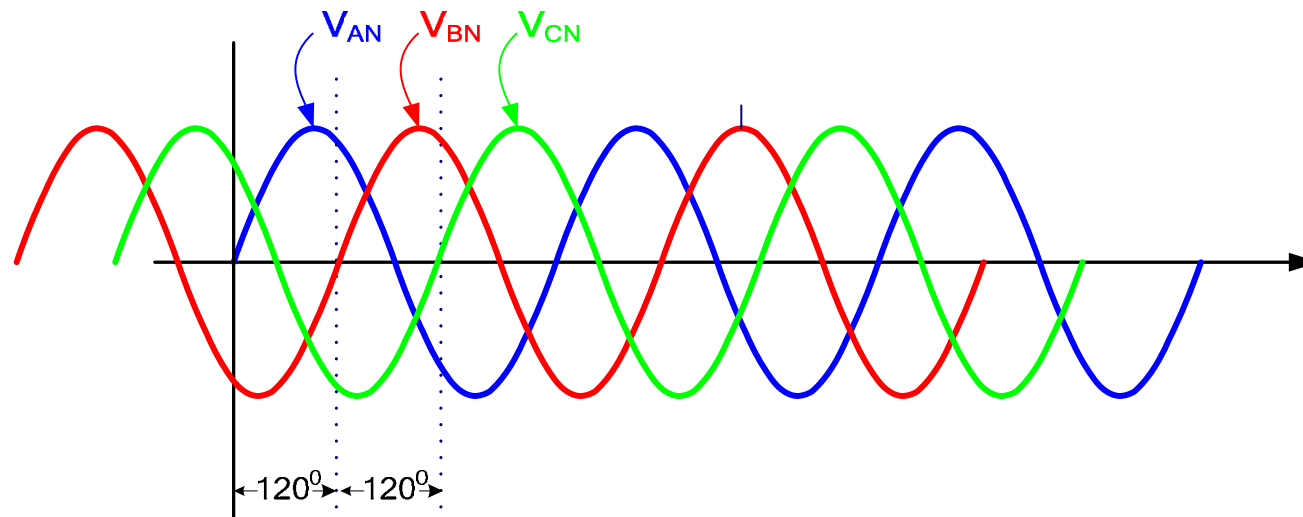


Figure 2. Phase Voltages of Balanced Three Phase source.

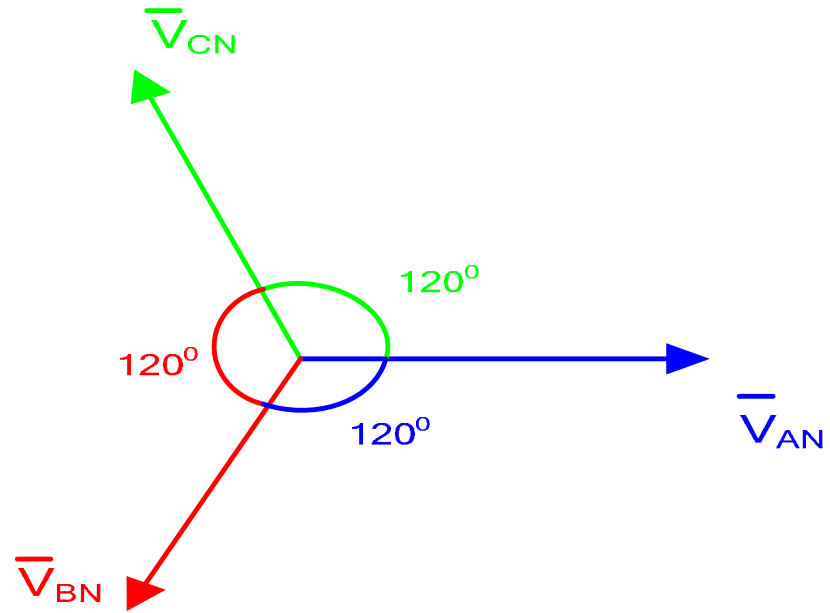


Figure 3. Phasor Diagram for Balanced Three Phase Voltages

## Positive Sequence Voltages

- When phase **b** voltage lags the reference phase **a** voltage by  $120^\circ$  and consequently phase **c** voltage must lead phase **a** voltage by  $120^\circ$ .
- The above relation between phases is known as **positive sequence** or **abc**.

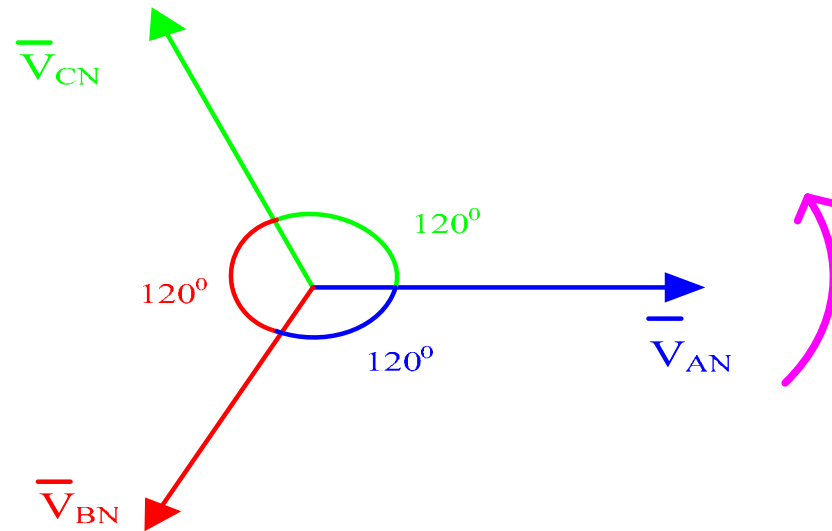


Figure 4. Phasor Diagram of Balanced Three Phase Voltages (abc) sequence

- In phasor notation we represent the set of balanced positive sequence voltage as:

$$V_a = V \angle 0^\circ$$

$$V_b = V \angle -120^\circ$$

$$V_c = V \angle +120^\circ$$



## Negative Sequence Voltages

- When phase **b** voltage leads the reference phase **a** voltage by  $120^\circ$  and consequently phase **c** voltage must lag phase **a** voltage by  $120^\circ$ .
- The above relation between phases is known as **negative sequence** or **acb**.

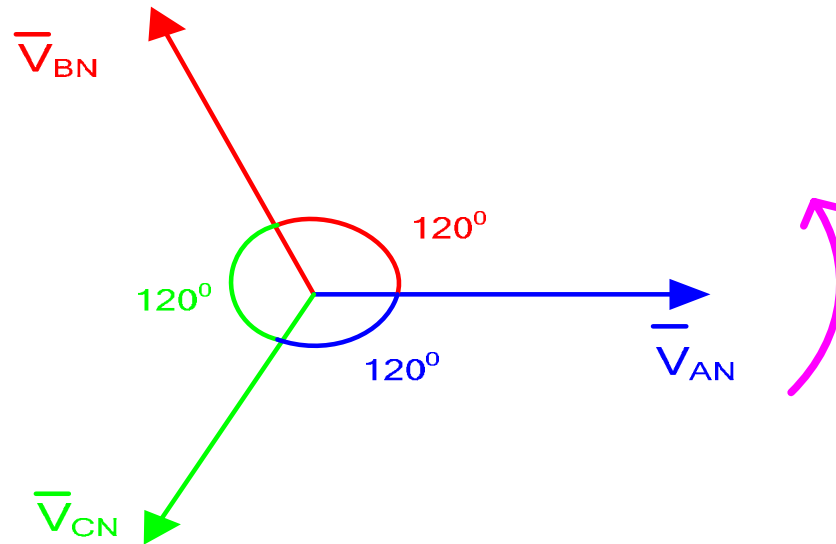


Figure 5. Phasor Diagram of Balanced Three Phase Voltages (acb) sequence

- In phasor notation we represent the set of balanced negative sequence voltage as:

$$V_a = V \angle 0^\circ$$

$$V_b = V \angle +120^\circ$$

$$V_c = V \angle -120^\circ$$

- An important Characteristic of a positive or negative sequence set of balanced voltages is that the sum the phasor voltages is equal to zero

$$V_a + V_b + V_c = 0$$

- As a consequence the sum the related instantaneous voltages is equal to zero

$$v_a + v_b + v_c = 0$$

- If the phase sequence is known and one of the voltages of the balanced set is known then the entire set becomes known.

**Example:**

- Define the phase sequence for this first set voltages

$$v_a = 208 \cos(\omega t + 27^\circ) V .$$

$$v_b = 208 \cos(\omega t + 147^\circ) V .$$

$$v_c = 208 \cos(\omega t - 93^\circ) V .$$

- The relevant phsors are :

$$V_a = 208 \angle 27^\circ V . \quad V_b = 208 \angle +147^\circ V . \quad V_c = 208 \angle -93^\circ V .$$

- Therefore the sequence is **acb**

- Define the phase sequence for this second set voltages

$$v_a = 4160 \cos(\omega t - 18^\circ) V.$$

$$v_b = 4160 \cos(\omega t - 138^\circ) V.$$

$$v_c = 4160 \cos(\omega t + 102^\circ) V.$$

- The relevant phsors are :

$$V_a = 4160 \angle -18^\circ V. \quad V_b = 4160 \angle -138^\circ V. \quad V_c = 4160 \angle +102^\circ V.$$

- Therefore the sequence is **abc**

## Self Test:

Which options are true for a set of three sinusoidal balanced voltages?

- a) Three sinusoidal voltages have the same amplitudes and different frequency.
- b) Two sinusoidal voltages are shifted in phase by  $120^\circ$  from the reference voltage
- c) The three voltages are shifted in phase by  $120^\circ$  with each other
- d) In a positive sequence phase b is lagging on phase a by  $240^\circ$ .
- e) In a negative sequence phase b is leading on phase a by  $120^\circ$ .

answer: c, and e