

EE205-052

Electric Circuits II

Balanced Three Phase Circuits

Lecture # 03

EE205-052

The material to be covered in this lecture is as follows:

- ❖ Transformation from Delta to Why.
- ❖ Transformation from Why to Delta.
- ❖ The single-phase equivalent circuit.
- ❖ The line and phase current quantities for a Delta circuit.
- ❖ Complete Analysis of Y- Δ circuit.

After finishing this lecture, you should be able to:

- ❖ Transform the three-phase circuit Y to Δ and vice versa.
- ❖ Extract the single-phase equivalent circuit for Y- Δ three-phase circuit.
- ❖ Deduce the line and phase current quantities for Δ connection.
- ❖ Identify the difference between delta and why currents and voltage relations.
- ❖ Conduct a complete analysis for Y- Δ circuit.

Transformation from Delta to Wye

- Starting from a Delta connection to reach Wye Connection

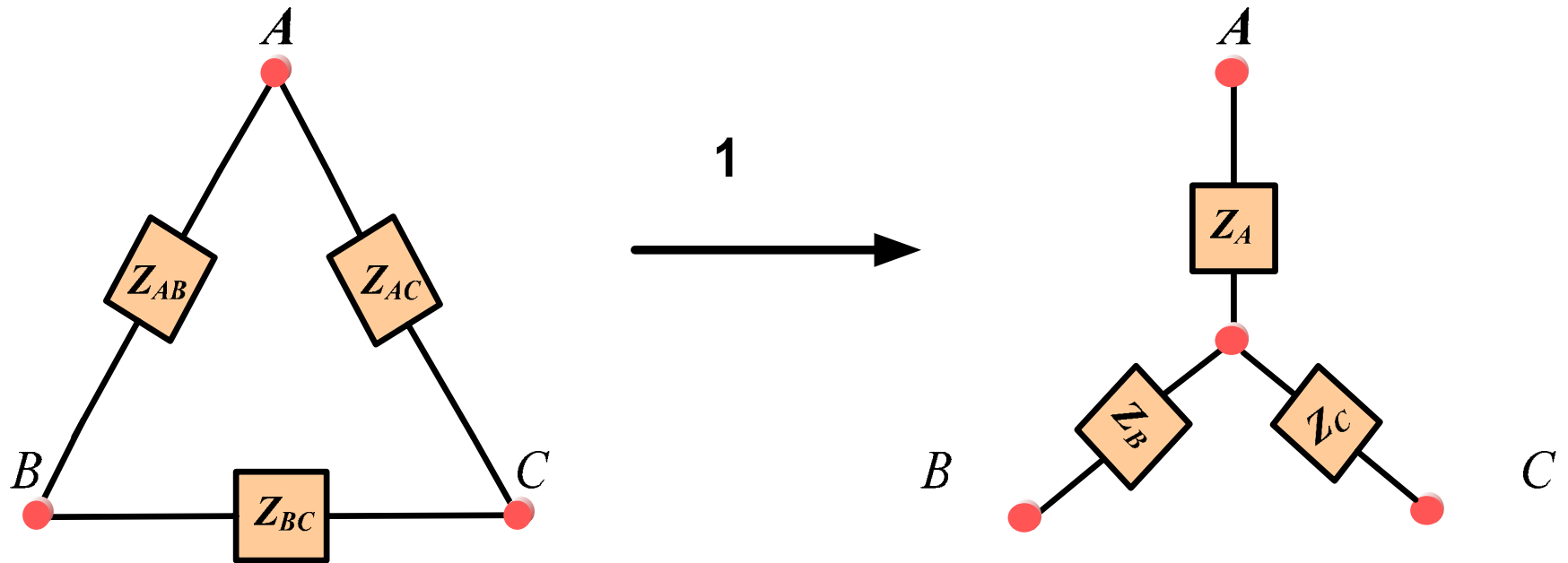


Figure 13 Delta to Wye Transformation circuits

Transformation from Delta to Why (Cont)

$$Z_A = \frac{Z_{AB} \cdot Z_{AC}}{Z_{AB} + Z_{BC} + Z_{AC}}$$

$$Z_B = \frac{Z_{AB} \cdot Z_{BC}}{Z_{AB} + Z_{BC} + Z_{AC}}$$

$$Z_C = \frac{Z_{AC} \cdot Z_{BC}}{Z_{AB} + Z_{BC} + Z_{AC}}$$

❖ In case where

$$Z_{AB} = Z_{AC} = Z_{BC} = Z$$

❖ Then

$$Z_A = \frac{Z^2}{3Z} = \frac{1}{3}Z$$

❖ So we can deduce that

$$Z_Y = \frac{1}{3}Z_{\Delta}$$

Transformation from Why to Delta

- Starting from a Why connection to reach Delta Connection

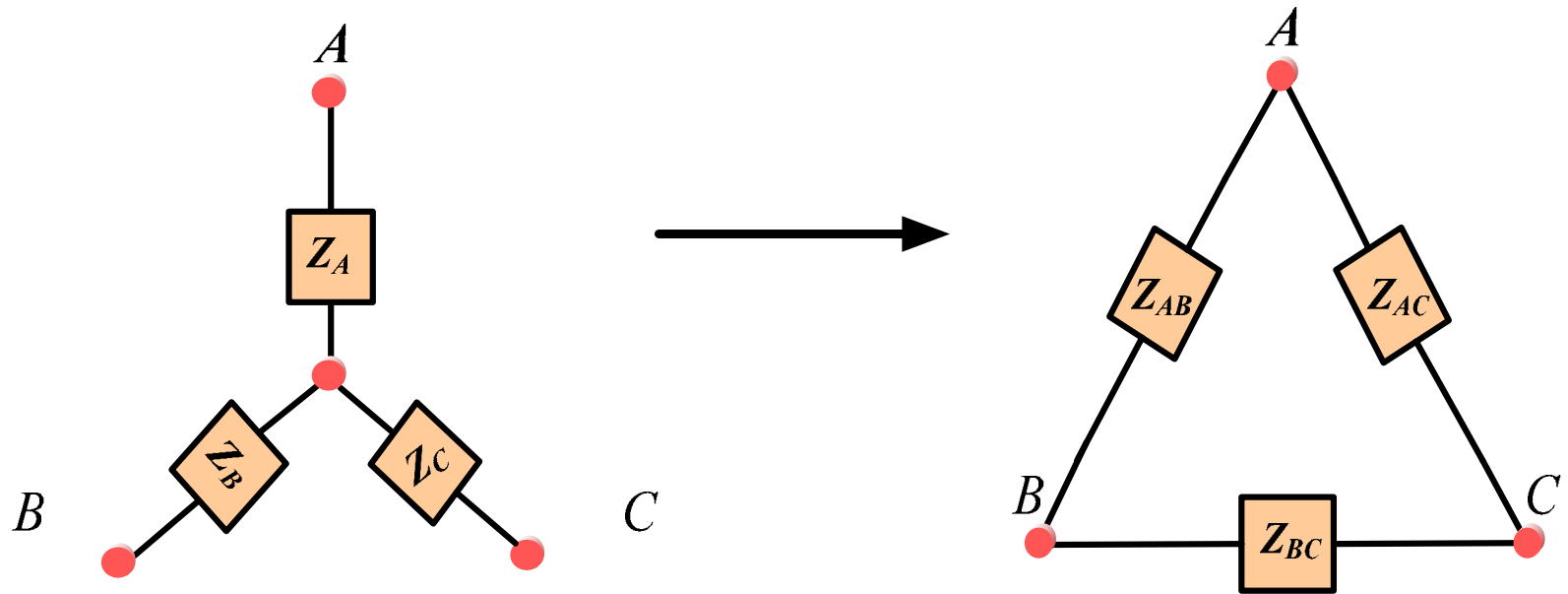


Figure 14 Wye to Delta to Transformation circuits

Transformation from Why to Delta (Cont)

$$Z_{AB} = \frac{Z_A Z_B + Z_B Z_C + Z_A Z_C}{Z_C}$$

$$Z_{BC} = \frac{Z_A Z_B + Z_B Z_C + Z_A Z_C}{Z_A}$$

$$Z_{AC} = \frac{Z_A Z_B + Z_B Z_C + Z_A Z_C}{Z_B}$$

❖ In case where

$$Z_A = Z_B = Z_C = Z$$

❖ Then

$$Z_{AB} = \frac{3Z^2}{Z} = 3Z$$

❖ So we can deduce that

$$Z_{AB} = \frac{3Z^2}{Z} = 3Z_Y$$

The single-phase equivalent circuit

- ❖ The source is Y connected and the load is Delta connected and balanced. So

$$Z_{AB} = Z_{BC} = Z_{CA} = Z_{\Delta}$$

- ❖ the conversion of or transformation of Δ to Y transformation gives

$$Z_Y = \frac{Z_{\Delta}}{3}$$

- ❖ After replacing the delta connected load by the equivalent Y connected load, the circuit can be analyzed by the equivalent **single phase equivalent circuit**.
- ❖ After replacing the delta connected load by the equivalent Y connected load, the circuit can be analyzed by the equivalent **single phase equivalent circuit**.

The single-phase equivalent circuit (cont)

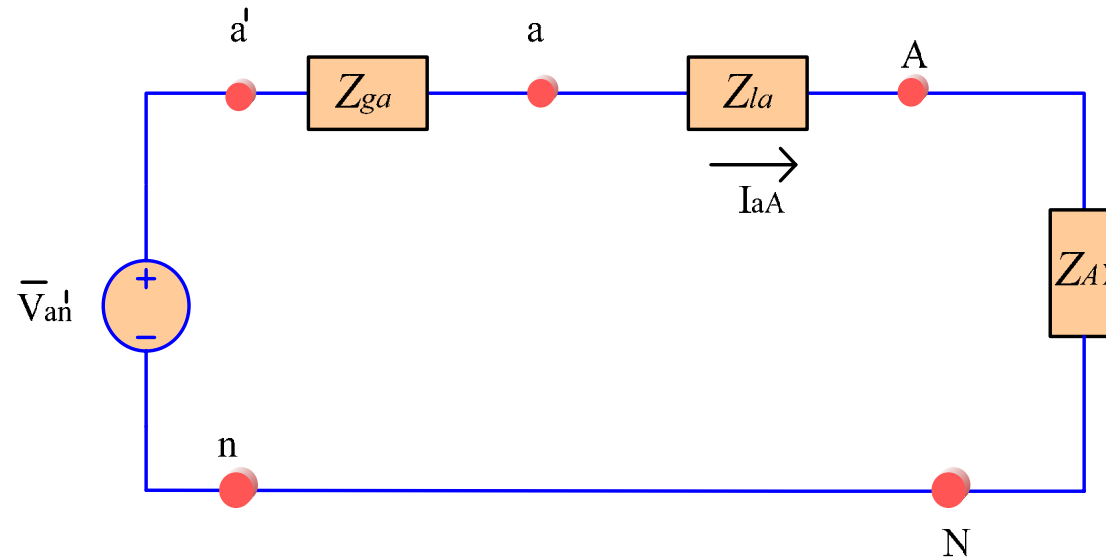


Figure 15 Delta to Wye Load Transformation Single Phase Equivalent Circuit

- ❖ This circuit is used to calculate phase voltages, phase currents, line voltages and line current.
- ❖ Generators phase and line voltages, in each of the original delta load.

The line and phase current quantities for a Delta circuit

❖ When positive phase sequence is assumed and $I\phi$ is taken for the phase reference current.

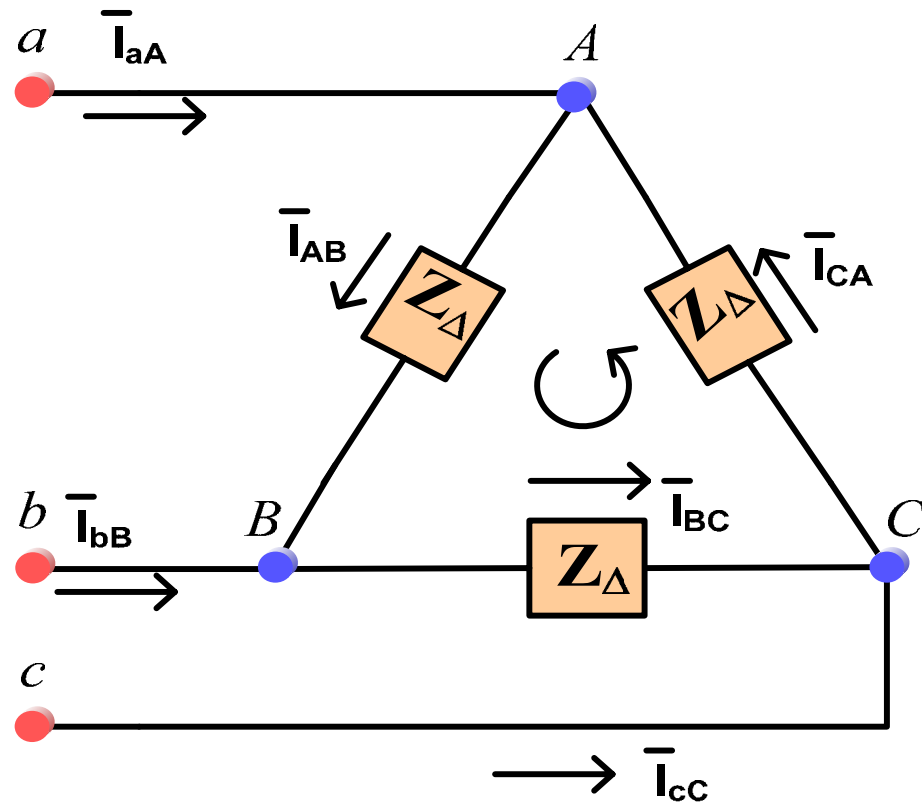


Figure 16 Delta balanced load connections

The line and phase current quantities for a Delta circuit (cont)

- ❖ Then

$$\bar{I}_{AB} = I_{\phi} \angle 0^{\circ} \text{ A}$$

$$\bar{I}_{BC} = I_{\phi} \angle -120^{\circ} \text{ A}$$

$$\bar{I}_{CA} = I_{\phi} \angle +120^{\circ} \text{ A}$$
- ❖ By KCL at node A we get

$$\bar{I}_{aA} = \bar{I}_{AB} - \bar{I}_{CA} = I_{\phi} \angle 0^{\circ} - I_{\phi} \angle +120^{\circ} = \sqrt{3} I_{\phi} \angle -30^{\circ} = \sqrt{3} \angle -30^{\circ} \bar{I}_{AB}$$
- ❖ By KCL at node B we get

$$\bar{I}_{cB} = \bar{I}_{BC} - \bar{I}_{AB} = \sqrt{3} \angle -30^{\circ} \bar{I}_{BC} = \sqrt{3} I_{\phi} \angle -150^{\circ}$$
- ❖ By KCL at node C we get

$$\bar{I}_{cC} = \bar{I}_{CA} - \bar{I}_{BC} = \sqrt{3} \angle -30^{\circ} \bar{I}_{CA} = \sqrt{3} I_{\phi} \angle 90^{\circ} \text{ A}$$

The line and phase current quantities for a Delta circuit (cont)

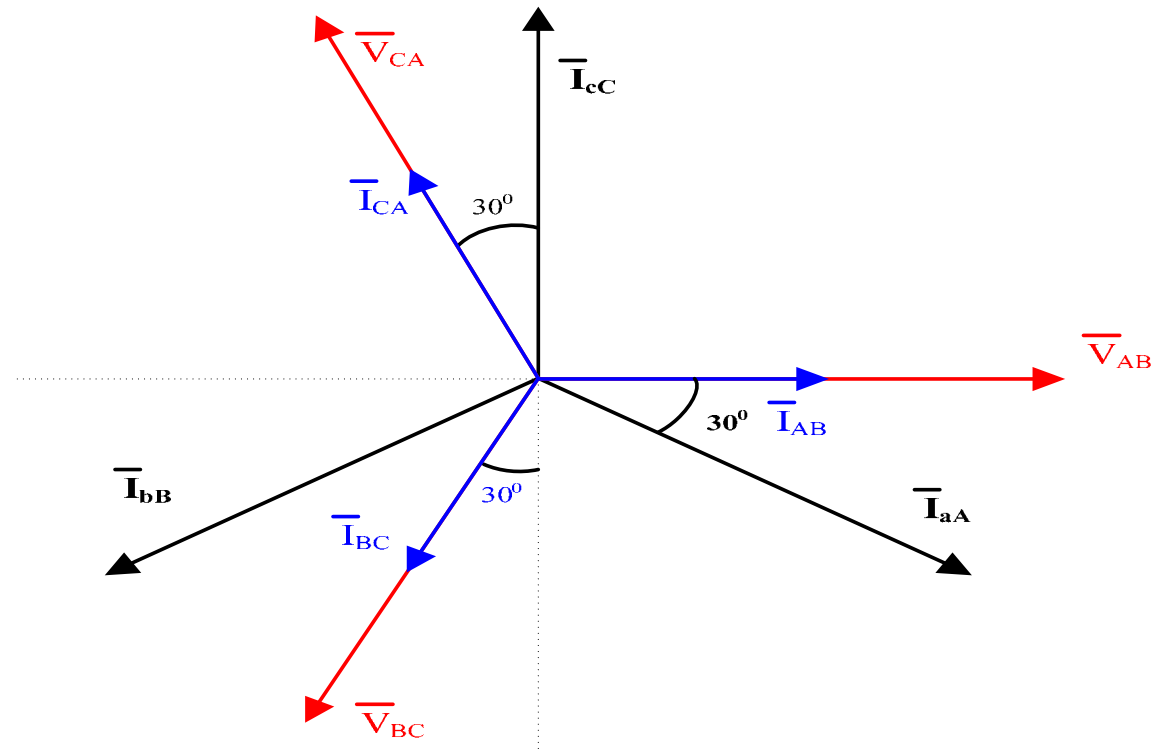


Figure 17 Phasor Diagram for Delta balanced currents and voltages

Complete Analysis of Y- Δ circuit.

- ❖ The analysis is conducted through the following application example.

Example:

- ❖ Y connected source load feeds Δ connected load through a distribution line having impedance of

$$0.3 + j0.9\Omega/\phi, Z_{\Delta} = 118.5 + j85.8\Omega/\phi \text{ et } V_{an} = 120\angle 0V/\phi \text{ is taken as reference.}$$

- ❖ The internal per phase impedance is $0.2 + j0.5\Omega/\phi$.

- Construct the single-phase equivalent circuit.

$$Z_y = \frac{Z_{\Delta}}{3} = (118.5 + j85.8)/3 = 39.5 + j28.6 = 146.3\angle 35.9/3$$

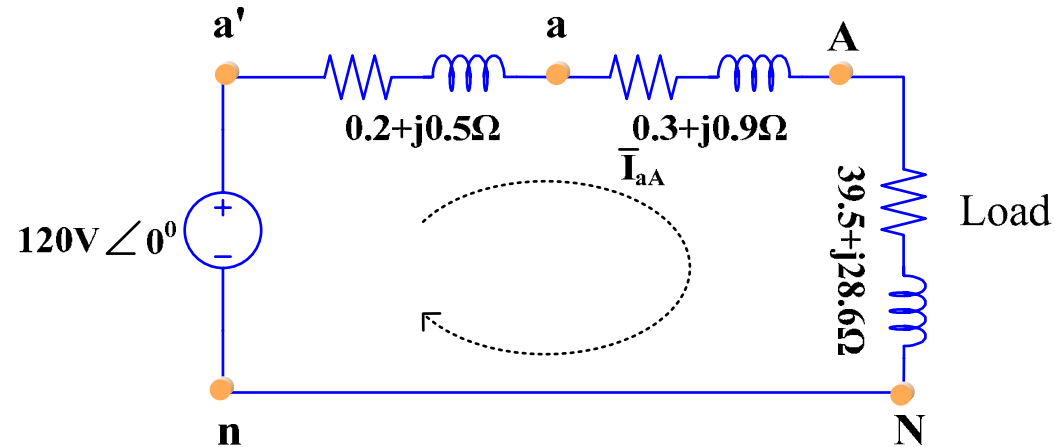


Figure 18 Single Phase Equivalent Converted Circuit .

- b) Calculate the line currents $\bar{I}_{aA}, \bar{I}_{bB}, \bar{I}_{cC}$.

$$\bar{I}_{aA} = \frac{120 \angle 0^\circ}{(0.2 + 0.3 + 39.5) + j(0.5 + 0.9 + 28.6)} = \frac{120 \angle 0^\circ}{40 + j30} \text{ A}$$

$$\bar{I}_{aA} = 2.4 \angle -36.87^\circ \text{ A}, \bar{I}_{bB} = 2.4 \angle -156.87^\circ \text{ A}, \bar{I}_{cC} = 2.4 \angle -83.13^\circ \text{ A}$$

Example(cont)

c) Calculate the phase voltages at the load terminals.

$$\bar{V}_{AN} = (39.5 + j28.6)(2.4 \angle -36.87^\circ) = 117.04 \angle -0.96^\circ \text{V}, \quad \bar{V}_{BN} = 117.04 \angle -120.96^\circ \text{V}$$

$$\bar{V}_{CN} = 117.04 \angle -240.96^\circ \text{V}$$

$$\bar{V}_{AB} = \sqrt{3} \angle 30^\circ \bar{V}_{AN} = 202.72 \angle 29.04^\circ \text{V}$$

$$\bar{V}_{BC} = 202.72 \angle -90.96^\circ \text{V}, \quad \bar{V}_{CA} = 202.72 \angle 149.04^\circ \text{V}$$

d) Calculate the phase current of the load.

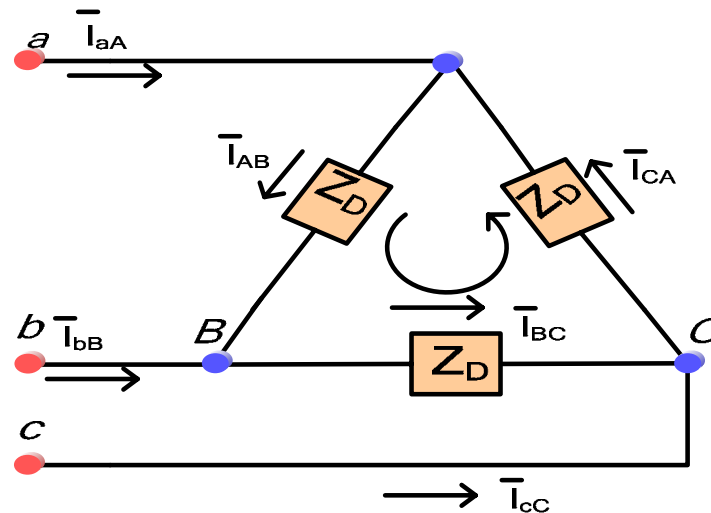


Figure 19 Three Phase Delta Connected Load.

Example(cont)

$$\bar{I}_{aA} = 1/\sqrt{3} \angle 30^\circ \bar{I}_{AB} = 1.39 \angle -6.87^\circ \text{ A}$$

$$\bar{I}_{BC} = 1.39 \angle -6.87 - 120^\circ = 1.39 \angle -126.87^\circ \text{ A}$$

$$\bar{I}_{CA} = 1.39 \angle 113.13^\circ \text{ A}$$

In an other way

$$\bar{I}_{AB} = V_{AB} / Z_{\phi\Delta} = \frac{202.72 \angle 29.04}{118.5 + j85.8} = 1.39 \angle -6.87^\circ \text{ A}$$

e) Calculate the line voltage at the source terminals.

$$V_{an} = (Z_l + Z_y) \bar{I}_{aA} = (39.8 + j29.5)(2.4 \angle -36.87^\circ)$$

$$V_{an} = 118.90 \angle -0.32^\circ \text{ V}, V_{bn} = 118.9 \angle -0.32 - 120^\circ$$

$$\bar{V}_{an} = 118.90 \angle -120.32 - 120^\circ = \bar{V}_{cn} = 118.9 \angle -240.32^\circ \text{ V}$$

$$\bar{V}_{ab} = \sqrt{3} \angle 30^\circ \bar{V}_{an} = 205.94 \angle 29.68^\circ \text{ V}$$

$$\bar{V}_{bc} = 205.94 \angle -90.32^\circ \text{ V}, \bar{V}_{ca} = 205.94 \angle 149.68^\circ \text{ V}$$

Self test:

To analyse a Y- Δ connected balanced circuit we have to ?

- a) Include the Delta phase load without any changes in the single-phase equivalent circuit.
- b) Include the transformed Delta to Y phase load in the single-phase equivalent circuit.
- c) Include three times the Delta phase load value in the single phase equivalent circuit.

Answer is b)

Self test:

Which options are true for a set of balanced delta variables?

- a) Each phase voltage leads its corresponding line voltage by 30° .
- b) Each phase current leads its corresponding line current by 30° .
- c) Each phase current is higher in magnitude than its corresponding line current.
- d) For the single-phase equivalent circuit, the line load voltage has to be used between A and N.
- f) Each line voltage magnitude is equal each phase voltage magnitude.

Answer b) and f)