



King Fahd University of Petroleum & Minerals
Department of Electrical Engineering
EE-205 Electric Circuits II


Exam: II
Date : May. 21, 2005
Place: Bldg. 6 Room 125
Time: 5:15 – 6:40 pm

Student Name	:	
Student ID	:	Sec. No.
Instructor	:	Dr. Abdelmalek ZIDOURI

Problem I	Problem II	Problem III	Total/20

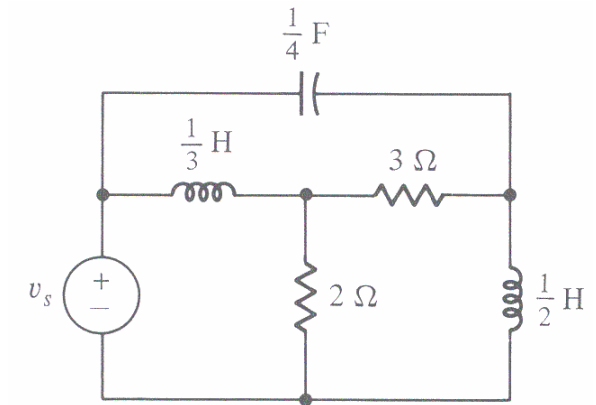Problem I (7pnts):



Write the matrix state equation for the circuit below.



Problem II (7pnts):

a) Find the resonance frequency for each of the circuits shown below.

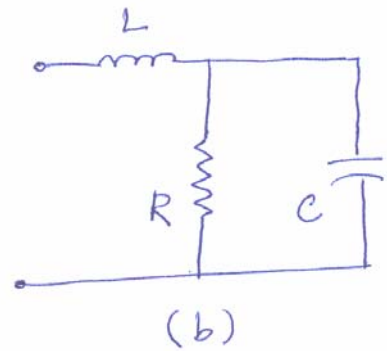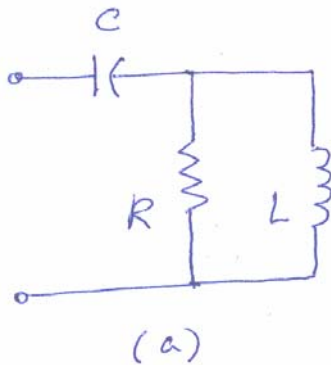c) Find the quality factor for the circuit in (a) given that $R = 5 \Omega$, $L = 2 \text{ H}$, $C = \frac{1}{5} \text{ F}$



Problem III (6pnts):

Draw the pole-zero plot of $\mathbf{H}(s) = \mathbf{V}_2/\mathbf{V}_1$ for the circuit below, given that: $R_1 = 8 \Omega$, $R_2 = 4 \Omega$, $L = 2 \text{ H}$,

$C = \frac{1}{8} \text{ F}$

