

EE 205 Dr. A. Zidouri

Electric Circuits II

The Transformer

Lecture #33

EE 205 Dr. A. Zidouri

The material to be covered in this lecture is as follows:

- Introduction to Transformers
- Analysis of a Linear Transformer Circuit
- Reflected Impedance

EE 205 Dr. A. Zidouri

After finishing this lecture you should be able to:

- Construct the frequency domain equivalent circuit of a transformer
- Analyze a linear transformer circuit
- Calculate the reflected impedance into the primary
- Calculate the scaling factor for the reflected impedance

Introduction

- A Transformer is a magnetic device that takes advantage of the phenomenon of mutual inductance.
- A Transformer is generally a four-terminal device comprising two (or more) magnetically coupled coils.
- A Transformer may also be regarded as one whose flux is proportional to the currents in its windings.

Consider the following general circuit model for a transformer used to connect a load to a source.

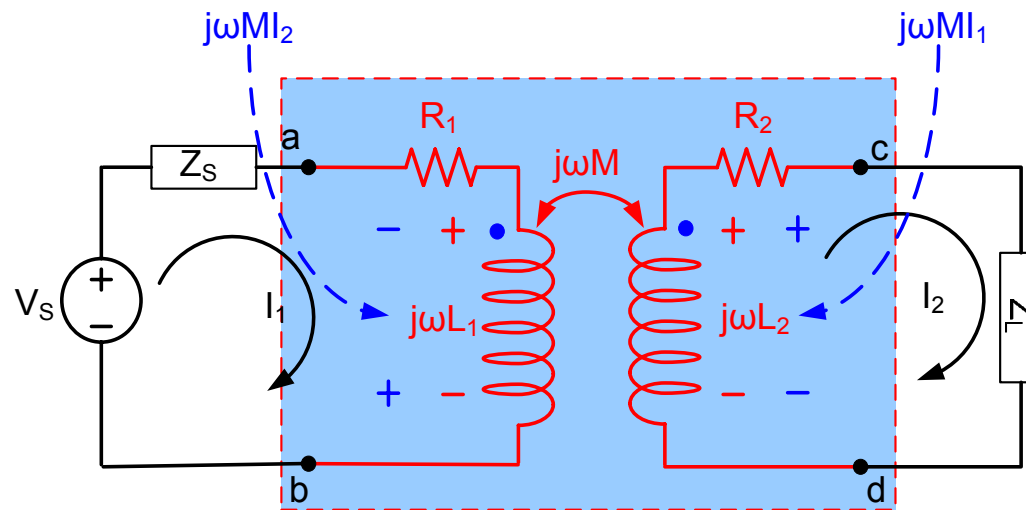


Fig.33-1 Frequency-domain circuit model for a Transformer

Introduction (cont)

Terminology

- The transformer winding connected to the source is the primary winding.
- The transformer winding connected to the load is the secondary winding.

Where:

- ✚ R_1 → The resistance of the primary winding
- ✚ R_2 → The resistance of the secondary winding
- ✚ L_1 → The self inductance of the primary winding
- ✚ L_2 → The self inductance of the secondary winding
- ✚ M → The mutual inductance
- ✚ V_S → The internal Voltage of the sinusoidal source
- ✚ Z_S → The internal impedance of the sinusoidal source
- ✚ Z_L → The Load impedance.

Analysis of a linear transformer circuit

The analysis of the circuit consists of finding I_1 and I_2 as a function of circuit parameters: R_1 , R_2 , L_1 , L_2 , M , V_S , Z_S , Z_L and ω .

$$\text{Mesh 1} \quad V_S = (Z_S + R_1 + j\omega L_1)I_1 - j\omega M I_2 \quad (33-1)$$

$$\text{Mesh 2} \quad 0 = -j\omega M I_1 + (Z_L + R_2 + j\omega L_2)I_2 \quad (33-2)$$

For simplification, let

$$Z_{11} = R_1 + j\omega L_1 + Z_S \quad \text{Self impedance of the primary} \quad (33-3)$$

$$Z_{22} = R_2 + j\omega L_2 + Z_L \quad \text{Self impedance of the secondary} \quad (33-4)$$

Thus,

$$V_S = Z_{11}I_1 - j\omega M I_2 \quad (33-5)$$

$$0 = -j\omega M I_1 + Z_{22}I_2 \quad (33-6)$$

$$\text{From (33-6) yields:} \quad I_2 = \frac{j\omega M}{Z_{22}} I_1 \quad (33-7)$$

Substitute in (33-5) yields

$$\mathbf{V}_S = \frac{\mathbf{Z}_{11}\mathbf{Z}_{22} + \omega^2 M^2}{\mathbf{Z}_{22}} \mathbf{I}_1 = \left(\mathbf{Z}_{11} + \frac{\omega^2 M^2}{\mathbf{Z}_{22}} \right) \mathbf{I}_1 \quad (33-8)$$

Therefore

$$\mathbf{I}_1 = \frac{\mathbf{Z}_{22}}{\mathbf{Z}_{11}\mathbf{Z}_{22} + \omega^2 M^2} \mathbf{V}_S \quad \text{Primary Current} \quad (33-9)$$

$$\mathbf{I}_2 = \frac{j\omega M}{\mathbf{Z}_{11}\mathbf{Z}_{22} + \omega^2 M^2} \mathbf{V}_S = \frac{j\omega M}{\mathbf{Z}_{22}} \mathbf{I}_1 \quad \text{Secondary Current} \quad (33-10)$$

The impedance at the terminals of the source is:

$\mathbf{Z}_{\text{int}} - \mathbf{Z}_S$ so,

$$\mathbf{Z}_{ab} = \mathbf{Z}_{11} + \frac{\omega^2 M^2}{\mathbf{Z}_{22}} - \mathbf{Z}_S = R_1 + j\omega L_1 + \frac{\omega^2 M^2}{R_2 + j\omega L_2 + \mathbf{Z}_L} \quad \text{Impedance looking into the primary} \quad (33-11)$$

Note: The impedance \mathbf{Z}_{ab} is independent of the magnetic polarity of the transformer.

Reflected Impedance

The quantity $\mathbf{Z}_r = \frac{\omega^2 M^2}{R_2 + j\omega L_2 + \mathbf{Z}_L}$ is called the **Reflected Impedance** (33-12)

This is due solely to the existence of mutual inductance.

To consider reflected impedance in more detail, we express the load impedance in rectangular form:

$$\mathbf{Z}_L = R_L + jX_L \quad (33-13)$$

where X_L is positive for inductive load and negative for capacitive load.

\mathbf{Z}_r in rectangular form will be:

$$\mathbf{z}_r = \frac{\omega^2 M^2 [(R_L + R_2) - j(\omega L_2 + X_L)]}{(R_L + R_2)^2 + (\omega L_2 + X_L)^2} \quad (33-14)$$

$$\mathbf{z}_r = \frac{\omega^2 M^2}{|\mathbf{Z}_{22}|^2} [(R_L + R_2) - j(\omega L_2 + X_L)] = \frac{\omega^2 M^2}{|\mathbf{Z}_{22}|^2} \mathbf{Z}_{22}^* \quad (33-15)$$

Therefore the Linear Transformer reflects **the conjugate** of the **self-impedance of the secondary** circuit $(\mathbf{Z}_{22})^*$ into the primary circuit.

The coefficient $\frac{\omega^2 M^2}{|\mathbf{Z}_{22}|^2}$ is called the **scaling factor** of the reflected impedance.

Example 33-1

Calculate the reflected impedance, the scaling factor, the primary and secondary currents for the Circuit of Fig.33-2:

Parameters of the transformer

$$R_2 = 40 \Omega, \quad X_1 = 400 \Omega,$$

$$R_L = 360 \Omega, \quad X_L = 200 \Omega,$$

$$R_1 = 100 \Omega, \quad X_2 = 100 \Omega, \quad \omega M = 80 \Omega,$$

$$Z_s = 184 + j0 \Omega, \quad V_s = \frac{245}{\sqrt{2}} \angle 0^\circ \text{ V}$$

$$M = k\sqrt{L_1 L_2}$$

$$M = 0.4\sqrt{(0.125)(0.5)} = 0.1 \Rightarrow \omega = 800 \text{ rad/s}$$

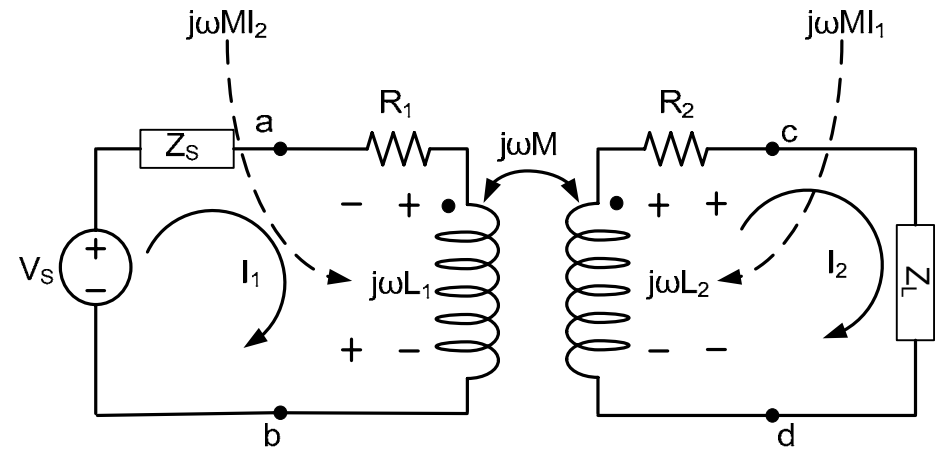


Fig.33-2 Circuit for Example 33-1

The reflected impedance:

Substituting equation (33-4) in equation (33-15) we get

$$Z_{22} = R_2 + j\omega L_2 + Z_L = (R_L + R_2) + j(X_2 + X_L) = 400 + j300$$

$$|Z_{22}| = |400 + j300| = 500 \Omega \quad \text{and} \quad \mathbf{z}_r = \frac{\omega^2 M^2}{|Z_{22}|^2} [(R_L + R_2) - j(\omega L_2 + X_L)]$$

Example 33-1(cont)

therefore

$$Z_r = \frac{80^2}{500^2} [400 - j300] = 1.6^2 \times 4 - j1.6^2 \times 3 = 10.24 - j7.68 \Omega$$

The scaling factor by which Z_{22}^* is reflected is $\frac{80^2}{500^2} = \frac{64}{2500} = 0.0256$

The primary current I_1 is given by equation 33-9 as:

$$I_1 = \frac{Z_{22}}{Z_{11}Z_{22} + \omega^2 M^2} V_s$$

where $Z_{11} = R_1 + j\omega L_1 + Z_s = 184 + 100 + j400 = 284 + j400 \Omega$ and $Z_{22} = 400 + j300$

$$\begin{aligned} \text{Therefore } I_1 &= \frac{400 + j300}{(284 + j400)(400 + j300) + 80^2} \frac{245}{\sqrt{2}} \angle 0^\circ \\ &= \frac{500 \angle 36.87^\circ}{245280 \angle 91.53^\circ + 6400} \frac{245}{\sqrt{2}} \angle 0^\circ \\ &= \frac{0.5}{\sqrt{2}} \angle -53.13^\circ \text{ A} \end{aligned}$$

In the time domain, $i_1 = 0.5 \cos(800t - 53.13^\circ) \text{ A}$

Example 33-1(cont)

The secondary current I_2 is given by equation 33-10 as:

$$I_2 = \frac{j\omega M}{Z_{22}} I_1$$

where $Z_{22} = 400 + j300$ and $\omega M = 80$

$$\text{Therefore } I_2 = \frac{80 \angle 90^\circ}{500 \angle 36.87^\circ} \frac{0.5}{\sqrt{2}} \angle -53.13^\circ$$

$$I_2 = \frac{80}{500\sqrt{2}} = \frac{0.08}{\sqrt{2}} \text{ A}$$

In the time domain, $i_2 = 0.08 \cos 800t \text{ A}$

Self Test:

For the following circuit of Fig.33-3

- ❖ What is the self-impedance of the primary?
a) $500+j100$
b) $700+j3700$
c) $200+j3600$
d) $1000+j4400$

Correct answer b

- ❖ What is the self-impedance of the secondary?
a) $900-j3700$
b) $800-j2500$
c) $900-j900$
d) $100+j1600$

Correct answer c

- ❖ What is the impedance reflected into the primary?
a) $800-j2500$
b) $100+j1600$
c) $1000+j4400$
d) $800+j800$

Correct answer d

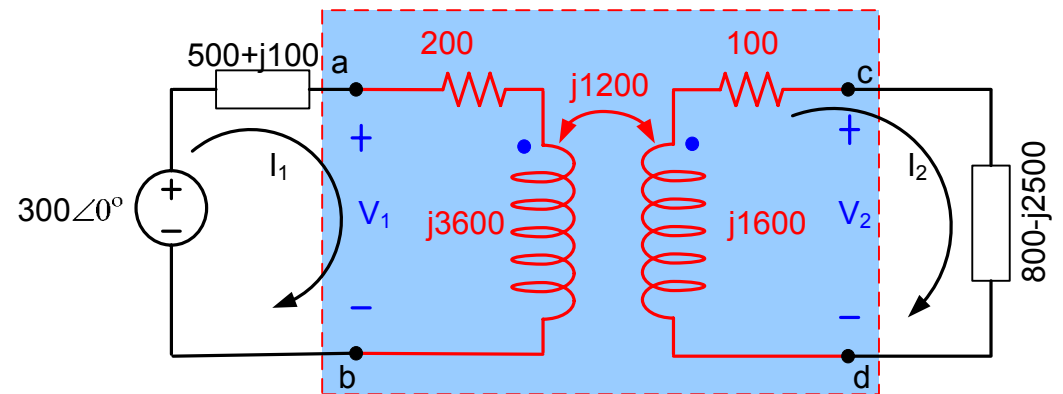


Fig.33-3 for SelfTest

- ❖ What is the impedance seen looking into the primary terminals?
a) $700+j4800$
b) $200+j3600$
c) $1000+j4400$
d) $800+j800$

Correct answer c