

Electric Circuits II

Frequency Selective Circuits (Filters)
Low and High Pass Filters

Lecture #37

EE 205 Dr. A. Zidouri

The material to be covered in this lecture is as follows:

- Series RC Circuit as a Low Pass filter
- Relating The Frequency Domain to the Time Domain
- Series RC Circuit as High-Pass filter
- Series RC Circuit- Qualitative Analysis
- The Series RC Circuit- Quantitative Analysis

EE 205 Dr. A. Zidouri

After finishing this lecture you should be able to:

- Understand the Behavior of High-Pass Filters
- Distinguish between Low-Pass and High-Pass Filters
- Relate The Cutoff Frequency to the Time Constant
- Analyze Qualitatively And Quantitatively A High-Pass Filter
- Design A Simple High-Pass Filter

The Series RC Circuit Low-Pass Filter

- ✚ The series RC Circuit shown in Fig. 37-1 also behaves as a low pass filter.

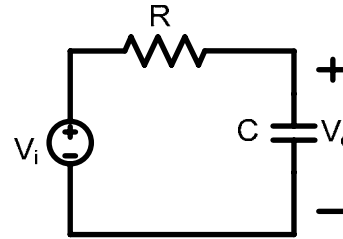


Fig. 37-1 A Series RC Low-Pass filter

- ✚ Note that the circuit's output is defined as the output across the capacitor.
- ✚ As we did in the previous qualitative analysis in Lec36, we use three frequency regions to develop the behavior of the series RC circuit in Fig. 37-1:
 1. Zero Frequency $\omega = 0$ → impedance of the capacitor $Z_c = \infty$, the capacitor acts as an open circuit. The input and output voltages are the same as shown in Fig. 37-2a

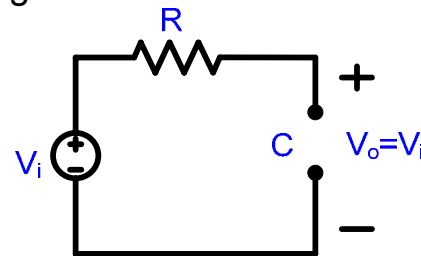


Fig. 37-2a A Series RC Circuit at $\omega = 0$

2. Frequencies increasing from zero. The impedance of the capacitor $Z_c \ll R$, The output voltage is smaller than the source voltage which divides between R and C.
3. Infinite frequency $\omega = \infty \rightarrow$ impedance of the capacitor $Z_c = 0$, the capacitor acts as a short circuit. The output voltage is zero as shown in Fig. 37-2b

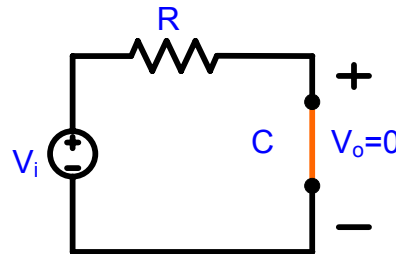


Fig. 37-2b A Series RC
Circuit at $\omega = \infty$

Based on this analysis we see that the series RC circuit functions as a low-pass filter. The following example explores the quantitative analysis of the circuit.

Example 37-1

For the series RC circuit in Fig. 37-1 above:

- ❖ Find the transfer function $H(j\omega) = \frac{V_o}{V_i}$
- ❖ Determine the cutoff frequency in the circuit
- ❖ Choose values of R and C that will yield a low pass filter with $\omega_c = 3kHz$. Take $C = 1\mu F$.

Solution:

To derive the transfer function, consider the s-domain circuit in Fig. 37-3:

$$H(s) = \frac{1}{s + \frac{1}{RC}} \text{ substituting } s = j\omega \text{ we get}$$

$$|H(j\omega)| = \frac{\frac{1}{RC}}{\sqrt{\omega^2 + \left(\frac{1}{RC}\right)^2}} \text{ The cutoff frequency can be found by}$$

$$\text{solving } |H(\omega_c)| = \frac{\frac{1}{RC}}{\sqrt{\omega_c^2 + \left(\frac{1}{RC}\right)^2}} = \frac{1}{\sqrt{2}} \text{ for } \omega_c \text{ we get: } \omega_c = \frac{1}{RC}$$

$$\text{Given } C = 1\mu F \text{ then } R = \frac{1}{\omega_c C} = \frac{1}{(2\pi)(3 \times 10^3)(1 \times 10^{-6})} = 53\Omega$$


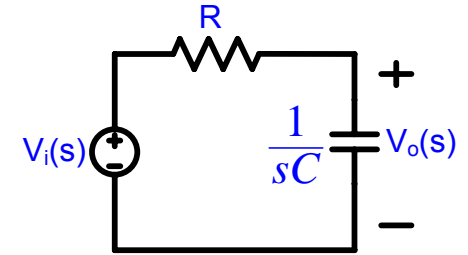


Fig. 37-3 s-domain equivalent for Fig. 37-1

Summary:


Fig. 37-4 summarizes the two low-pass filter circuits we have seen in Lec36 and this lecture. Look how similar in form their transfer functions are:
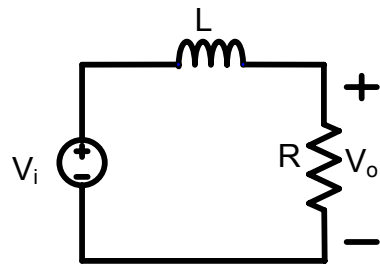
$$H(s) = \frac{\omega_c}{s + \omega_c} \quad (37-1)$$



$$H(s) = \frac{R}{s + \frac{R}{L}}$$

$$\omega_c = \frac{R}{L}$$

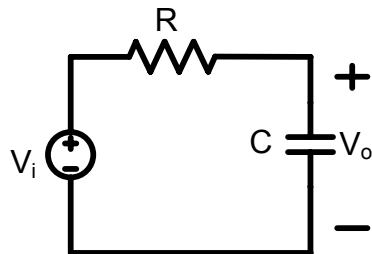

$$H(s) = \frac{1}{s + \frac{1}{RC}}$$

$$\omega_c = \frac{1}{RC}$$

Relating the Frequency Domain to the Time Domain

An other important relationship is relating the time constant to the cutoff frequency.

Remember that for RL circuit the time constant is

$\tau = \frac{L}{R}$ and for an RC circuit the time constant is

$\tau = RC$

Compare the time constants to the cutoff frequencies for these circuits, notice that

$$\tau = \frac{1}{\omega_c} \quad (37-2)$$

Fig. 37-4 Two Low-Pass filters together with their Transfer Functions and Cutoff Frequencies

High Pass Filter

The Series RC Circuit – Qualitative Analysis

- ✚ Now we examine a High-Pass Filter, series RC Circuit shown in Fig. 37-5a
- ✚ The circuit's output is the voltage across **R**.
- ✚ Behavior of **R** will **not** change with changing frequency
- ✚ Behavior of capacitor **C** will change with changing frequency
- ✚ Recall that the impedance of a capacitor is $1/j\omega C$ at **high** frequencies the capacitor's impedance is very **small** compared with the resistor's impedance,
- ✚ The capacitor effectively functions as a **short** circuit. The term high frequencies thus refers to any frequencies for which $\omega C \gg R$
- ✚ The equivalent circuit for $\omega = \infty$ is shown in Fig. 37-5b
- ✚ At this frequency $V_i = V_o$ both in magnitude and phase angle
- ✚ Decreasing the frequency causes the capacitor's impedance to increase.
- ✚ Increasing the capacitor's impedance causes a corresponding **increase** in the magnitude of the voltage drop across **C**
- ✚ Increasing the capacitor's impedance causes a corresponding **decrease** in the magnitude of V_o the **output voltage** drop across **R**
- ✚ Increasing the capacitor's impedance also introduces a shift in phase angle between V_C the voltage across the capacitor and I_C the current in the capacitor

- ✚ This results in a phase angle difference between the input and output voltage, V_o Leads V_i as the frequency decreases this phase lead approaches 90°
- ✚ The capacitor effectively functions as an **open** circuit. The term **Low** frequencies thus refers to any frequencies for which $\omega C \ll R$
- ✚ The equivalent circuit for $\omega = 0$ is shown in Fig. 37-5c

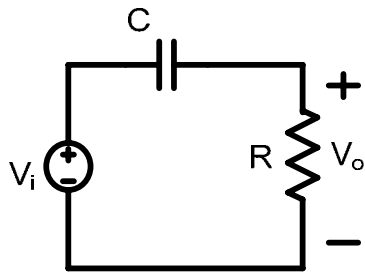


Fig. 37-5a A Series RC High-Pass filter

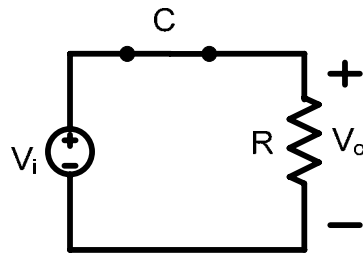


Fig. 37-5b RC Circuit Equivalent at $\omega = \infty$


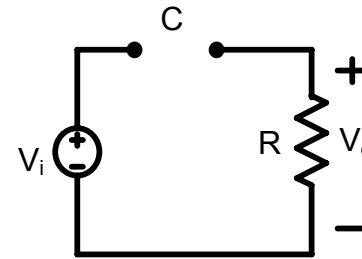


Fig. 37-5c RC Circuit Equivalent at $\omega = 0$

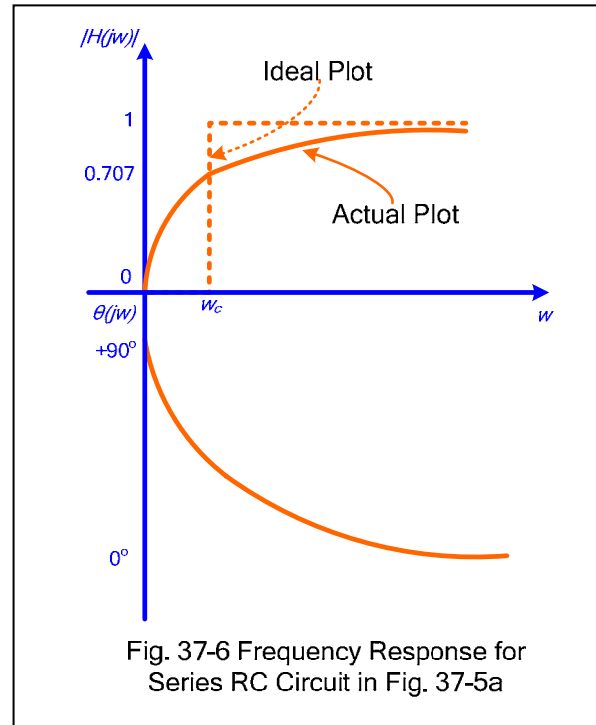- ✚ Based on the behavior of the output voltage magnitude at **low** frequencies $V_o = 0$ at $\omega = 0$ this series RC circuit selectively passes **high**-frequency inputs to the output.
- ✚ This circuit response is shown in Fig. 37-6



The Series RC Circuit – Quantitative Analysis

✚ Consider the circuit of Fig. 37-7

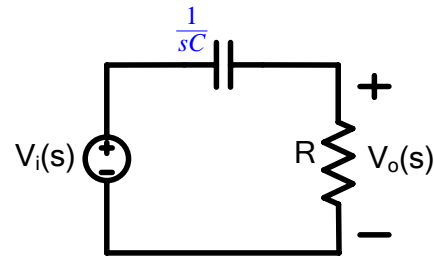


Fig. 37-7 s-domain equivalent for the Circuit of Fig. 37-5a

The voltage transfer function for this circuit is:
$$H(s) = \frac{s}{s + \frac{1}{RC}} \quad (37-3)$$

To study the frequency response we replace $s = j\omega$ in equ. (37-3):
$$H(j\omega) = \frac{j\omega}{j\omega + \frac{1}{RC}} \quad (37-4)$$

The Series RL Circuit – Quantitative Analysis (cont)

Equation (37-4) expressed in polar form gives the magnitude and phase:

$$\left| H(j\omega) \right| = \frac{\omega}{\sqrt{\omega^2 + \left(\frac{1}{RC} \right)^2}} \quad (37-5)$$

$$\theta(j\omega) = 90^\circ - \tan^{-1} \omega RC \quad (37-6)$$

Close examination of these equations provide quantitative support for the plots seen in Fig. 37-6. We can now compute ω_c in terms of the circuit elements:

Recall from (36-1) that $\left| H(j\omega_c) \right| = \frac{1}{\sqrt{2}} H_{\max}$, and for high-pass filter, $H_{\max} = \left| H(j\infty) \right|$ as seen in

Fig. 37-6 thus: $\left| H(j\omega_c) \right| = \frac{1}{\sqrt{2}} = \frac{\omega}{\sqrt{\omega^2 + \left(\frac{1}{RC} \right)^2}} \quad (37-7),$

Solving we get: $\omega_c = \frac{1}{RC} \quad (37-8).$

Not surprising it is the same as for Low-pass filter as the RC circuit has the same time constant whether configured as a low-pass or high-pass filter, as seen in equ. (37-2)

Example 37.2

Consider the circuit of Fig. 37-8, determine what type of filter is this and calculate its cutoff frequency. Take $R=2k\Omega$, $L=2H$, and $C=2\mu F$.

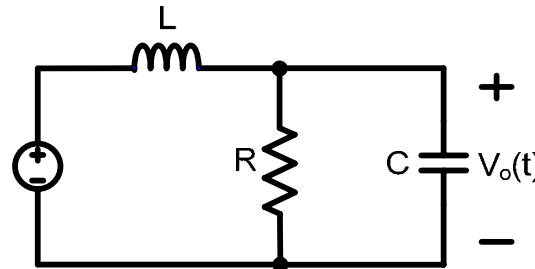


Fig. 37-8 Circuit for Example 37-2

Solution:

The transfer function

$$H(s) = \frac{V_o}{V_i} = \frac{R \parallel \frac{1}{sC}}{sL + R \parallel \frac{1}{sC}} \quad (37-9)$$

But $R \parallel \frac{1}{sC} = \frac{R/sC}{R + 1/sC} = \frac{R}{1 + sRC}$ substituting gives:

$$H(s) = \frac{V_o}{V_i} = \frac{\frac{R}{1 + sRC}}{sL + \frac{R}{1 + sRC}} = \frac{R}{s^2RLC + sL + R} \quad (37-10)$$

Example 37.2 cont.

or $H(\omega) = \frac{R}{-\omega^2 RLC + j\omega L + R}$ (37-11)

since $H(0) = 1$ and $H(\infty) = 0$, we conclude that it is a **Low-Pass Filter**.

Cutoff frequency:

$$\left| H(\omega_C) \right| = \frac{R}{\sqrt{(R - \omega_C^2 RLC)^2 + \omega_C^2 L^2}} = \frac{1}{\sqrt{2}}$$

Or $2 = \left(1 - \omega_C^2 LC\right)^2 + \left(\frac{\omega_C L}{R}\right)^2$

Substituting the values given, we obtain:

$$2 = \left(1 - \omega_C^2 4 \times 10^{-6}\right)^2 + \left(\omega_C \times 10^{-3}\right)^2 \text{ or } 16\omega_C^4 - 7\omega_C^2 - 1 = 0 \text{ solving we get : } \omega_C^2 = 0.5509 \text{ or } \omega_C = 0.742$$

Assuming $\omega_C = 0.742 \text{krad/s}$, therefore the cutoff frequency is $\omega_C = 742 \text{rad/s}$

Summary:

Similarly to RC we can also form a High-Pass filter using RL Circuit and take the output across the inductor. Fig. 37-9 summarizes two High-pass filter circuits and their transfer functions. Look how similar in form their transfer functions are:

$$H(s) = \frac{s}{s + \omega_c} \quad (37-12)$$

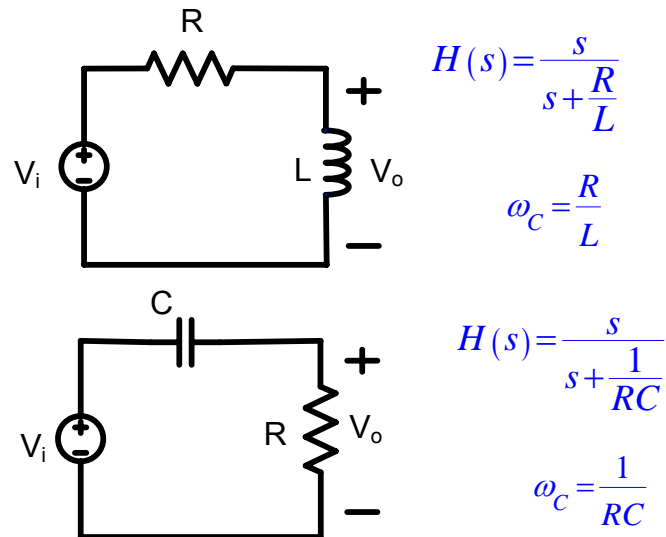


Fig. 37-9 Two High-Pass filters together with their Transfer Functions and Cutoff Frequencies

Self Test 37:

For the circuit in Fig. 37-10, obtain the transfer function $H(s) = \frac{V_o(\omega)}{V_i(\omega)}$ Identify the type of filter the circuit represents and determine the cutoff frequency. Take $R_1 = 100\Omega = R_2$, $L = 2mH$,

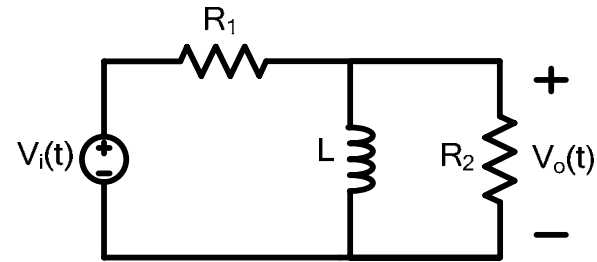


Fig. 37-10 Circuit for Self Test 37

Answer:

The transfer function $H(s) = \frac{V_o}{V_i} = \frac{sR_2L}{R_1R_2 + sL(R_1 + R_2)}$ (37-13)

$$= \frac{\frac{R_2 s L}{R_2 + s L}}{R_1 + \frac{R_2 s L}{R_2 + s L}} = \frac{\left(\frac{R_2}{R_1 + R_2}\right) s}{s + \left(\frac{R_2}{R_1 + R_2}\right) \frac{R_1}{L}} = \frac{K s}{s + \omega_C} \quad (37-14)$$

$$\text{or } H(\omega) = \frac{R_2}{(R_1 + R_2)} \left(\frac{j\omega}{j\omega + \frac{R_1 R_2}{(R_1 + R_2) L}} \right) \quad (37-15)$$

since $H(0) = 0$ and $H(\infty) = 1$, we conclude that it is a **High-Pass Filter**.

Cutoff frequency:

$$\omega_C = K \frac{R_1}{L} = \frac{R_1 R_2}{(R_1 + R_2) L} = 25 \text{krad/s}$$