

Electric Circuits II

Frequency Selective Circuits (Filters)  
**Bandpass Filters**

**Lecture #38**

EE 205 Dr. A. Zidouri

The material to be covered in this lecture is as follows:

- Introduction to Bandpass filters
- Center Frequency, Bandwidth and Quality factor
- Bandpass Series RLC Circuit Analysis
- Relationship between different parameters

EE 205 Dr. A. Zidouri

After finishing this lecture you should be able to:

- Understand the behavior of Bandpass filters
- Determine the different Bandpass filter parameters
- Relate each parameter in terms of other parameters
- Analyze Bandpass filter
- Design a simple Bandpass filter

## Introduction to Bandpass filters

- + Bandpass filters are those that pass voltages within a band of frequencies to the output while filtering out voltages at frequencies outside this band.
- + Bandpass filters and Bandstop filters thus perform complementary functions in the frequency domain.
- + These filters are characterized by same parameters
  - Two cutoff frequencies  $\omega_{C1}$ ,  $\omega_{C2}$
  - The center frequency  $\omega_0$
  - The bandwidth  $\beta$
  - The quality factor  $Q$
- + Only two of these five parameters can be specified independently
- + These parameters are defined in the same way for both types of filters. So we examine only the Bandpass filter at the beginning

## Bandpass Filter: Center Frequency, Bandwidth, and Quality Factor

- ✚ The center frequency  $\omega_0$  is defined as the frequency for which a circuit's TF is purely real. It is also referred to as the resonant frequency.
- ✚ The center frequency is the geometric center of the passband, that is,  $\omega_0 = \sqrt{\omega_{C1}\omega_{C2}}$  (38-1)
- ✚ The magnitude of the TF is maximum at the center frequency  $H_{\max} = \left| H(j\omega_0) \right|$  (38-2)
- ✚ The bandwidth  $\beta$  is the width of the passband  $\beta = \omega_{C2} - \omega_{C1}$  (38-3)
- ✚ The quality factor  $Q$  is the ratio of the center frequency to the bandwidth  $Q = \frac{\omega_0}{\beta}$  (38-4)

## Analysis of the Bandpass Series RLC Circuit

Consider the Bandpass Circuit of Fig. 38-1. Using the same arguments used for Low-pass and High-pass filters, so as before changing the frequency of the source results in changes to the impedance of the capacitor and the inductor.

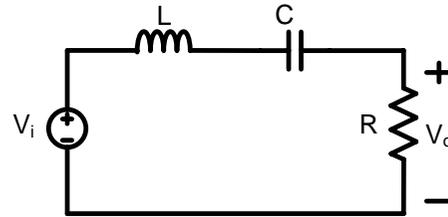


Fig. 38-1a A Series RLC Bandpass filter

- At  $\omega=0$  the impedance of the capacitor is  $\frac{1}{j\omega C}=\infty$  so the capacitor behaves like an open circuit, and the impedance of the inductor is  $j\omega L=0$  so the inductor behaves like a short circuit. Fig. 38-1b depicts this result. Thus  $V_o=0$

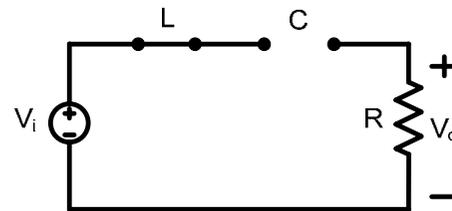


Fig. 38-1b Series RLC  
Equivalent circuit for  $\omega=0$

## Bandpass Series RLC Circuit Analysis cont.

- At  $\omega = \infty$  the impedance of the capacitor is  $\frac{1}{j\omega C} = 0$  so the capacitor behaves like a short circuit, and the impedance of the inductor is  $j\omega L = \infty$  so the inductor behaves like an open circuit. Fig. 38-1c depicts this result. Thus  $V_o = 0$  also.

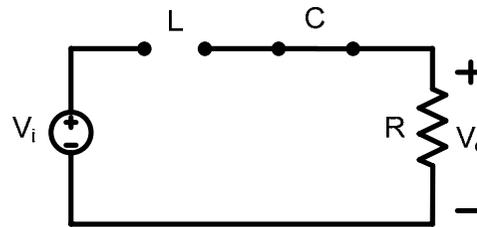


Fig. 38-1c Series RLC  
Equivalent circuit for  $\omega = \infty$

- Between these two extreme values, both the inductor and capacitor have finite impedances.
- At some special frequency in between, the center frequency  $\omega_0$ , the two impedances cancel out causing the output voltage to equal the source voltage  $V_o = V_i$ . At  $\omega_0$  the series combination of L and C appears as a short circuit.
- The plot of the voltage magnitude ratio is shown in Fig. 38-2a. Note the ideal Bandpass filter plot is also overlaid on the plot of the RLC circuit.
- At very low frequencies the phase angle at the output maximizes at  $+90^\circ$ , and at very high frequencies the phase angle at the output reaches its negative maximum of  $-90^\circ$  as seen in Fig. 38-2b

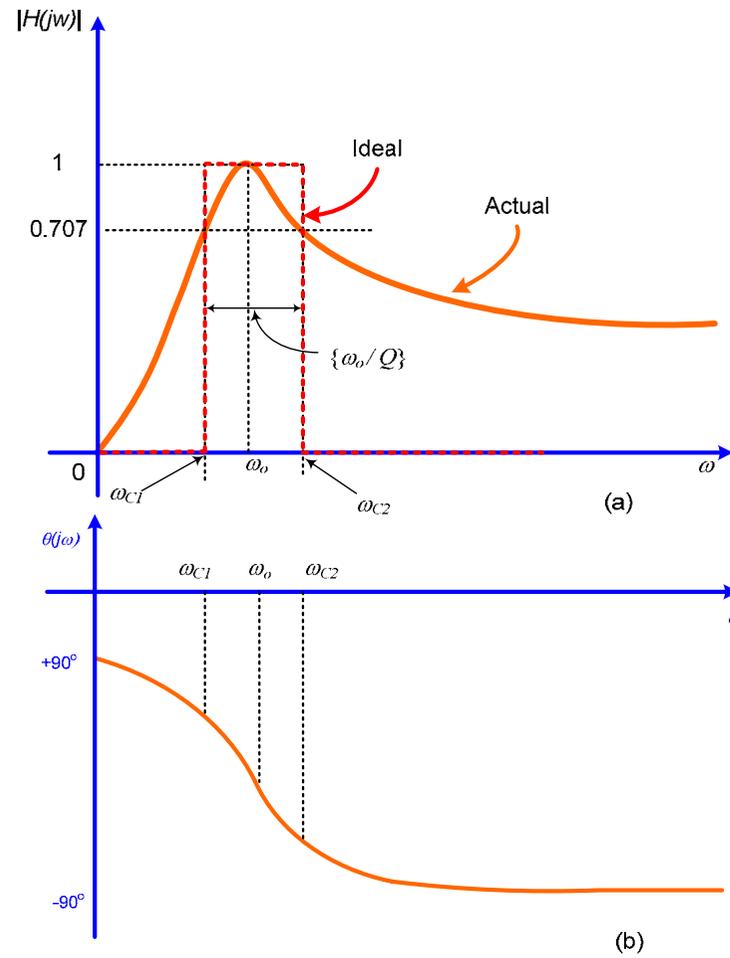


Fig. 38-2 The frequency response plot for the series RLC bandpass filter circuit in Fig. 38-1

## Bandpass Series RLC Circuit Analysis Cont.

Let's now examine the circuit quantitatively. Consider the s-domain equivalent circuit for the series RLC shown in Fig. 38-3 below

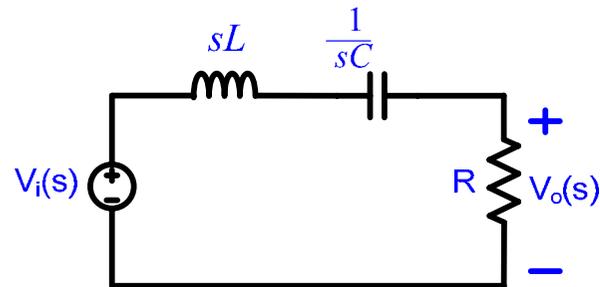


Fig. 38-3 s-domain equivalent for the circuit in Fig. 38-1a

Transfer function of the circuit:

$$H(s) = \frac{\left(\frac{R}{L}\right)s}{s^2 + \left(\frac{R}{L}\right)s + \frac{1}{LC}} \quad (38-5)$$

This equation gives magnitude and phase as before if we express it in polar form and substituting  $s = j\omega$  we get:

$$|H(j\omega)| = \frac{\omega \frac{R}{L}}{\sqrt{\left(\frac{1}{LC} - \omega^2\right)^2 + \left(\omega \frac{R}{L}\right)^2}} \quad (38-6)$$

$$\theta(j\omega) = 90^\circ - \tan^{-1} \left( \frac{\omega \frac{R}{L}}{\frac{1}{LC} - \omega^2} \right) \quad (38-7)$$

We now calculate the five parameters that characterize this RLC bandpass filter:

**Center Frequency:** The TF in (38-5) will be purely real when  $j\omega_0 L + \frac{1}{j\omega_0 C} = 0$  (38-8)

solving for  $\omega_0$  we get:

$$\omega_0 = \sqrt{\frac{1}{LC}} \quad (38-9)$$

Cutoff Frequencies  $\omega_{c1}$  and  $\omega_{c2}$ : At the cutoff frequency  $|H(j\omega_c)| = \frac{1}{\sqrt{2}} H_{\max}$  (38-10) where

$H_{\max} = |H(j\omega_0)|$  we can calculate  $H_{\max}$  by substituting equ. (38-9) into equ. (38-6)

$$H_{\max} = \frac{\omega_0 \frac{R}{L}}{\sqrt{\left(\frac{1}{LC} - \omega_0^2\right)^2 + \left(\omega_0 \frac{R}{L}\right)^2}}$$

$$= \frac{\sqrt{\frac{1}{LC}} \frac{R}{L}}{\sqrt{\left(\frac{1}{LC} - \frac{1}{LC}\right)^2 + \left(\sqrt{\frac{1}{LC}} \frac{R}{L}\right)^2}} = 1$$

Solving for  $\omega_{c1}$  and  $\omega_{c2}$ , using (38-9) we get:

$$|H(j\omega_c)| = \frac{1}{\sqrt{2}} = \frac{\omega_c \frac{R}{L}}{\sqrt{\left(\frac{1}{LC} - \omega_c^2\right)^2 + \left(\omega_c \frac{R}{L}\right)^2}}$$

$$\frac{1}{\sqrt{2}} = \frac{1}{\sqrt{\left(\omega_c \frac{L}{R} - \frac{1}{\omega_c RC}\right)^2 + 1}} \quad (38-11)$$

$$\pm 1 = \omega_c \frac{L}{R} - \frac{1}{\omega_c RC} \quad (38-12)$$

rearranging and solving gives:

$$\omega_{c1} = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \left(\frac{1}{LC}\right)} \quad (38-13)$$

$$\omega_{c2} = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \left(\frac{1}{LC}\right)} \quad (38-14)$$

We can use these last two equations to confirm that  $\omega_0$  is the geometric mean of the two cutoff

$$\text{frequencies } \omega_0 = \sqrt{\omega_{c1}\omega_{c2}} = \sqrt{\frac{1}{LC}} \quad (38-15)$$

$$\text{We can compute also the bandwidth } \beta = \omega_{c2} - \omega_{c1} = \frac{R}{L} \quad (38-16)$$

And the Quality factor  $Q = \frac{\omega_0}{\beta} = \frac{\sqrt{1/LC}}{(R/L)} = \sqrt{L/CR^2}$  (38-17)

Note that we can express the cutoff frequencies in terms of center frequency and bandwidth as:

$$\omega_{c1} = -\frac{\beta}{2} + \sqrt{\left(\frac{\beta}{2}\right)^2 + \omega_0^2} \quad (38-18)$$

$$\omega_{c2} = \frac{\beta}{2} + \sqrt{\left(\frac{\beta}{2}\right)^2 + \omega_0^2} \quad (38-19)$$

### Example 38-1

- Show that the RLC circuit in Fig. 38-4 is a bandpass filter by deriving an expression for the transfer function  $H(s)$
- Compute the center frequency  $\omega_0$
- Calculate the Cutoff Frequencies  $\omega_{c1}$  and  $\omega_{c2}$ , the Bandwidth  $\beta$  and the Quality factor  $Q$ .
- Compute values for  $R$  and  $L$  to yield a bandpass filter with  $\beta = 200\text{Hz}$  a center frequency  $\omega_0 = 5\text{kHz}$ , using  $5\mu\text{F}$  capacitor

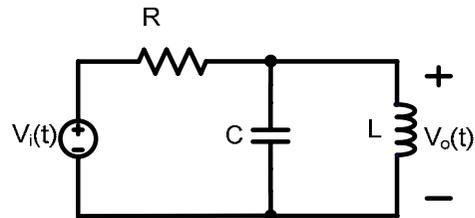


Fig. 38-4 Circuit for Example 38-1

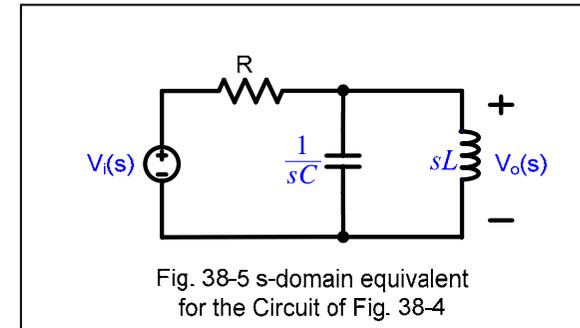


Fig. 38-5 s-domain equivalent for the Circuit of Fig. 38-4

**Solution:**

a) To derive the **transfer function**, consider the s-domain circuit in Fig. 38-5:

Using voltage division  $Z_{eq}(s) = \frac{L}{sL + \frac{1}{sC}}$  Now,  $H(s) = \frac{\frac{s}{RC}}{s^2 + \frac{s}{RC} + \frac{1}{LC}}$

b) **Center frequency:** Substituting  $s = j\omega$  we get

$$|H(j\omega)| = \frac{\frac{\omega}{RC}}{\sqrt{\left(\frac{1}{LC} - \omega^2\right)^2 + \left(\frac{\omega}{RC}\right)^2}} = \frac{1}{\sqrt{1 + \left(\omega RC - \frac{1}{\omega \frac{L}{R}}\right)^2}}$$

the magnitude of this TF is maximum when the term  $\left(\frac{1}{LC} - \omega^2\right)^2$  is zero.

Thus,  $\omega_0 = \sqrt{\frac{1}{LC}}$  and  $H_{\max} = |H(j\omega_0)| = 1$

c) At the **cutoff frequencies**  $|H(j\omega_c)| = \frac{1}{\sqrt{2}} H_{\max} = \frac{1}{\sqrt{2}}$  Substituting this constant in the magnitude

equation above and simplifying, we get:  $\left( \omega_c RC - \frac{1}{\omega_c \frac{L}{R}} \right) = \pm 1$  Solving gives:

$$\omega_{c1} = -\frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \left(\frac{1}{LC}\right)} \quad \omega_{c2} = \frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \left(\frac{1}{LC}\right)}$$

**Bandwidth**  $\beta = \omega_{c2} - \omega_{c1} = \frac{1}{RC}$  Finally the **Quality factor**  $Q = \frac{\omega_0}{\beta} = \sqrt{\frac{R^2C}{L}}$

Note that we can express the cutoff frequencies in terms of center frequency and bandwidth as seen in equations (38-18) and (38-19)

$$\omega_{c1} = -\frac{\beta}{2} + \sqrt{\left(\frac{\beta}{2}\right)^2 + \omega_0^2} \quad \omega_{c2} = \frac{\beta}{2} + \sqrt{\left(\frac{\beta}{2}\right)^2 + \omega_0^2}$$

**Self Test 38:**

Design a bandpass filter of the form in Fig. 38-1a, with  $\omega_{C1} = 20.1\text{kHz}$ ,  $\omega_{C2} = 20.3\text{kHz}$ . Take  $R = 20\text{k}\Omega$ . Calculate L, C, and Q

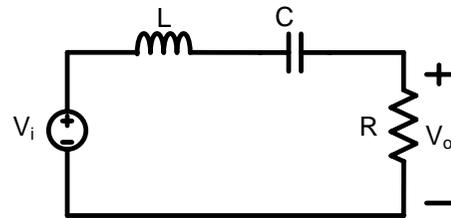


Fig. 38-1a A Series RLC Bandpass filter

**Answer:**

$L = 15.92\text{H}$ ,  $C = 3.9\text{pF}$ ,  $Q = 101$