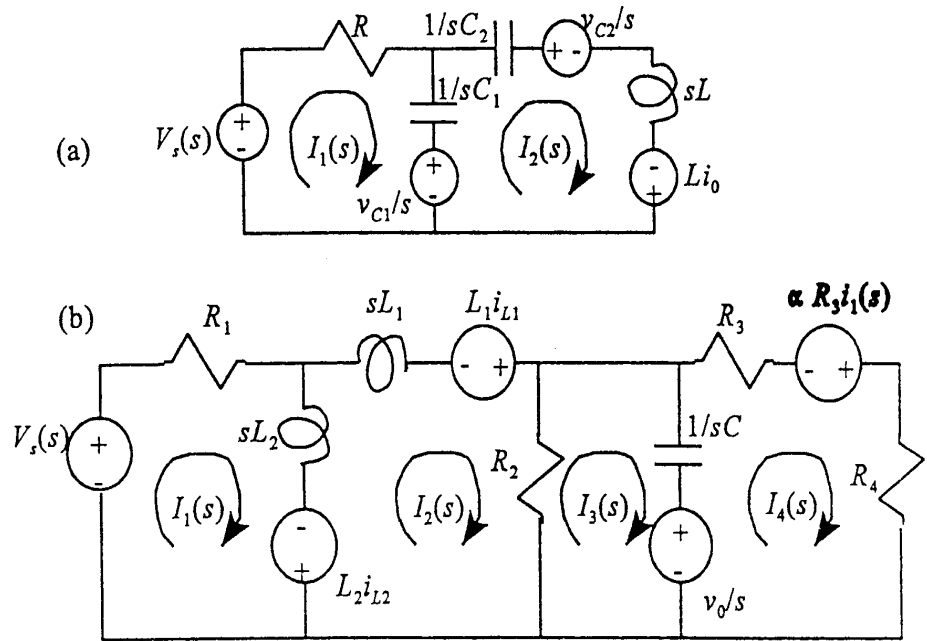


**Problem 6-1**



**Problem 6-2**

(a) The loop equations are:


$$\begin{bmatrix} R + 1/sC_1 & -1/sC_1 \\ -1/sC_1 & 1/sC_1 + 1/sC_2 + sL \end{bmatrix} \begin{bmatrix} I_1(s) \\ I_2(s) \end{bmatrix} = \begin{bmatrix} V_s(s) - v_{C_1}/s \\ v_{C_1}/s - v_{C_2}/s + Li_0 \end{bmatrix}$$

(b) The loop equations for this case are:

$$\begin{bmatrix} R_1 + sL_2 & -sL_2 & 0 & 0 \\ -sL_2 & sL_1 + sL_2 + R_2 & -R_2 & 0 \\ 0 & -R_2 & R_2 + 1/sC & -1/sC \\ -\alpha R_3 & 0 & -1/sC & 1/sC + R_3 + R_4 \end{bmatrix} \begin{bmatrix} I_1(s) \\ I_2(s) \\ I_3(s) \\ I_4(s) \end{bmatrix} = \begin{bmatrix} V_s(s) + L_2 i_{L_2} \\ -L_2 i_{L_2} + L_1 i_{L_1} \\ -v_\phi/s \\ v_\phi/s \end{bmatrix}$$

**Problem 6-3**

Do a Thevenin to Norton transformation of all voltage sources. For example, the circuit of part (a) becomes:

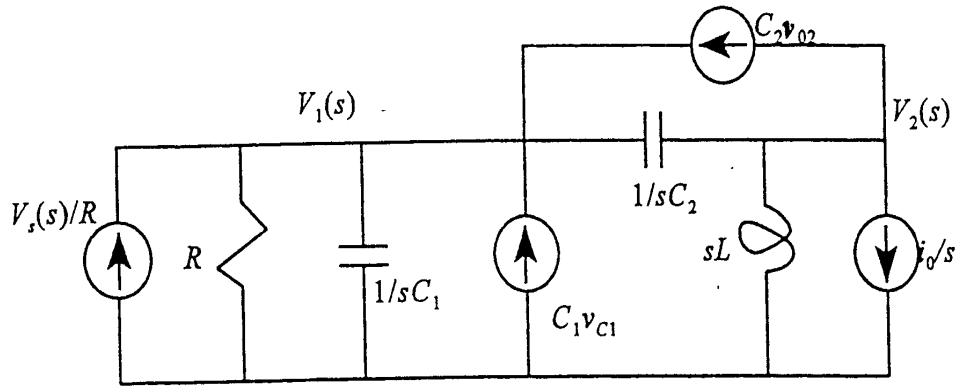

**Problem 6-4**

(a) The matrix equations for the nodal analysis are:

$$\begin{bmatrix} 1/R + sC_1 + sC_2 & -sC_2 \\ -sC_2 & sC_2 + 1/sL \end{bmatrix} \begin{bmatrix} V_1(s) \\ V_2(s) \end{bmatrix} = \begin{bmatrix} V_s(s)/R + C_1 v_{c1} + C_2 v_{c2} \\ -C_2 v_{c2} - i_0/s \end{bmatrix}$$

(b) The nodal analysis matrix equations are:

$$\begin{bmatrix} 1/R_1 + 1/sL_1 + 1/sL_2 & -1/sL_1 & 0 \\ -1/sL_1 & 1/sL_1 + sC + 1/R_2 + 1/R_3 & -1/R_3 \\ 0 & -1/R_3 & 1/R_3 + 1/R_4 \end{bmatrix} \begin{bmatrix} V_1(s) \\ V_2(s) \\ V_3(s) \end{bmatrix} = \begin{bmatrix} V_s(s)/R_1 - i_{L1}/s - i_{L2}/s \\ i_{L1}/s + Cv_0 - \alpha I_1(s) \\ \alpha I_1(s) \end{bmatrix}$$

Note that

$$I_1(s) = [V_s(s) - V_1(s)]/R_1$$


When substituted for  $I_1(s)$  on the right-hand side and rearranging, we obtain the following matrix equation:

$$\begin{bmatrix} 1/R_1 + 1/sL_1 + 1/sL_2 & -1/sL_1 & 0 \\ -1/sL_1 - \alpha/R_1 & 1/sL_1 + sC + 1/R_2 + 1/R_3 & -1/R_3 \\ \alpha/R_1 & -1/R_3 & 1/R_3 + 1/R_4 \end{bmatrix} \begin{bmatrix} V_1(s) \\ V_2(s) \\ V_3(s) \end{bmatrix} = \begin{bmatrix} V_s(s)/R_1 - i_{L1}/s - i(0^-)/s \\ i_{L1}/s + Cv_0 - \alpha V_s(s)/R_1 \\ \alpha V_s(s)/R_1 \end{bmatrix}$$

**Problem 6-6**

Replace the coupled coils with a T-equivalent circuit:

3/6

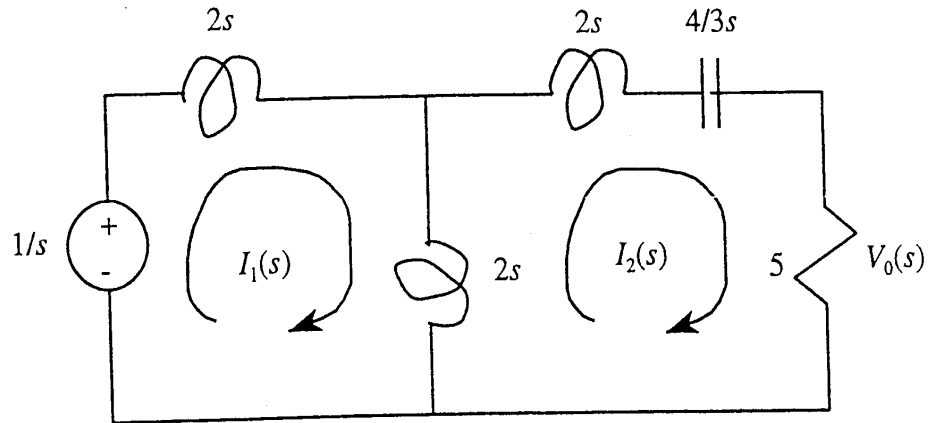

Writing KVL equations around each loop, we obtain

$$\begin{bmatrix} 4s & -2s \\ -2s & 4s + \frac{4}{3s} + 5 \end{bmatrix} \begin{bmatrix} I_1(s) \\ I_2(s) \end{bmatrix} = \begin{bmatrix} 1/s \\ 0 \end{bmatrix}$$

Solve for  $I_2(s)$  and then find the output voltage:

$$V_0(s) = 5I_2(s) = \frac{5}{6\left(s^2 + \frac{5}{3}s + \frac{4}{9}\right)} = \frac{5}{6(s + 1/3)(s + 4/3)} = \frac{A}{s + 1/3} + \frac{B}{s + 4/3}$$

The expansion coefficients are

$$A = (s + 1/3)V_0(s)|_{s=-1/3} = \frac{5}{6} \text{ and } B = (s + 4/3)V_0(s)|_{s=-4/3} = -\frac{5}{6}$$

Thus the output current is

$$v_0(t) = \frac{5}{6} [e^{-t/3} - e^{-4t/3}] u(t)$$

**Problem 6-10**

(a) Use the fact that



$$Z_{eq}(s) = \frac{V_{oc}(s)}{I_{sc}(s)}$$

The first circuit shown can be used to compute  $V_{oc}$ . Write KCL equations at nodes a and b:

$$\frac{1}{2} \left( V_a - \frac{1}{s^2} \right) + I + \frac{V_a - V_b}{3s} = 0, \quad V_1 = \frac{I}{s}$$

$$\frac{V_b - V_a}{s} = 3I = 3sV_a$$

4/6

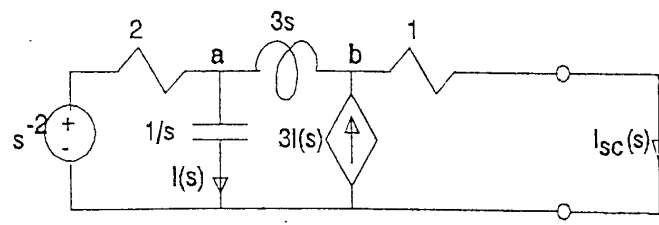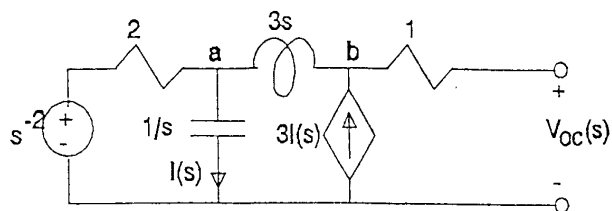

Solve the second equation for  $V_b$  in terms of  $V_a$  and substitute into the first equation after substituting for  $I(s)$ :

$$V_a \left( \frac{1}{2} + \frac{1}{3s} + s \right) - \frac{V_b}{3s} = \frac{1}{2s^2}, \text{ or } V_a \left( \frac{1}{2} + \frac{1}{3s} + s - \frac{1}{3s} - 3s \right) = \frac{1}{2s^2}$$

Thus

$$V_a = \frac{1}{s^2(1-4s)} \text{ and } V_b = V_{oc} = \frac{1+9s}{s^2(1-4s)}$$

Now use the lower circuit to find  $I_{sc}$ . Write KCL at nodes a and b:

$$\frac{V_a - 1/s^2}{2} + sV_a + \frac{V_a - V_b}{3s} = 0$$

$$\frac{V_b - V_a}{3s} - 3I' + V_b = 0, \quad I' = sV_a$$

(Note that all voltages and currents are different in the short circuit case than in the open circuit case - in particular, the current through the capacitor.) Substitute for  $I'$  in the second equation and solve for  $V_a$  in terms of  $V_b$ . This gives

$$V_a = \frac{1+3s}{1+9s^2} V_b$$


Collect terms in the first equation and substitute for  $V_a$ :

$$V_b = \frac{1+9s^2}{s^2(3-s+6s^2)} = I_{sc} = \frac{V_b}{1}$$

Therefore


$$Z_{eq} = \frac{V_{oc}}{I_{sc}} = \frac{6s^2 - s + 3}{1 - 4s}$$

The Thevinin and Norton equivalent circuits are shown below:

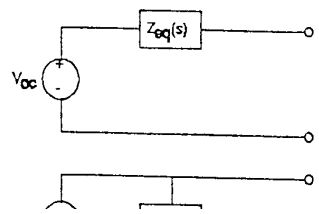

**Problem 6-17**

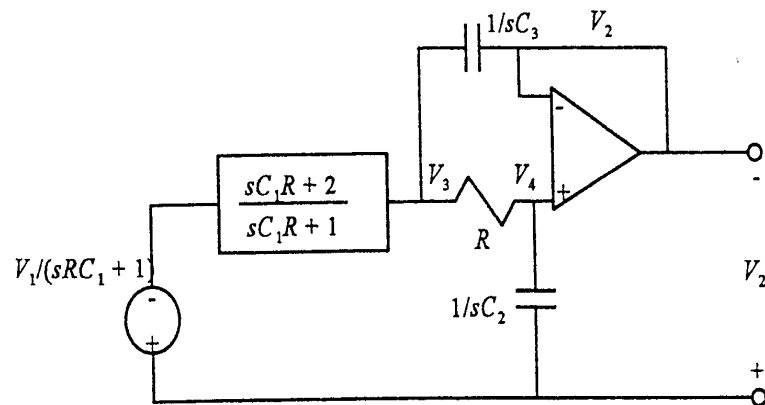(a) Do a Thevenin-to-Norton equivalent of the input, and a parallel combination of  $R$  and  $1/sC_1$ ; then combine  $R \parallel 1/sC_1$  and the second  $R$  in series to finally end up with the Laplace-equivalent circuit shown below:



Write a KCL equation at node 3:

$$\frac{V_3 - V_1/(sC_1R + 1)}{(sC_1R + 2)/(sC_1R + 1/R)} + \frac{V_3 - V_2}{R} + sC_3(V_3 - V_2) = 0 \quad (1)$$

Write a KCL equation at node 4:

$$\frac{V_4 - V_3}{R} + sC_2V_4 = 0 \quad (2)$$

Because of the ideal operational amplifier,  $V_2 = V_4$ . We may use (2) to replace  $V_4$  by  $V_2$  in (1) and (2). Then from (2) with the substitution, we obtain

$$V_3 = (1 + sC_2R)V_2 \quad (3)$$

Replace  $V_3$  in (1) using (3). We then solve for  $V_2/V_1$  to get

$$H(s) = \frac{1}{R^3C_1C_2C_3s^3 + 2R^2C_2(C_1 + C_3)s^2 + R(C_1 + 3C_2)s + 1}$$

or

$$H(s) = \frac{1}{R^3C_1C_2C_3s^3 + \frac{2}{R}\left(\frac{1}{C_1} + \frac{1}{C_3}\right) + \frac{1}{R^2C_3}\left(\frac{3}{C_1} + \frac{1}{C_2}\right)s + \frac{1}{R^3C_1C_2C_3}}$$

With the parameter values given, the following MATLAB program (echo on) gives the values of the denominator polynomial coefficients, the roots or poles, and compares the complex poles obtained with what should be the case for the complex poles of a Butterworth filter with the real root matching.

```
% Solution for Problem 6-17
%
C1 = 0.0022*10^(-6);
C2 = 0.00033*10^(-6);
C3 = 0.0056*10^(-6);
R = 10000;
A = (2/R)*(1/C1+1/C3)
A =
    1.2662e+005
B = (1/(R^2*C3))*(3/C1+1/C2)
B =
    7.8463e+009
C = 1/(R^3*C1*C2*C3)

C =
    2.4597e+014
p = [1 A B C];
s_poles = roots(p)
s_poles =
    1.0e+004 *
    -6.4078
    -3.1273 + 5.3484i
    -3.1273 - 5.3484i
s_poles_butter = s_poles(1)*(cos(pi/3)+i*sin(pi/3))
s_poles_butter =
    -3.2039e+004- 5.5493e+004i
```

Note that the poles of the designed filter and the true Butterworth filter match up fairly well. One could adjust the  $R$  and  $C$  values to give a closer match.