
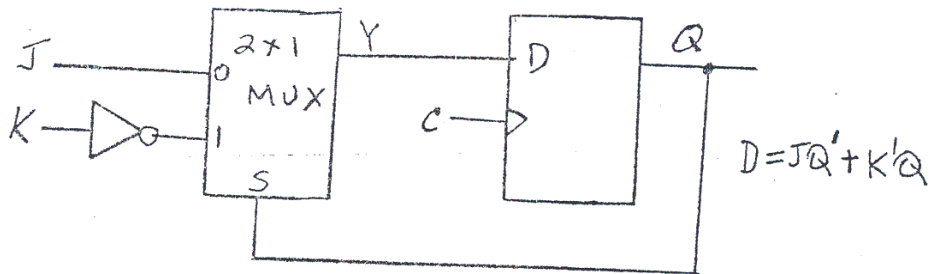


5-2 /

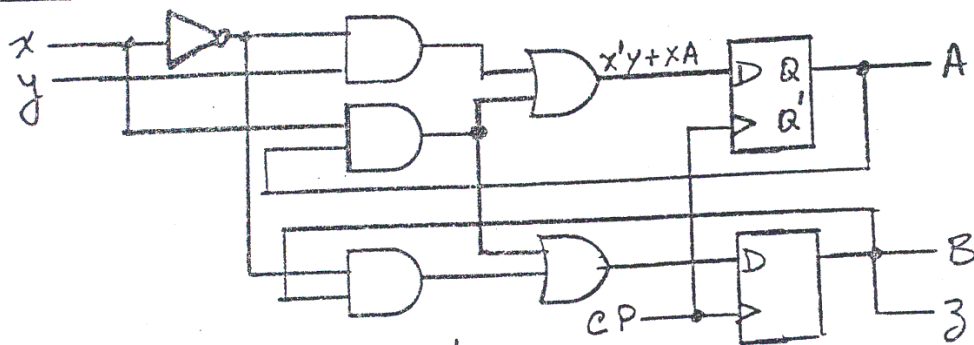


5-6 (a)



(b)


Present state AB	inputs xy	Next state AB	output z
00	00	00	0
00	01	10	0
00	10	00	0
00	11	00	0
01	00	01	1
01	01	11	1
01	10	00	1
01	11	00	1
10	00	00	0
10	01	10	0
10	10	11	0
10	11	11	0
11	00	01	1
11	01	11	1
11	10	11	1
11	11	11	1

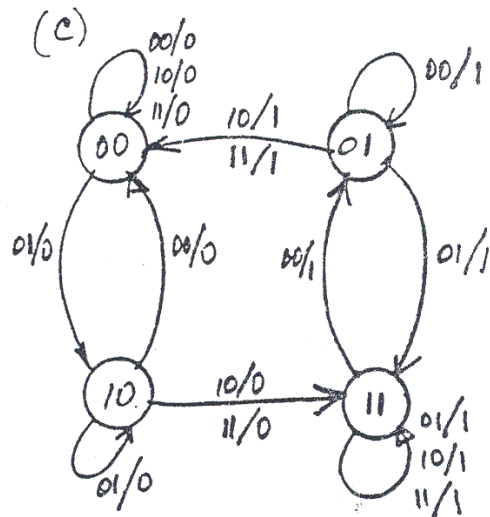

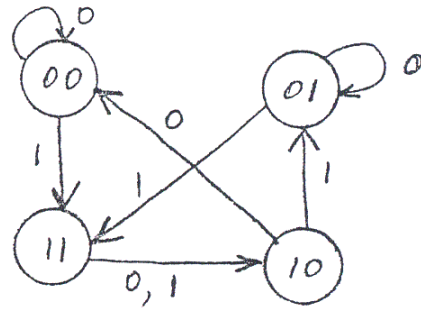5-9 ✓

$$A(t+1) = J_A A' + K' A \\ = x A' + B A$$

$$B(t+1) = J_B B' + K'_B B \\ = x B' + A' B$$



(5-12)

Present state	Next state		Output	
	0	1	0	1
<i>a</i>	<i>f</i>	<i>b</i>	0	0
<i>b</i>	<i>d</i>	<i>a</i>	0	0
<i>d</i>	<i>g</i>	<i>a</i>	1	0
<i>f</i>	<i>f</i>	<i>b</i>	1	1
<i>g</i>	<i>g</i>	<i>d</i>	0	1

5-19 (a)

Present state	Input	Next state	output
ABC	x	ABC	y
000	0	011	0
000	1	100	1
001	0	001	0
001	1	100	1
010	0	010	0
010	1	000	1
011	0	001	0
011	1	010	1
100	0	010	0
100	1	011	0

$$d(A, B, C, x) = \Sigma(10, 11, 12, 13, 14, 15)$$

AB	Cx	01	11	10
00	00	1	1	
01				
11		x	x	x
10			x	x

$$DA = A'B'x$$

AB	Cx	01	11	10
00	00	1		
01		1		
11		x	x	x
10		1	1	x

$$DB = A + C'x + BCx$$


1			1
			1
x	x	x	x
	1	x	x

$$DC = Cx' + Ax + A'B'x'$$

	1	1	
	1	1	
x	x	x	x
		x	x

$$y = A'x$$

self-correcting

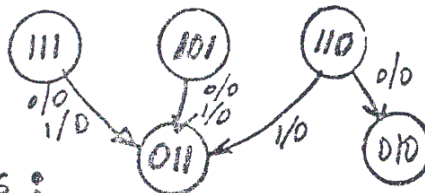

(b) Use JK flip flops:  
same state table as in part (a).

Flip-flop inputs					
JA	KA	JB	KB	JC	KC
0	x	1	x	1	x
1	x	0	x	0	x
0	x	0	x	0	x
1	x	0	x	x	1
0	x	x	0	0	x
0	x	x	1	0	x
0	x	x	0	x	1
x	1	1	x	1	x
x	1	1	x	1	x

$$JA = B'x$$

$$JB = A + C'x'$$

$$JC = Ax + AB'x'$$

$$y = A'x$$

self-correcting

$$KA = 1$$

$$KB = C'x + Cx'$$

$$KC = x$$

because

$$KA = 1$$

5-24)

```
module Async_preset_clear_FF (Q,D,CLK,preset,clear);  
  output Q;  
  input D,CLK,preset,clear;  
  reg Q;  
  always @ (posedge CLK or negedge preset or negedge clear)  
    if (~ preset) Q = 1'b1;  
    else if (~ clear) Q = 1'b0;  
    else Q = D;  
endmodule
```

5-26

$$Q(t + 1) = JQ' + K'Q.$$

When  $Q = 0$ ,  $Q(t + 1) = J$ ;

When  $Q = 1$ ,  $Q(t + 1) = K'$

```
always @ posedge (CLK)
```

```
  if (Q == 0) Q = J;
```

```
    else Q = ~K;
```