

72

$$R_o = r_{o1} // r_{o2} = \frac{r_o}{2} = \frac{|V_A|}{2 I_{REF}}$$

$$1 \text{ M}\Omega = \frac{50 \text{ V}}{2 I_{REF}}$$

$$I_{REF} = \frac{50}{2} = \underline{\underline{25 \mu\text{A}}}$$

$$A_v = -g_{m1} (r_{o1} // r_{o2})$$

$$= -g_{m1} R_o$$

Thus, $-100 = -g_{m1} \times 1 \text{ M}\Omega$

$$g_{m1} = \frac{100}{1} \mu\text{A/V} = 100 \mu\text{A/V}$$

But, $g_{m1} = \sqrt{2 k_n' \left(\frac{W}{L}\right)_1 I_{REF}}$

Thus, $100 = \sqrt{2 \times 50 \times \left(\frac{W}{L}\right)_1 \times 25}$

$$= 50 \sqrt{\left(\frac{W}{L}\right)_1}$$


$$\left(\frac{W}{L}\right)_1 = \underline{\underline{4}}$$

5

79

$$\begin{aligned}
 v_x &= r_o (i_x - g_m v_{gs}) \\
 &\quad + v_s \\
 &= i_x r_o - g_m r_o v_{gs} \\
 &\quad - v_{gs} \\
 &= i_x r_o - (1 + g_m r_o) v_{gs} \\
 &= i_x r_o + (1 + g_m r_o) i_x R_s
 \end{aligned}$$
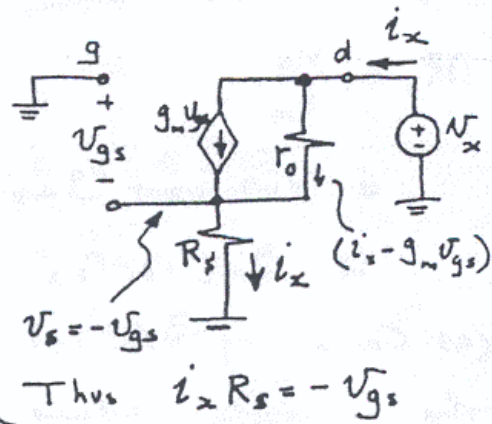
$$\begin{aligned}
 R_o &\equiv \frac{v_x}{i_x} = r_o + (1 + g_m r_o) R_s \\
 &= R_s + r_o (1 + g_m R_s)
 \end{aligned}$$



P. E. D.

80 Refer to Fig. 5.48.

5

$$g_{m1} = \sqrt{2k_n' \left(\frac{W}{L}\right)_1 I_{REF}}$$

$$= \sqrt{2 \times 20 \times 10 \times 200} = \underline{\underline{0.28 \text{ mA/V}}}$$

$$r_{o1} = r_{o2} = \frac{|V_A|}{I_{REF}} = \frac{100 \text{ V}}{0.2 \text{ mA}} = \underline{\underline{500 \text{ k}\Omega}}$$

$$A_v = \frac{g_{m1}}{g_{m1} + g_{mb1} + \frac{1}{r_{o1}} + \frac{1}{r_{o2}}}$$
$$= \frac{0.28}{0.28 + 0.1 \times 0.28 + \frac{1}{500} + \frac{1}{500}}$$

$$= \underline{\underline{0.9 \text{ V/V}}}$$

$$R_o = (1/g_{m1}) \parallel (1/g_{mb1}) \parallel r_{o1} \parallel r_{o2}$$
$$= \frac{1}{0.28 + 0.028 + \frac{1}{500} + \frac{1}{500}}$$
$$= \underline{\underline{3.2 \text{ k}\Omega}}$$

With a 10-k Ω load,

$$A_v = 0.9 \frac{R_L}{R_L + R_o} = 0.9 \times \frac{10}{10 + 3.2}$$
$$= \underline{\underline{0.68 \text{ V/V}}}$$

118 $V_{DS} \gg V_{GS} - V_P$


Thus, $V_{DSmin} = -1 - (-2) = \underline{\underline{+1V}}$

Correspondingly,

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$= 4 \left(1 - \frac{-1}{-2}\right)^2$$
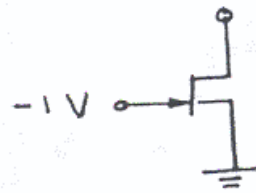
$$= \underline{\underline{1 \text{ mA}}}$$



5

For a 10-V increase in drain voltage, I_D increases by $\frac{10V}{r_o}$ where $r_o = \frac{1}{\lambda I_D} = \frac{1}{0.01 \times 1} = 100 \text{ k}\Omega$.

Thus, I_D increases by 0.1 mA to 1.1 mA.

123 Refer to Fig. P 5.123.

(a) $V_G = V_{DD} \frac{R_{G2}}{R_{G1} + R_{G2}} = 20 \frac{0.6}{1.4 + 0.6} = \underline{\underline{6V}}$

$$V_S = I_D R_S \quad V_{GS} = 6 - I_D R_S = 6 - 2.7 I_D$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$I_D = 12 \left(1 - \frac{6 - 2.7 I_D}{-4} \right)^2$$

$$= 12 \left(1 + \frac{6}{4} - \frac{2.7}{4} I_D \right)^2$$

$$\Rightarrow I_D \approx \underline{\underline{3 \text{ mA}}}$$

$$V_{GS} = \underline{\underline{-2 \text{ V}}}$$


$$V_D = 20 - I_D R_D = 20 - 3 \times 2.7$$

$$= \underline{\underline{11.9 \text{ V}}}$$

(b) $g_m = \frac{2 I_{DSS}}{-V_p} \sqrt{\frac{I_D}{I_{DSS}}}$

$$= \frac{2 \times 2}{4} \sqrt{\frac{3}{12}} = \underline{\underline{3 \text{ mA/V}}}$$

$$r_o = \frac{|V_A|}{I_D} = \frac{12 \times 25}{3} = \underline{\underline{100 \text{ k}\Omega}}$$

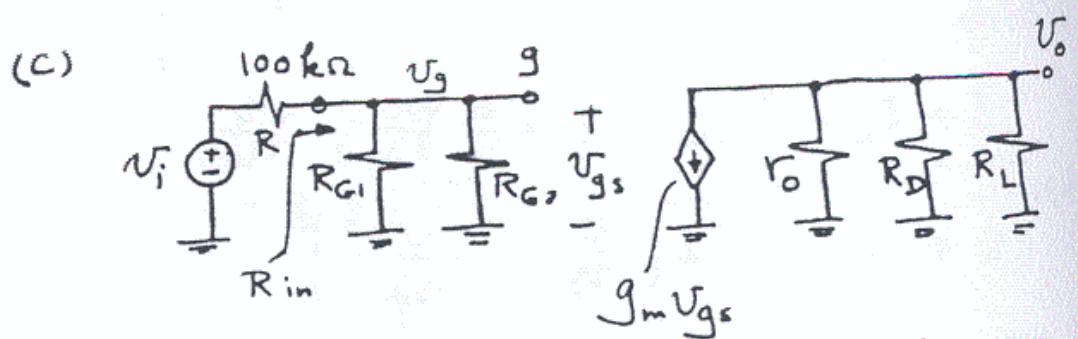

(d) $R_{in} = R_{G1} // R_{G2} = 1.4 // 0.6 = \underline{\underline{420 \text{ k}\Omega}}$

$$\frac{V_g}{V_i} = \frac{R_{in}}{R + R_{in}} = \frac{420}{100 + 420} = \underline{\underline{0.808 \text{ V/V}}}$$