 
 
 
 
 
 
 
 


Slide 1

Logic Symbols with Truth Tables																																	
	<p>BUFFER</p> <table border="1"> <thead> <tr> <th>A</th> <th>B</th> </tr> </thead> <tbody> <tr> <td>1</td> <td>1</td> </tr> <tr> <td>0</td> <td>0</td> </tr> </tbody> </table>	A	B	1	1	0	0		<p>INVERTER</p> <table border="1"> <thead> <tr> <th>A</th> <th>B</th> </tr> </thead> <tbody> <tr> <td>1</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> </tr> </tbody> </table>	A	B	1	0	0	1																		
A	B																																
1	1																																
0	0																																
A	B																																
1	0																																
0	1																																
	<p>AND</p> <table border="1"> <thead> <tr> <th>A</th> <th>B</th> <th>C</th> </tr> </thead> <tbody> <tr> <td>1</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>0</td> <td>0</td> <td>0</td> </tr> </tbody> </table>	A	B	C	1	1	1	1	0	0	0	1	0	0	0	0		<p>NAND</p> <table border="1"> <thead> <tr> <th>A</th> <th>B</th> <th>C</th> </tr> </thead> <tbody> <tr> <td>1</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>0</td> <td>0</td> <td>1</td> </tr> </tbody> </table>	A	B	C	1	1	0	1	0	1	0	1	1	0	0	1
A	B	C																															
1	1	1																															
1	0	0																															
0	1	0																															
0	0	0																															
A	B	C																															
1	1	0																															
1	0	1																															
0	1	1																															
0	0	1																															
	<p>OR</p> <table border="1"> <thead> <tr> <th>A</th> <th>B</th> <th>C</th> </tr> </thead> <tbody> <tr> <td>1</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>0</td> <td>0</td> <td>0</td> </tr> </tbody> </table>	A	B	C	1	1	1	1	0	1	0	1	1	0	0	0		<p>NOR</p> <table border="1"> <thead> <tr> <th>A</th> <th>B</th> <th>C</th> </tr> </thead> <tbody> <tr> <td>1</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>0</td> <td>0</td> <td>1</td> </tr> </tbody> </table>	A	B	C	1	1	0	1	0	0	0	1	0	0	0	1
A	B	C																															
1	1	1																															
1	0	1																															
0	1	1																															
0	0	0																															
A	B	C																															
1	1	0																															
1	0	0																															
0	1	0																															
0	0	1																															
	<p>XOR</p> <table border="1"> <thead> <tr> <th>A</th> <th>B</th> <th>C</th> </tr> </thead> <tbody> <tr> <td>1</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>0</td> <td>0</td> <td>0</td> </tr> </tbody> </table>	A	B	C	1	1	0	1	0	1	0	1	1	0	0	0		<p>XNOR</p> <table border="1"> <thead> <tr> <th>A</th> <th>B</th> <th>C</th> </tr> </thead> <tbody> <tr> <td>1</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>0</td> <td>0</td> <td>1</td> </tr> </tbody> </table>	A	B	C	1	1	1	1	0	0	0	1	0	0	0	1
A	B	C																															
1	1	0																															
1	0	1																															
0	1	1																															
0	0	0																															
A	B	C																															
1	1	1																															
1	0	0																															
0	1	0																															
0	0	1																															

6.071 Digital Logic 1

Digital logic can be described in terms of standard logic symbols and their corresponding truth tables. The electronics companies have made transistor based chips that carry out the function of each of these. The horizontal lines represent inputs or outputs (in the examples above read from left to right). The small circles at the outputs on the right correspond to an inverter (performs a logical NOT operation to the output).

Slide 2


Boolean Algebra	
AND $0 \cdot 0 = 0$ $0 \cdot 1 = 1 \cdot 0 = 0$ $1 \cdot 1 = 1$	OR $0 + 0 = 0$ $0 + 1 = 1 + 0 = 1$ $1 + 1 = 1$
XOR $0 \oplus 0 = 0$ $0 \oplus 1 = 1 \oplus 0 = 1$ $1 \oplus 1 = 0$	NOT If $A = 0$, then $\bar{A} = 1$ If $A = 1$, then $\bar{A} = 0$

6.071 Digital Logic 2

The action of logic circuits can be understood in terms of Boolean logic. We will typically use three elements of this. First you should recall that in our short hand notation 0 is FALSE and 1 is TRUE. The AND operation is indicated by a dot (which is often left out), and the logical table above looks familiar. The OR operation is indicated by a + sign, and the set of outcomes is mostly familiar, but notice that TRUE or TRUE is TRUE. The NOT operation is simply and inversion and is indicated by a bar over the state.

We will also have occasional need for the EXCLUSIVE OR gate which is similar to the OR but is indicated by a + with a circle around it and TRUE EXCLUSIVE OR TRUE is FALSE.

Slide 3

 

We can rewrite the logic gate in terms of Boolean algebra. Notice that the AND and OR gates can be extended to beyond two inputs, in fact they can have any number.

Slide 4

Table of Logic Identities	
1) $A+B = B+A$	13) $A+A = A$
2) $AB = BA$	14) $\overline{AA} = A$
3) $A+(B+C) = (A+B)+C$	15) $\overline{\overline{A}} = A$
4) $A(BC) = (AB)C$	16) $A+\overline{A} = 1$
5) $A(B+C) = AB+AC$	17) $\overline{AA} = 0$
6) $(A+B)(C+D) = AC+AD+BC+BD$	18) $\overline{A+B} = \overline{A}\overline{B}$
7) $\overline{\overline{1}} = 0$	19) $\overline{AB} = \overline{A+B}$
8) $\overline{\overline{0}} = 1$	20) $A+\overline{AB} = A+B$
9) $A \cdot 0 = 0$	21) $\overline{A+AB} = \overline{A+B}$
10) $A \cdot 1 = A$	22) $A \oplus B = \overline{AB} + \overline{A\overline{B}} = (A+B)\overline{AB}$
11) $A+0 = A$	23) $A \oplus B = AB + \overline{AB}$
12) $A+1 = 1$	

6.071 Digital Logic 4

Boolean algebra is simple once you are used to it but takes some getting to know. The above sets of identities are straightforward to show. The first column you probably know (if you say them out in terms of TRUE and FALSE) and second column entries can be figured out and do not need to be memorized.

Slide 5

DeMorgan's Theorem

$$\overline{(X+Y)} = \bar{X} \cdot \bar{Y}$$

Not of the quantity, X OR Y is equal to
NOT X AND NOT Y

X	Y	X+Y	$\overline{X+Y}$	X	Y	\bar{X}	\bar{Y}	$\bar{X} \cdot \bar{Y}$
0	0	0	1	0	0	1	1	1
0	1	1	0	0	1	1	0	0
1	0	1	0	1	0	0	1	0
1	1	1	0	1	1	0	0	0

Compress to


6.071 Digital Logic 5

DeMorgan's theorem is probably the most important of the identities that are not immediately known. Here we show that it is true. Notice that DeMorgan's theorem make concrete the concept that there are many ways of achieving the same truth table. In fact we will demonstrate latter that all logic can be created with NAND gates alone (though this is usually not the most convenient method). Also note that the bubble inverting the input or output of a device can take the place of an inverter.


Slide 6

DeMorgan's Theorem 2

A second version is
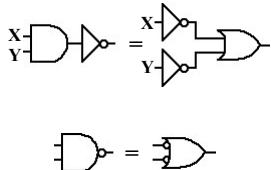
$$\overline{X \cdot Y} = \overline{X} + \overline{Y}$$


or

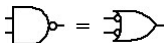


6.071 Digital Logic 6

Another versions of DeMorgan's theorem, this time taking a AND type circuit to an OR. Since all logic could be created with NANDs and NANDs can be mapped into NORs then all logic could also be constructed solely out of NORs.

Slide 7

Problem:

Convince yourself that

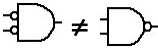


6.071 Digital Logic 7

Write out the truth table of this and convince yourself that you can not simply invert all inputs and outputs and have the same action.


Slide 8

Bubble Pushing


DeMorgan's Theorem says

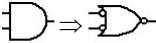


or

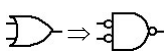

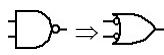
Note: as we quoted DeMorgan's Theorem, it said $\overline{A \cdot B} = \overline{A} + \overline{B}$



Now we add a NOT to each output:

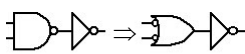

or

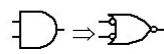

6.071 Digital Logic 8

Now we look at a much more general statement of De Morgan's theorem.

Slide 9

Bubble Pushing 2

1.) change AND to OR
or OR to AND.

2.) invert all inputs and outputs.

The diagrams illustrate the transformation of logic gates according to the rules. The first diagram shows an AND gate with inverted inputs and output becoming an OR gate. The second diagram shows an OR gate with inverted inputs and output becoming an AND gate. The third diagram shows an OR gate with inverted inputs and output becoming an AND gate.

6.071 Digital Logic 9

This does not sound as elegant or mathematical as DeMorgan's theorem, but it covers a much broader set of examples.

Slide 10

 
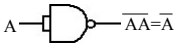
 
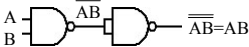
 
 

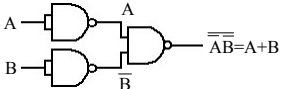
Generalized DeMorgan's Theorem

$$\overline{A \cdot B \cdot C} = \bar{A} + \bar{B} + \bar{C}$$
$$\overline{A + B + C} = \bar{A} \cdot \bar{B} \cdot \bar{C}$$

6.071 Digital Logic 10

 
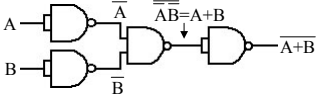
 
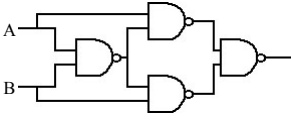

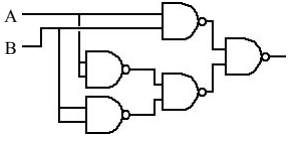
The entire thing can be generalized to any number of inputs and always keeps the same structure.

Slide 11


NAND equivalent circuits	
Logic Gate	NAND Equivalent
NOT 	 $\overline{AA} = \overline{A}$
AND 	 $\overline{\overline{AB}} = AB$
NAND 	
OR 	 $\overline{\overline{A}\overline{B}} = A+B$

As we said, all logic can be written in terms of NANDs and here are some examples. Notice that in some cases the two inputs of the NAND are tied together to make an inverter.

Slide 12


NAND equivalent circuits 2	
Logic Gate	NAND Equivalent
 <p>NOR</p>	 <p>$\overline{A} \overline{B} = A+B$</p>
 <p>XOR</p>	
 <p>XNOR</p>	

Slide 13

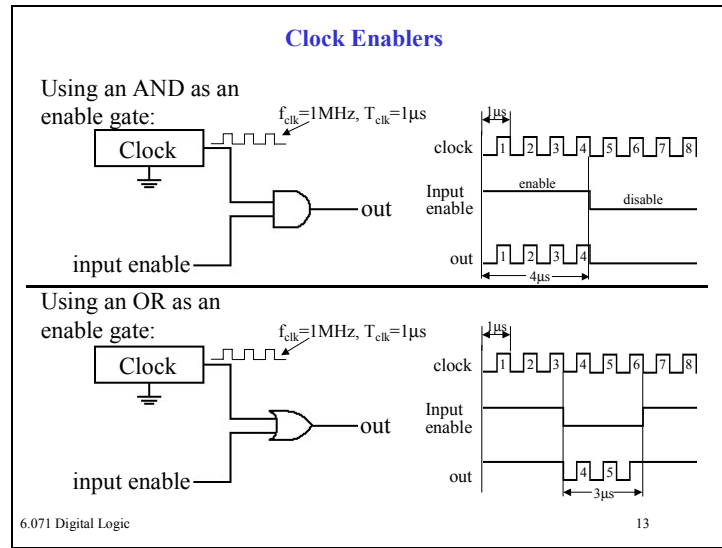


One of the many uses of digital logic is to enable a signal to be transmitted. In this case the clock is the signal and the AND or OR acts to control if it is transmitted. Notice the different actions and the output states when the device is disabled.

Slide 14

 

You can directly build digital circuits from Boolean logic. Two two circuits are the same, the left written as a product of sums and the right as a sum of products. There are also approaches to simplifying a network (including software packages).

Slide 15

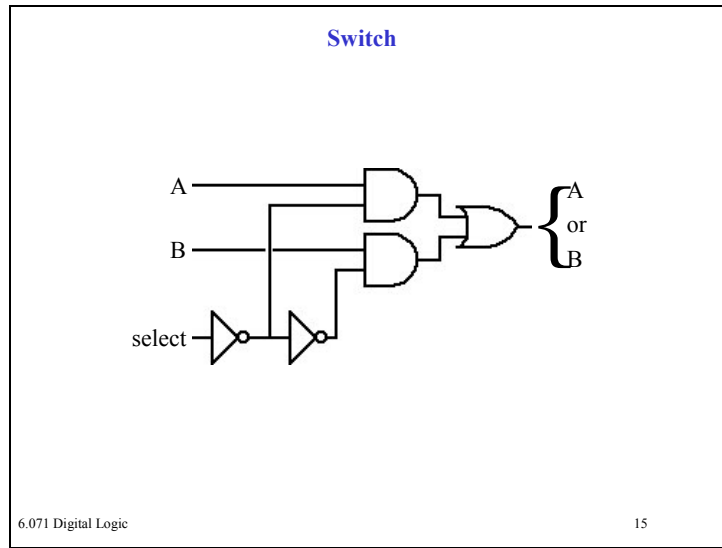

This shows the simple action of a multiplexer, it takes two inputs and switches the output between them.

74LS157 Data Sheet

FAIRCHILD
SEMICONDUCTOR

September 1966
Revised April 2000

DM74LS157 • DM74LS158
Quad 2-Line to 1-Line Data Selectors/Multiplexers

General Description

These data selector/multiplexers contain inverters and drivers to supply full on-chip data selection to the four output gates. A separate strobe input is provided. A 4-bit word is selected from one of two sources and is routed to the four outputs. The DM74LS157 presents true data whereas the DM74LS158 presents inverted data to minimize propagation delay time.

Applications

- Expand any data input point
- Multiplex dual data buses
- Generate four functions of two variables (one variable is common)
- Source programmable counters

Features

- Buffered inputs and outputs
- Typical Propagation Time
DM74LS157 9 ns
DM74LS158 7 ns
- Typical Power Dissipation
DM74LS157 49 mW
DM74LS158 24 mW

Ordering Code:

Order Number	Package Number	Package Description
DM74LS157N	M16A	16-Lead Small Outline Integrated Circuit (SOIC), JEDEC MS-012, 0.150 Narrow
DM74LS157SJ	M16D	16-Lead Small Outline Package (SOP), EIAJ TYPE II, 5.3mm Wide
DM74LS157N	N16E	16-Lead Plastic Dual-In-Line Package (PDIP), JEDEC MS-001, 0.300 Wide
DM74LS158M	M16A	16-Lead Small Outline Integrated Circuit (SOIC), JEDEC MS-012, 0.150 Narrow
DM74LS158N	N16E	16-Lead Plastic Dual-In-Line Package (PDIP), JEDEC MS-001, 0.300 Wide

*Devices also available in Tape and Reel. Specify by appending the suffix letter "X" to the ordering code.

6.071 Digital Logic
16

There are higher level devices that are designed for specific applications. Here is a already implemented multiplexer.

74LS157 Data Sheet 2

Connection Diagrams

leaves

© 2000 Fairchild Semiconductor Corporation DS000306 www.fairchildsemi.com

DM74LS157 - DM74LS158

Function Table

Strobe	Inputs		Output Y	
	Select	A	B	DM74LS157 DM74LS158
H	X	X	X	H
L	L	L	X	L
L	L	H	X	H
L	H	X	L	L
L	H	X	H	H

H = HIGH Level
 L = LOW Level
 X = Don't Care

74LS157 Data Sheet 3

Absolute Maximum Ratings (Note 1)

Supply Voltage 7V
 Input Voltage 7V
 Operating Free Air Temperature Range 0°C to +70°C
 Storage Temperature Range -65°C to +150°C

DM74LS157 Recommended Operating Conditions

Symbol	Parameter	Min	Nom	Max	Units
V _{CC}	Supply Voltage	4.75	5	5.25	V
V _{IL}	Input Low Level Input Voltage	2			V
V _{OL}	Low Level Output Voltage			0.8	V
I _{OL}	High Level Output Current			-0.4	mA
I _{OL}	Low Level Output Current			8	mA
T _A	Free Air Operating Temperature	0		70	°C

DM74LS157 Electrical Characteristics
over recommended operating free air temperature range (unless otherwise noted)

Symbol	Parameter	Conditions	Min	Typ (Note 2)	Max	Units
V _I	Input Clamp Voltage	V _{CC} = Max, I _I = -10 mA			-1.5	V
V _{OH}	High Level Output Voltage	V _{CC} = Max, I _{OL} = Max, V _I = Max, V _{OL} = Min	2.7	3.4		V
V _{OL}	Low Level Output Voltage	V _{CC} = Min, I _{OL} = Max, V _I = Max, V _{OH} = Min	0.30	0.5		V
I _{CC}	Supply Current	V _{CC} = 4.5V, V _{OL} = Min		0.25	0.4	mA
I _I	Input Current @ Max Input Voltage	V _{CC} = Max, V _I = 7V	A or B		0.1	mA
I _I	High Level Input Current	V _{CC} = Max, V _I = 2.0V	A or B		40	µA
I _I	Low Level Input Current	V _{CC} = Max, V _I = 0.4V	A or B		-0.8	mA
I _{CC}	Short Circuit Output Current	V _{CC} = Max (Note 3)	-20		-100	mA
I _{CC}	Supply Current	V _{CC} = Max (Note 4)		0.7	1.0	mA

Note 1: All signals are at V_{CC} = 5V, T_A = 25°C.
 Note 2: Not more than one output should be shorted at a time, and the duration should not exceed one second.
 Note 3: I_{CC} is measured with A or B applied to all inputs and all outputs 100 Ω.

DM74LS157 - DM74LS158

6.071 Digital Logic
18

74LS157 Data Sheet 4


DM74LS157 Switching Characteristics
 at $V_{CC} = 5V$ and $T_A = 25^\circ C$

Symbol	Parameter	From (Input) To (Output)	$R_L = 2\ k\Omega$				Units
			$C_L = 15\ pF$		$C_L = 50\ pF$		
			Min	Max	Min	Max	
t_{PLH}	Propagation Delay Time LOW-to-HIGH Level Output	Data to Y		14		18	ns
t_{PHL}	Propagation Delay Time HIGH-to-LOW Level Output	Data to Y		14		20	ns
t_{PLS}	Propagation Delay Time LOW-to-HIGH Level Output	Strobe to Y		20		24	ns
t_{PHS}	Propagation Delay Time HIGH-to-LOW Level Output	Strobe to Y		21		30	ns
t_{PL1}	Propagation Delay Time LOW-to-HIGH Level Output	Select to Y		23		28	ns
t_{PH1}	Propagation Delay Time HIGH-to-LOW Level Output	Select to Y		27		32	ns

3


www.farchildsemi.com

Slide 20

 


The multiplexer can be expanded to many more lines. Notice that in this case each AND gate has been expanded to three inputs so that the full coding can appear at each. We would need to add one more input to each AND for every power of two increase in the number of inputs. How do you build the same circuit using the ANDs only as enables?

Slide 21

 

Of course the opposite action can also be implemented. A demultiplexer sends one signal to one of many lines.

Slide 22

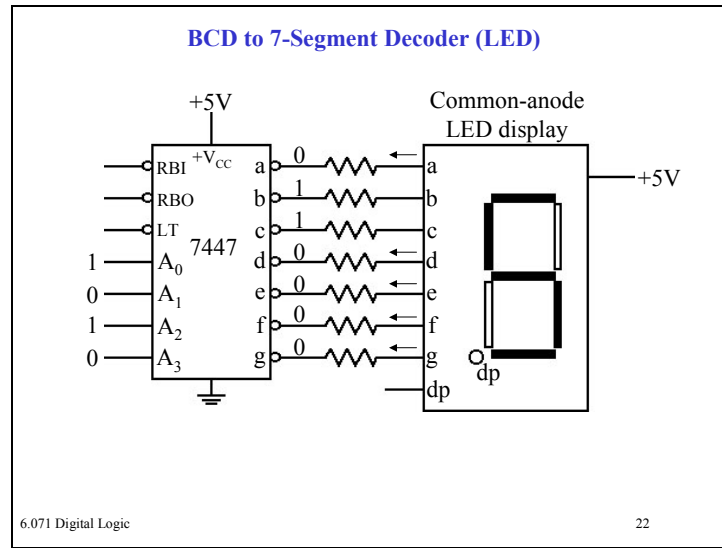

Another complex chip, in this case designed to control an LED numeric display.

7447 Data Sheet

FAIRCHILD
SEMICONDUCTOR

DM7446A, DM7447A
BCD to 7-Segment Decoders/Drivers

General Description
The 46A and 47A feature active-low outputs designed for driving common-anode LEDs or incandescent indicators directly. All of the circuits have full ripple-blanking input/output controls and a lamp test input. Segment identification and resultant displays are shown on a following page. Display patterns for BCD input counts above nine are unique symbols to authenticate input conditions.

All of the circuits incorporate automatic leading and trailing-edge, zero-blanking control (RBI and RBO). Lamp test (LT) of these devices may be performed at any time.

when the BURST mode is at a high logic level. All types contain an overdriving blanking input (OB) which can be used to control the lamp intensity (by pulsing) or to inhibit the outputs.

Features

- All series types feature lamp intensity modulation capability
- Open-collector outputs drive indicators directly
- Lamp test provision
- Leading/trailing zero suppression

March 1968

DM7446A, DM7447A BCD to 7-Segment Decoders/Drivers

Connection Diagram

16-Pin DIP Package

Order Number DM5447AJ, DM7446AN or DM7447AN
See Package Number J16A or N16E

6.071 Digital Logic

23

7447 Data Sheet 2

Absolute Maximum Ratings (Note 1)			DM54	-55°C to +125°C
Supply Voltage	7V	DM74	0°C to +70°C	
Input Voltage	5.5V	Storage Temperature Range	-65°C to +150°C	
Operating Free Air Temperature Range				

Recommended Operating Conditions

Symbol	Parameter	DM5447A			DM7447A			Units
		Min	Nom	Max	Min	Nom	Max	
V _{CC}	Supply Voltage	4.5	5	5.5	4.75	5	5.25	V
V _{BI}	High Level Input Voltage	2			2			V
V _{IL}	Low Level Input Voltage			0.8			0.8	V
V _{OH}	High Level Output Voltage (a thru g)			15			15	V
I _{OH}	High Level Output Current (BI/RBO)			-0.2			-0.2	µA
I _{OL}	Low Level Output Current (a thru g)			40			40	mA
I _{OL}	Low Level Output Current (BI/RBO)			8			8	mA
T _A	Free Air Operating Temperature	-55		125	0		70	°C

7447 Data Sheet 3

'47A Electrical Characteristics
over recommended operating free air temperature range (unless otherwise noted)

Symbol	Parameter	Conditions	Min	Typ (Note 4)	Max	Units
V_i	Input Clamp Voltage	$V_{CC} = \text{Min}, I_i = -12 \text{ mA}$			-1.5	V
V_{OH}	High Level Output Voltage (B/RBO)	$V_{CC} = \text{Min}$ $I_{OH} = \text{Max}$	2.4	3.7		V
I_{EX}	High Level Output Current (a thru g)	$V_{CC} = \text{Max}, V_O = 15\text{V}$ $V_{IL} = \text{Max}, V_{IH} = \text{Min}$			250	μA
V_{OL}	Low Level Output Voltage	$V_{CC} = \text{Min}, I_{OL} = \text{Max}$ $V_{IH} = \text{Min}, V_{IL} = \text{Max}$		0.3	0.4	V
I_i	Input Current @ Max Input Voltage	$V_{CC} = \text{Max}, V_i = 5.5\text{V}$			1	mA
I_{IH}	High Level Input Current	$V_{CC} = \text{Max}, V_i = 2.4\text{V}$			40	μA
I_{IL}	Low Level Input Current	$V_{CC} = \text{Max}$ $V_i = 0.4\text{V}$			-4	mA
I_{OS}	Short Circuit Output Current	$V_{CC} = \text{Max}$ (B/RBO)			-4	mA
I_{CC}	Supply Current	$V_{CC} = \text{Max}$ (Note 5)			60 85 103	mA

Note 4: All typicals are at $V_{CC} = 5\text{V}, T_A = 25^\circ\text{C}$.

'47A Switching Characteristics
at $V_{CC} = 5\text{V}$ and $T_A = 25^\circ\text{C}$ (See Section 1 for Test Waveforms and Output Load)

Symbol	Parameter	Conditions	Min	Max	Units
t_{PLH}	Propagation Delay Time Low to High Level Output	$C_L = 15 \text{ pF}$ $R_L = 120\Omega$		100	ns
t_{PHL}	Propagation Delay Time High to Low Level Output			100	ns

7447 Data Sheet 4

Function Table

46A, 47A

Decimal or Function	Inputs					BIRBO (Note 6)	Outputs							Note	
	LT	RBI	D	C	B		A	a	b	c	d	e	f		g
0	H	H	L	L	L	L	H	L	L	L	L	L	L	H	
1	H	X	L	L	L	H	H	H	L	L	H	H	H	H	
2	H	X	L	L	H	L	H	L	L	H	L	L	H	L	
3	H	X	L	L	H	H	H	L	L	L	L	H	H	L	
4	H	X	L	H	L	L	H	H	L	L	H	H	L	L	
5	H	X	L	H	L	H	H	L	H	L	L	H	L	L	
6	H	X	L	H	H	L	H	H	H	L	L	L	L	L	
7	H	X	L	H	H	H	H	L	L	L	H	H	H	H	(Note 7)
8	H	X	H	L	L	L	H	L	L	L	L	L	L	L	
9	H	X	H	L	L	H	H	L	L	L	H	H	L	L	
10	H	X	H	L	H	L	H	H	H	L	L	L	H	L	
11	H	X	H	L	H	H	H	H	H	L	L	H	H	L	
12	H	X	H	H	L	L	H	H	L	H	H	H	L	L	
13	H	X	H	H	L	H	H	L	H	H	L	H	L	L	
14	H	X	H	H	H	L	H	H	H	L	L	L	L	L	
15	H	X	H	H	H	H	H	H	H	H	H	H	H	H	
BI	X	X	X	X	X	X	L	H	H	H	H	H	H	H	(Note 8)
RBI	H	L	L	L	L	L	L	H	H	H	H	H	H	H	(Note 9)
LT	L	X	X	X	X	X	H	L	L	L	L	L	L	L	(Note 10)

H = High level, L = Low level, X = Don't Care
 Note 6: BIRBO is a wire-OR'd logic serving as blanking input (BI) and/or ripple blanking output (RBO).
 Note 7: The blanking input (BI) must be open or held at a high logic level when output functions 0 through 15 are decoded. The ripple blanking input (RBI) must be open or high if blanking of a decimal zero is not desired.
 Note 8: When a low logic level is applied directly to the blanking input (BI), all segment outputs are high regardless of the level of any other input.
 Note 9: When ripple-blanking input (RBI) and inputs A, B, C, and D are at a low level with the lamp test input high, all segment outputs go 11 and the ripple-blanking output (RBO) goes to a low level (response condition).
 Note 10: When the blanking input/ripple-blanking output (BIRBO) is open or held high and a low is applied to the lamp test input, all segment outputs are 1.