

### 3 - 19

$S = 500 \text{ MVA}$ ,  $V_L = V_{ph} = 345 \text{ kV}$ ,  $\Delta$ -Load,  $\text{PF} = 0.866$  lagging

$$I_{ph} = \frac{(500,000/3)}{345} \angle -\cos^{-1} 0.866 = 483.1 \angle -30^\circ \text{ A}$$

$$\textcircled{a} \quad Z_{\Delta, ph} = \frac{345 \angle 0^\circ \text{ kV}}{483.1 \angle -30^\circ \text{ A}} = 714.2 \angle 30^\circ \Omega$$

$$Z_{Y, ph} = \frac{1}{3} Z_{\Delta, ph} = 238 \angle 30^\circ \Omega$$

$$\textcircled{b} \quad I_{ph} = 483.1 \angle -30^\circ \text{ A}$$

$$I_L = \sqrt{3} I_{ph} \angle 30^\circ = \sqrt{3} (483.1 \angle -30^\circ) \angle 30^\circ = 836.8 \angle 10^\circ \text{ A}$$

$$\textcircled{c} \quad P_{ph} = \frac{500}{3} \cos 30^\circ = 144.3 \text{ MW}$$

$$Q_{ph} = \frac{500}{3} \sin 30^\circ = 83.3 \text{ MVAR}$$

$$\textcircled{d} \quad P_T = 3 P_{ph} = 500 \cos 30^\circ = 433 \text{ MW}$$

$$Q_T = 3 Q_{ph} = 500 \sin 30^\circ = 250 \text{ MVAR}$$

### 3-22

$$S_M = 40 \text{ kVA}, V_M = 230 \text{ V}, PF_M = 0.65 \text{ lagging}$$

$$P_M = 40 (0.65) = 26 \text{ kW}$$

$$\theta_M = \cos^{-1} 0.65 = 49.46^\circ$$

$$\textcircled{a} \quad Q_M = P_M \tan \theta_M = 26 \tan 49.46^\circ = 30.4 \text{ kVAR}$$

$$PF_{\text{new}} = 0.95$$

$$\theta_{\text{new}} = \cos^{-1} 0.95 = 18.19^\circ$$

$$Q_{\text{new}} = P_M \tan \theta_{\text{new}} = 8.54 \text{ kVAR} = Q_M + Q_C$$

$$\therefore Q_C = Q_{\text{new}} - Q_M = 8.54 - 30.4 = -21.86 \text{ kVAR}$$

$$\textcircled{b} \quad I_{\text{before}} = \frac{40,000}{\sqrt{3} (230)} \angle -\cos^{-1} 0.65^\circ = 100 \angle -49.46^\circ$$

$$I_{\text{after}} = \frac{26,000}{\sqrt{3} (230) (0.95)} \angle -\cos^{-1} 0.95^\circ = 68.7 \angle -18.19^\circ$$

### 3-23

$$S_1 = 15 \text{ kVA}, V_L = 2400 \angle 10^\circ, \text{PF} = 0.8 \text{ leading}$$

$$P_2 = 20 \text{ kW}, V_L = 2400 \angle 10^\circ, \text{PF}_2 = 0.9 \text{ leading}$$

$$\textcircled{a} \quad I_1 = \frac{15,000}{\sqrt{3}(2400)} \angle \cos^{-1} 0.8 = 3.61 \angle -36.9^\circ \text{ A}$$

$$I_2 = \frac{20,000}{\sqrt{3}(2400)(0.9)} \angle \cos^{-1} 0.9 = 5.34 \angle 25.8^\circ \text{ A}$$

$$\textcircled{b} \quad P_1 = 15 \cos 10^\circ = 12 \text{ kW}$$

$$Q_1 = 15 \sin 36.9^\circ = 9 \text{ kVAR}$$

$$P_2 = 20 \text{ kW}$$

$$Q_2 = -20 \tan 25.8^\circ = -9.7 \text{ kVAR}$$

$$\textcircled{c} \quad I_T = I_1 + I_2 = 3.61 \angle -36.9^\circ + 5.34 \angle 25.8^\circ = 7.7 \angle 11.2^\circ \text{ A}$$

$$\textcircled{d} \quad P_T = P_1 + P_2 = 12 + 20 = 32 \text{ kW}$$

$$Q_T = Q_1 + Q_2 = 9 - 9.7 = -0.7 \text{ kVAR}$$

$$\textcircled{e} \quad \text{PF} = \cos 11.2^\circ = 0.999 \text{ leading}$$

- - -

### 3-25

$$P_1 = 50 \text{ kW}, V = 460 \text{ V}_{LL}, \text{PF} = 0,866 \text{ lagging}$$

$$S_2 = 36 \text{ kVA}, V = 460 \text{ V}_{LL}, \text{PF} = 0,9 \text{ leading}$$

$$Z_{far} = 0,5 + j2,0 \Omega, V_{ph} = \frac{460}{\sqrt{3}} \angle 0^\circ = 265,6 \angle 0^\circ \text{ V}_{LN}$$

$$I_1 = \frac{50,000 \angle -0,866}{\sqrt{3}(460)(0,866)} = 72,46 \angle -30^\circ \text{ A}$$

$$I_2 = \frac{36,000}{\sqrt{3}(460)} \angle 0,9^\circ = 45,18 \angle 25,8^\circ \text{ A}$$

$$\textcircled{a} \quad Z_1 = \frac{265,6 \angle 0^\circ}{72,46 \angle -30^\circ} = 3,66 \angle 30^\circ \Omega$$

$$Z_2 = \frac{265,6 \angle 0^\circ}{45,18 \angle 25,8^\circ} = 5,88 \angle -25,8^\circ \Omega$$

$$\textcircled{b} \quad I_T = I_1 + I_2 = 72,46 \angle -30^\circ + 45,18 \angle 25,8^\circ = 104,7 \angle -9,1^\circ$$

$$\textcircled{c} \quad V_B = V_{ph} + Z_{far} I_T = 265,6 \angle 0^\circ + (0,5 + j2,0) \times 104,7 \angle -9,1^\circ$$

$$= 402,7 \angle 29,5^\circ \text{ V}_{LN}$$

$$= 697,5 \angle 59,5^\circ \text{ V}_{LL}$$

$$\textcircled{d} \quad S_B = \sqrt{3} V_B I_T^* = \sqrt{3} (697,5 \angle 29,5^\circ) (104,7 \angle -9,1^\circ)^*$$

$$= 126,5 \angle 38,6^\circ \text{ kVA}$$

$$= 98,86 + j78,92 \text{ kVA}$$

$$P_B = 98,86 \text{ kW}$$

$$Q_B = 78,92 \text{ kVAR}$$

## 3-26

$$Z_\Delta = 45 \angle 60^\circ \Omega ; Z_{fdr} = 1.2 + j1.6 \Omega$$

$$\textcircled{a} \quad Z_y = \frac{1}{3} Z_\Delta = 15 \angle 60^\circ = 7.5 + j13 \Omega$$

$$Z_T = Z_{fdr} + Z_y = 7.5 + j13 + 1.2 + j1.6 = 8.7 + j14.6 \Omega$$

$$I = \frac{V_{ph}}{Z_T} = \frac{(208/\sqrt{3}) \angle 0^\circ}{8.7 + j14.6} = 7.06 \angle -59.2^\circ A$$

$$\begin{aligned} V_{load} &= V_{ph} - Z_{fdr} I = 120 \angle 0^\circ - (1.2 + j1.6)(7.06 \angle -59.2^\circ) \\ &= 120 + j0 - (14.04 - j1.49) = 106 \angle 0.81^\circ V_{LN} \\ &= 183.6 \angle 30.81^\circ V_{LL} \end{aligned}$$

$$\textcircled{b} \quad Z_{c,\Delta} = 60 \angle -90^\circ = -j60 \Omega$$


$$Z_{c,y} = \frac{1}{3} Z_{c,\Delta} = 20 \angle -90^\circ = -j20 \Omega$$

$$Z_{eq} = \frac{(7.5 + j13)(-j20)}{7.5 + j13 - j20} = 28.5 + j6.6 \Omega$$

$$I = \frac{120 \angle 0^\circ}{28.5 + j6.6 + 1.2 + j1.6} = \frac{120 + j0}{29.7 + j8.2} = 3.89 \angle -15.4^\circ A$$

$$\begin{aligned} V_{load} &= 120 \angle 0^\circ - (1.2 + j1.6)(3.89 \angle -15.4^\circ) \\ &= 120 + j0 - (6.16 + j4.76) \\ &= 113.9 \angle -2.4^\circ \\ &= 197.3 \angle 27.6^\circ \end{aligned}$$

### 3-27

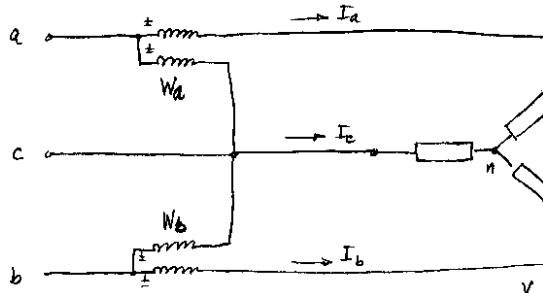

$$|I| = \frac{S}{\sqrt{3}V} = \frac{30,000}{\sqrt{3}(2400)} = 7.22A$$

$$P_a = V_{ac} I_a \cos \alpha \left[ \frac{V_{ac}}{I_a} \right]$$

$$P_b = V_{bc} I_b \cos \beta \left[ \frac{V_{bc}}{I_b} \right]$$

④ PF = 1.0 ;  $\theta = \cos^{-1} 1.0 = 0^\circ$

$$P_a = (2400)(7.22) \cos 0^\circ = 15 \text{ kW}$$

$$P_b = (2400)(7.22) \cos 0^\circ = 15 \text{ kW}$$

⑤ PF = 0.2 ;  $\theta = \cos^{-1} 0.2 = 78.5^\circ$  lagging

$$P_a = (2400)(7.22) \cos (30^\circ - 78.5^\circ) = 11.48 \text{ kW}$$

$$P_b = (2400)(7.22) \cos (30^\circ + 78.5^\circ) = -5.5 \text{ kW}$$

⑥ PF = 0.5 ;  $\theta = \cos^{-1} 0.5 = 60^\circ$  leading

$$P_a = (2400)(7.22) \cos (30^\circ + 60^\circ) = 0$$

$$P_b = (2400)(7.22) \cos (30^\circ - 60^\circ) = 15 \text{ kW}$$

